

CS & IT ENGINEERING

Digital Logic
Logic Gate



Lecture No. 07



By- CHANDAN SIR



TOPICS TO
BE
COVERED

X-NOR GATE

01 Question Practice

02 Discussion

$$\underline{\underline{t_e}} \rightarrow \underline{t.me / CSIR}$$

number of 1 = parity



Odd number of 1 detector

→ Odd parity detector

X-NOR GATE :-

① Symbol



$$\overline{A \oplus B} = A \odot B = \overline{A} \overline{B} + AB$$

② Truth Table

A	B	$A \odot B$
0	0	1
0	1	0
1	0	0
1	1	1

③ $A = B \quad Y = 1$

$A \neq B \quad Y = 0$

④ Even parity Detector
Equal Detector
Equivalence Logic
Coincidence Logic


⑤

$$A \odot A = 1$$


$$A \odot 1 = A$$

$$A \odot \bar{A} = 0$$

$$A \odot 0 = \bar{A}$$

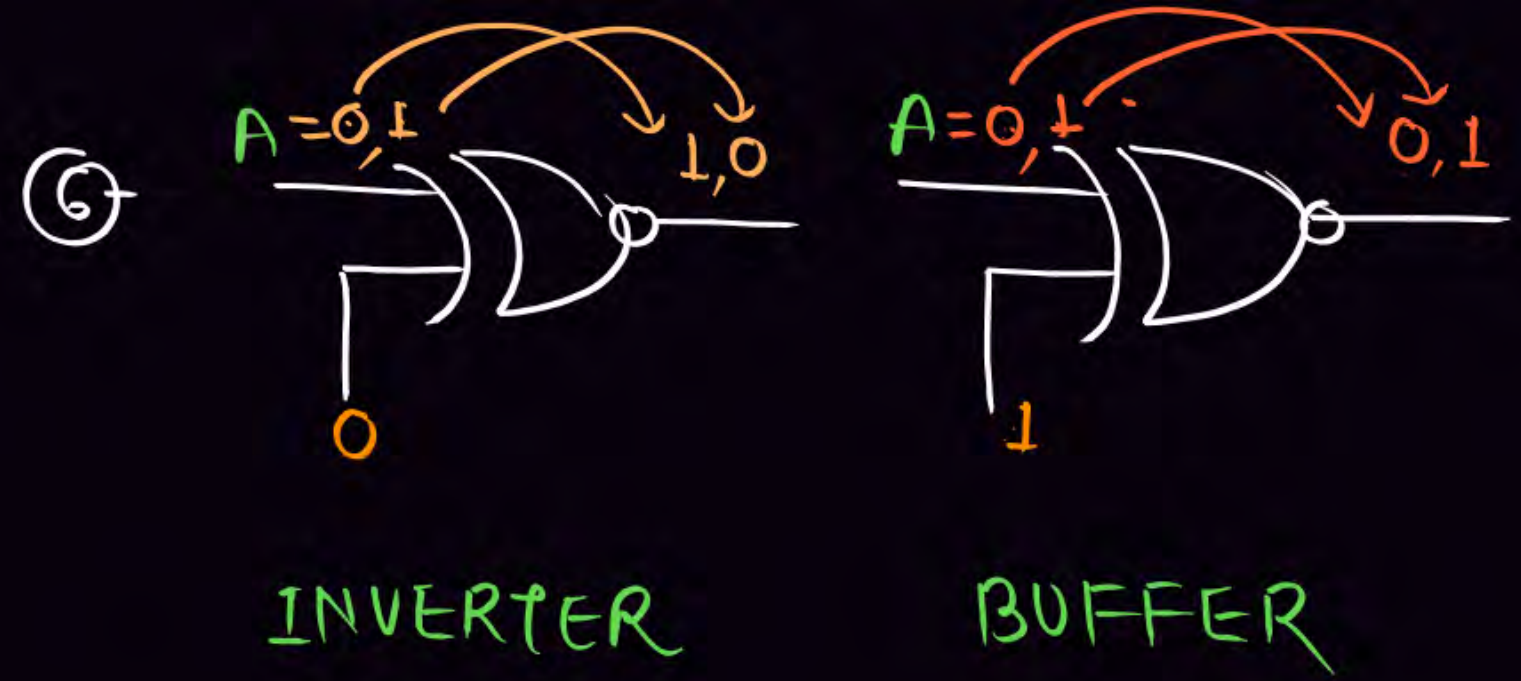

Ex

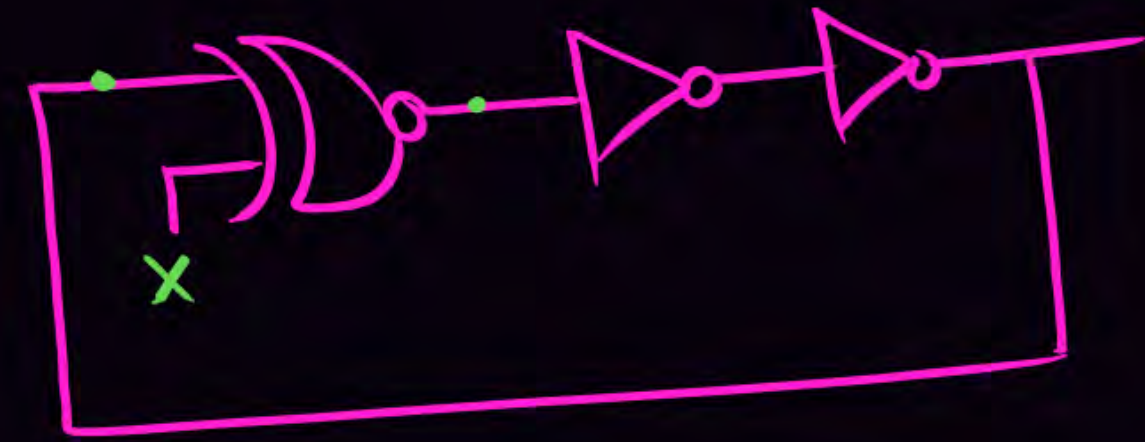


- (A) Astable Multivibrator $x=0$
 (B) Bistable Multivibrator $x=1$

⑦ X-NOR GATE Commutative as well as associative Law
follow karta hai...

EVEN NUMBER OF INPUT :->

Case (1)

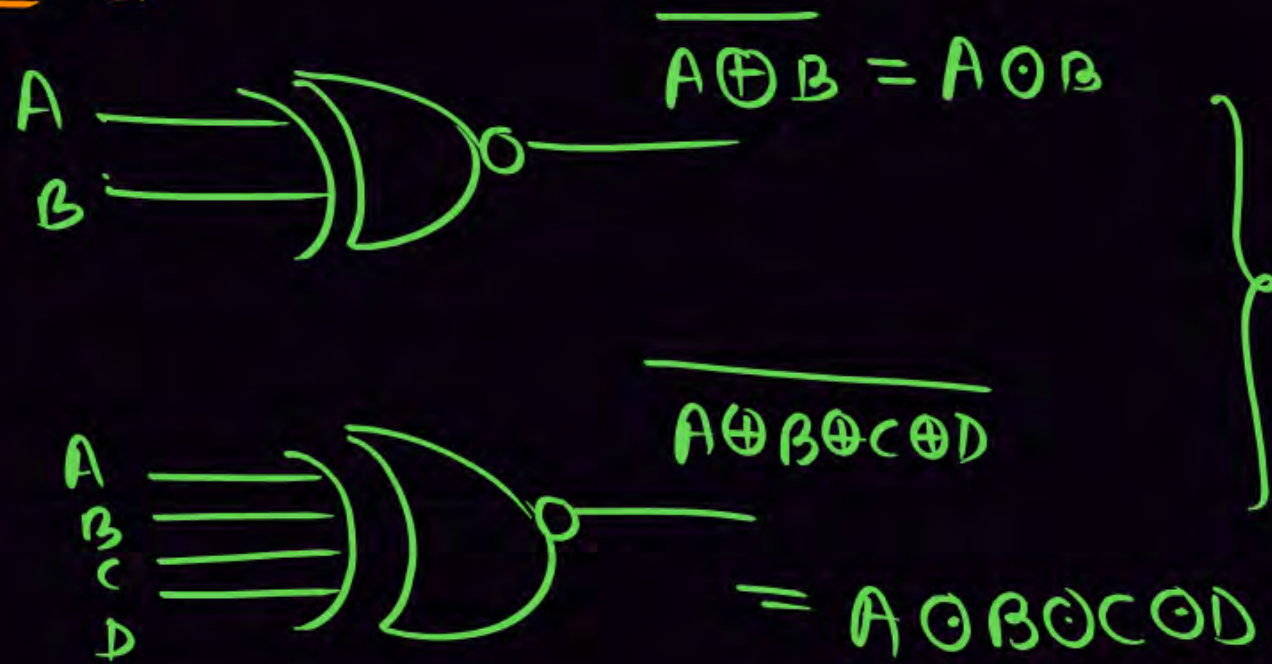


Output will be high for even no. of inputs are high.

$$A \odot B = \overline{A \oplus B}$$

$$A \odot B \odot C \odot D = \overline{A \oplus B \oplus C \oplus D}$$

Case (2)

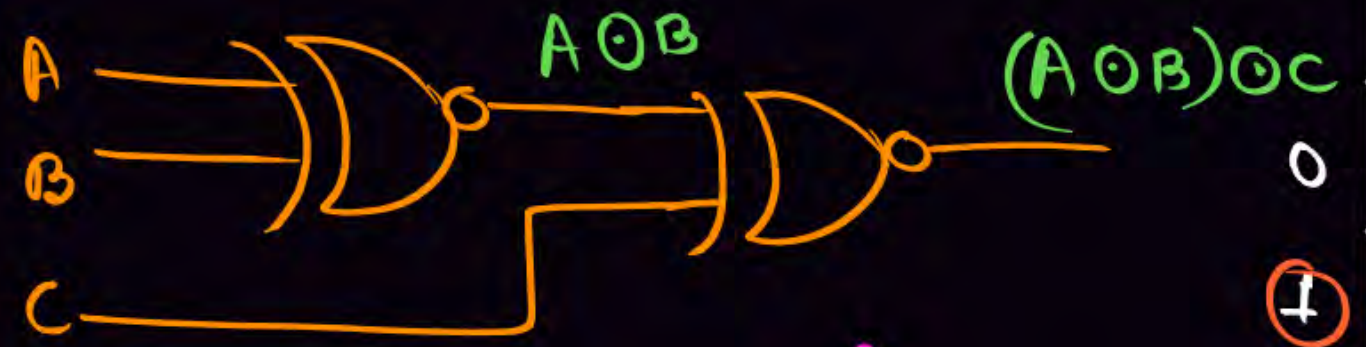




$$(A \odot B) \odot C = A \odot (B \odot C)$$

→ Associative Law ✓



	A	B	C	$(A \odot B) \odot C$	$A \odot (B \odot C)$
0	0	0	0	0	0
①	0	0	1	1	1
②	0	1	0	1	1
3	0	1	1	0	0
④	1	0	0	1	1
5	1	0	1	0	0
6	1	1	0	0	0
⑦	1	1	1	1	1


$$(A \oplus B) \oplus C = A \oplus B \oplus C$$


For Even Variables.

$$A \odot B = \overline{A \oplus B}$$

$$A \odot B \odot C \odot D = \overline{A \oplus B \oplus C \oplus D}$$

$$A \odot B \odot C \odot D \odot E \odot F = \overline{A \oplus B \oplus C \oplus D \oplus E \oplus F}$$

* o/p will be high for even no. of 1's in the inputs.




For odd variables.

$$(A \odot B) \odot C = A \oplus B \oplus C$$

$$(((A \odot B) \odot C) \odot D) \odot E = A \oplus B \oplus C \oplus D \oplus E$$

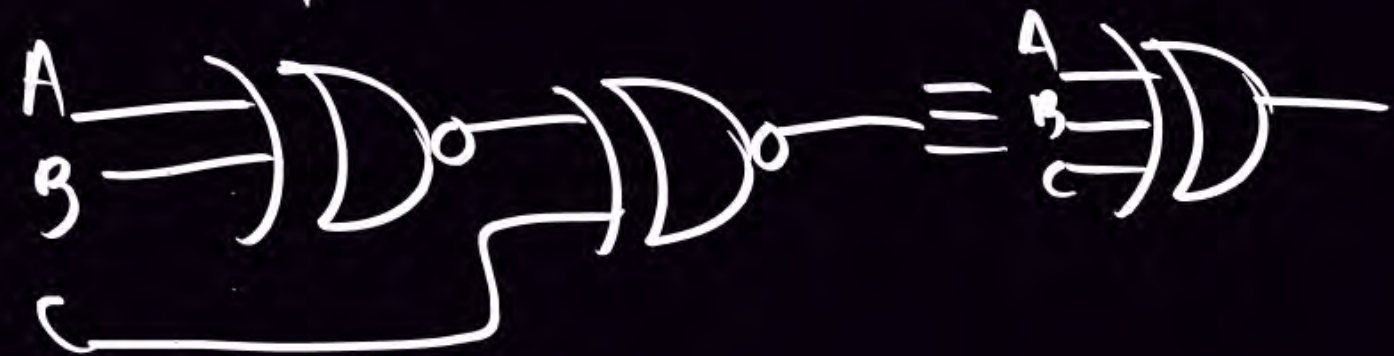O/p will be high for odd number of 1's in the inputs.






Impractical (Theoretical)



o/p will be high for even inputs
are high.

Magic

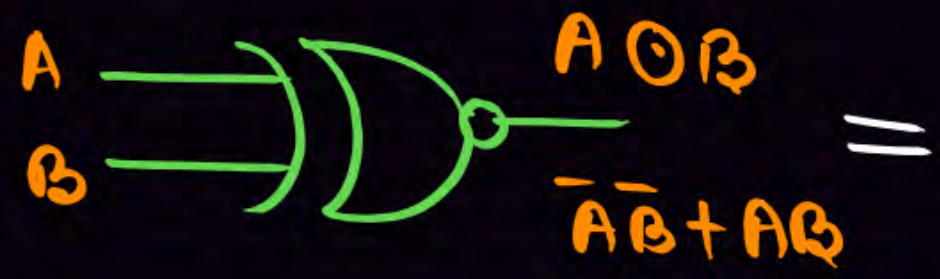

=






$\bar{B} = X$

$$\bar{A}X + A\bar{X}$$

$$\bar{A}\bar{B} + A\bar{B}$$

$$\bar{A}\bar{B} + AB = A \oplus B$$

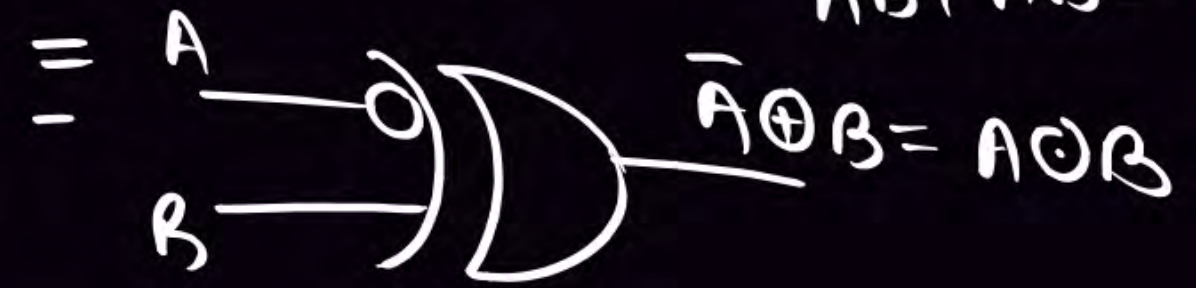

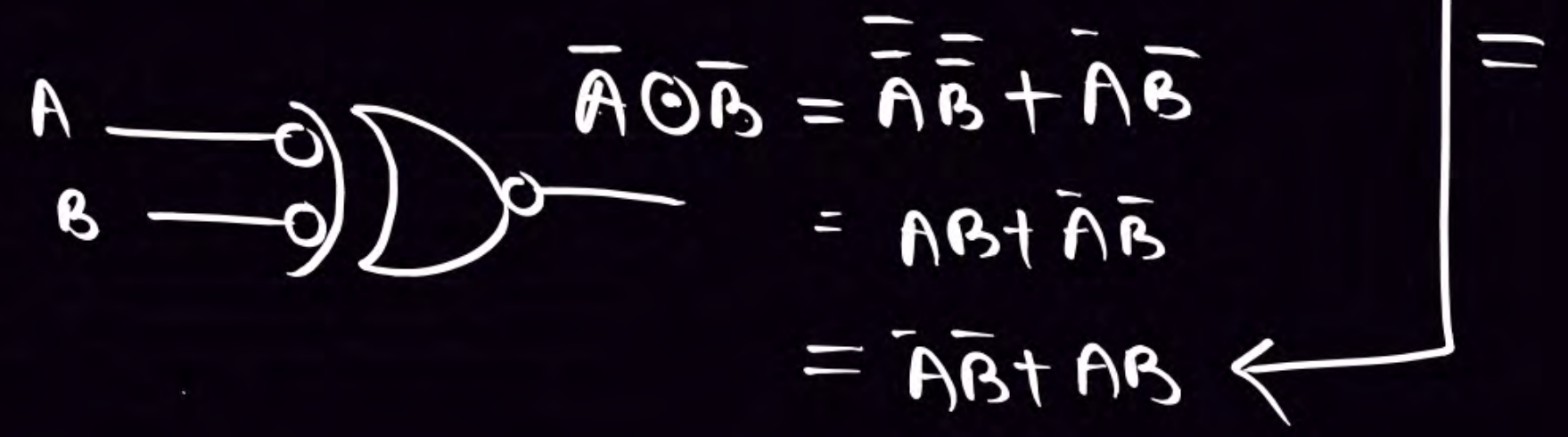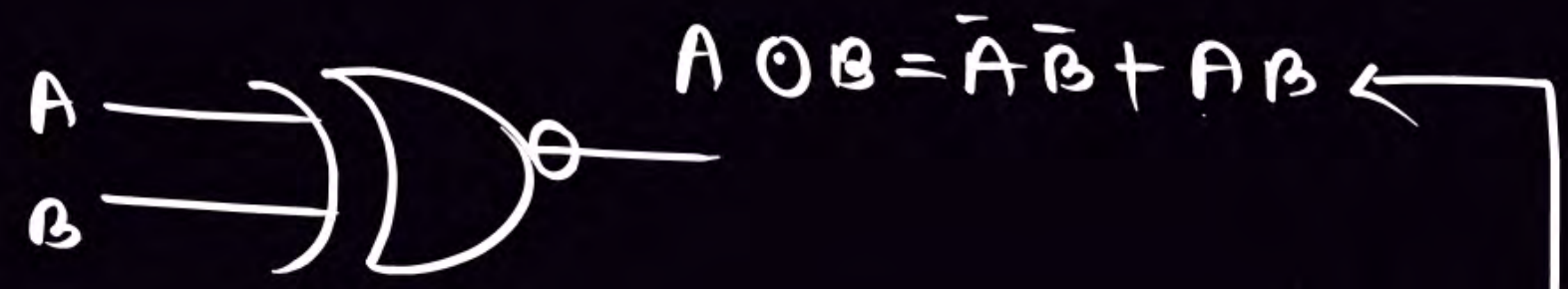

$=$

♥ $A \odot B = \bar{A} \oplus B = A \oplus \bar{B} = \bar{A} \odot \bar{B} = \overline{A \oplus B}$

♥ $A \oplus B = \bar{A} \odot B = A \odot \bar{B} = \bar{A} \oplus \bar{B} = \overline{A \odot B}$

HW

Q1 $\bar{A} \oplus B \oplus C =$

Q2 $A \oplus B \oplus AB$

Q3 $(A \odot B) \oplus C$

Q4 $(A \oplus B) \odot C$

Q.1

"MSQ"



The Boolean function given below:

$$f(A, B) = A \oplus B \oplus AB = A \oplus B \oplus X$$

which statement is/are correct?

A	B	AB	$A \oplus B \oplus X$
0	0	0	0
0	1	0	1
1	0	0	1
1	1	1	1

A, C

$$f = A + B$$

- ☒ A It is a OR GATE
- ☐ B It is a NAND GATE
- ☒ C It requires 3 NAND gate to implement the function
- ☐ D It required 2 NAND gates to implement the function

$$f(A, B) = \underline{(A \oplus B)} \oplus AB$$

$$= X \oplus AB$$

$$= \bar{X}AB + X\bar{A}\bar{B}$$

$$= [\bar{A}\bar{B} + AB] \cdot AB + [\bar{A}B + A\bar{B}] \cdot [\bar{A} + \bar{B}]$$

$$= \cancel{\bar{A}\bar{B}}^0 AB + AB \cdot AB + \bar{A}B \cdot \bar{A} + \cancel{A\bar{B}}^0 \bar{A} + \cancel{\bar{A}\bar{B}}^0 \bar{B} + A\bar{B} \cdot \bar{B}$$

$$= AB + \bar{A}B + A\bar{B}$$

$$= AB + A\bar{B} + \bar{A}B$$

$$= A[B + \bar{B}] + \bar{A}B$$

$$= A \cdot 1 + \bar{A}B \Rightarrow \overset{\text{OR}}{A + \bar{A}B} = (A + \bar{A})(A + B) = A + B$$

$$A \oplus B = X = \bar{A}B + A\bar{B}$$

$$\overline{A \oplus B} = \bar{X} = A \odot B = \bar{A}\bar{B} + AB$$

Q.2

MCQ

Minimized expression will be $Y = A \oplus (A + B)$

A $A \oplus B$

B $A \odot B$

C $\bar{A} \cdot B$

D $A + B$

Associative Law
does not follow
by X-OR GATE
OVER OR GATE

~~$$\begin{aligned}
 &A \oplus (A + B) \\
 &(A \oplus A) + (A \oplus B) \\
 &0 + A \oplus B \\
 &A \oplus B
 \end{aligned}$$~~

$$A + B = X$$

$$A \oplus X$$

$$\bar{A}X + A\bar{X}$$

$$\overline{A+B} = \bar{A} \cdot \bar{B}$$

$$\bar{A}[A+B] + A[\overline{A+B}]$$

$$\bar{A} \cdot \overset{0}{A} + \bar{A} \cdot B + A \cdot \overset{0}{\bar{A} \cdot \bar{B}}$$


$$= \bar{A}B$$

$$A \oplus (A+B)$$

$$A \oplus X$$

A	B	A	$A+B$ X	$A \oplus X$
0	0	0	0	0
0	1	0	1	1
1	0	1	1	0
1	1	1	1	0
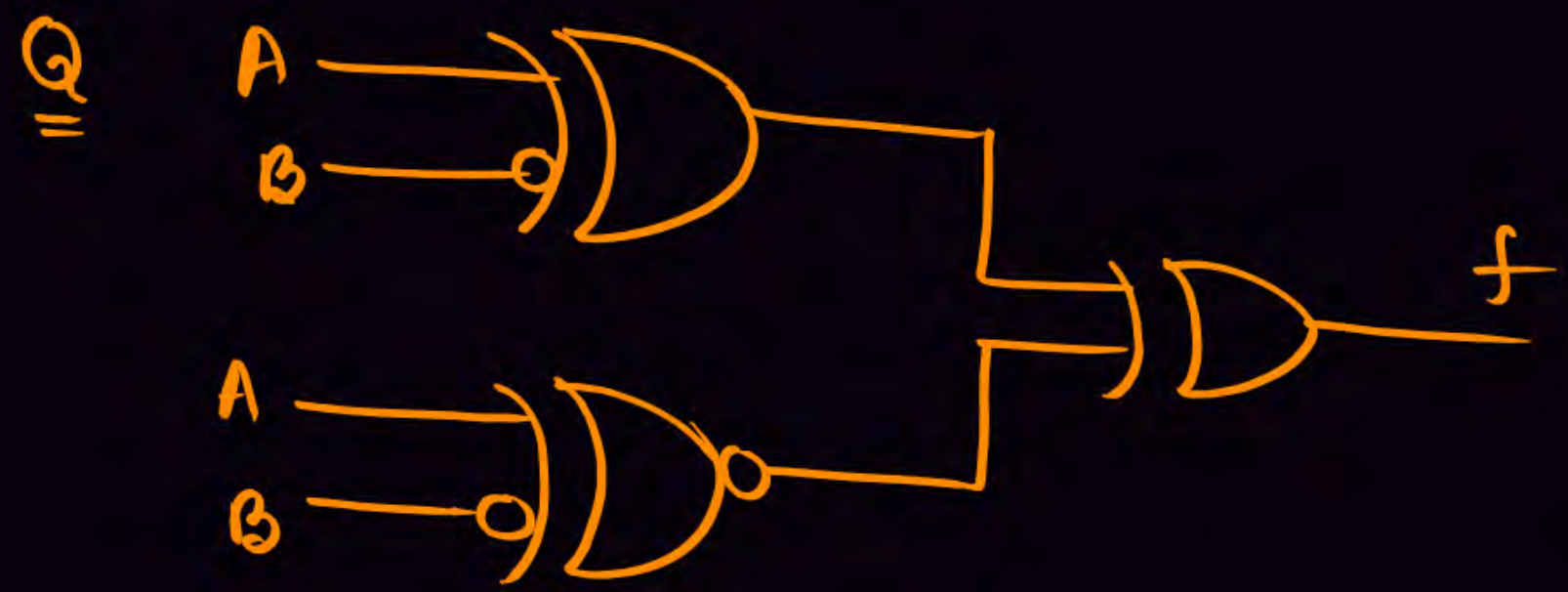
$$\begin{aligned}
 A \oplus X &= \bar{A}X \\
 &= \bar{A}(A+B) \\
 &= \bar{A} \cdot A + \bar{A}B \\
 &= \bar{A}B \quad \underline{\underline{Ans}}
 \end{aligned}$$



f will be = ?

(A)



~~(B) 1~~

(C) $A \oplus B$

(D) $A \odot B$

(E) $A \oplus B \oplus \dots \oplus A \oplus B \oplus \dots \oplus A \oplus B$

Q

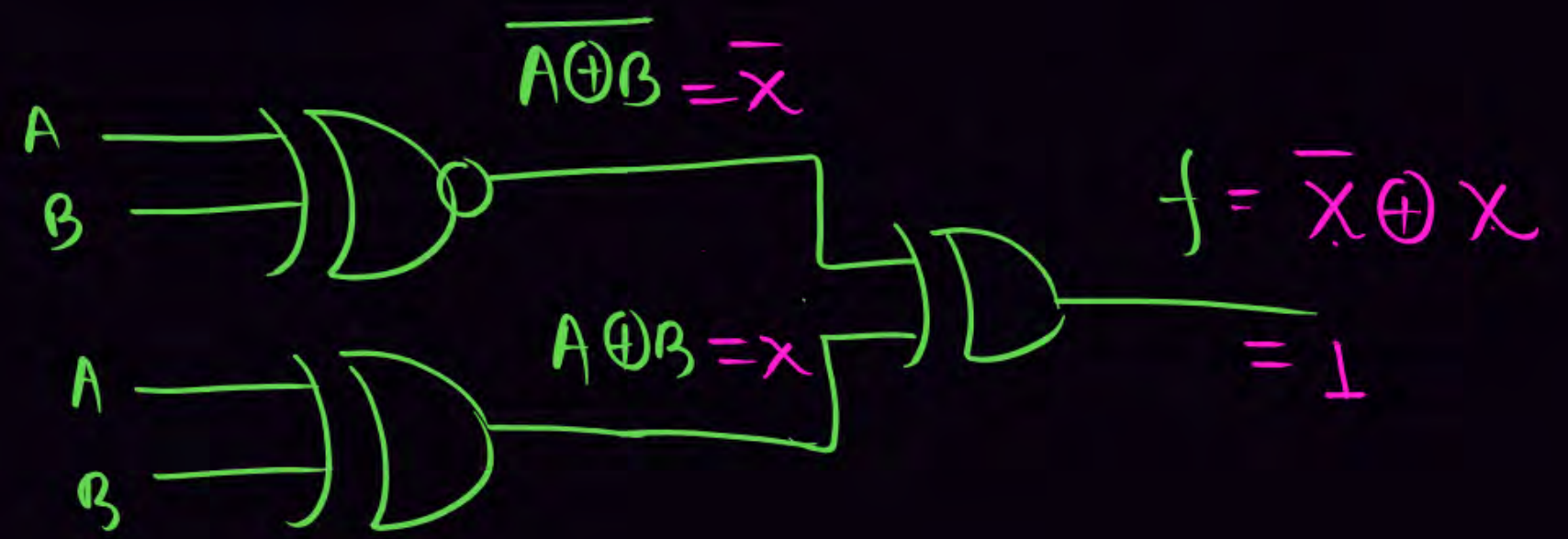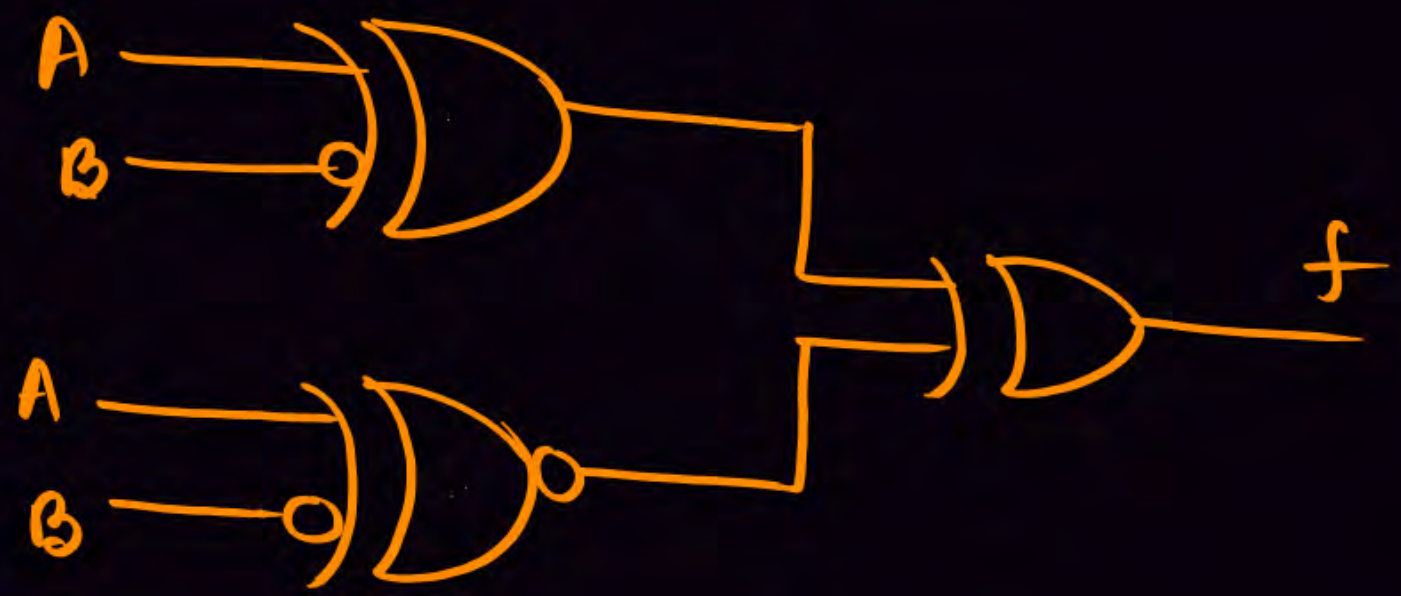


Q.3

MSQ

If the output $y = 1$
Then correct input is/are-

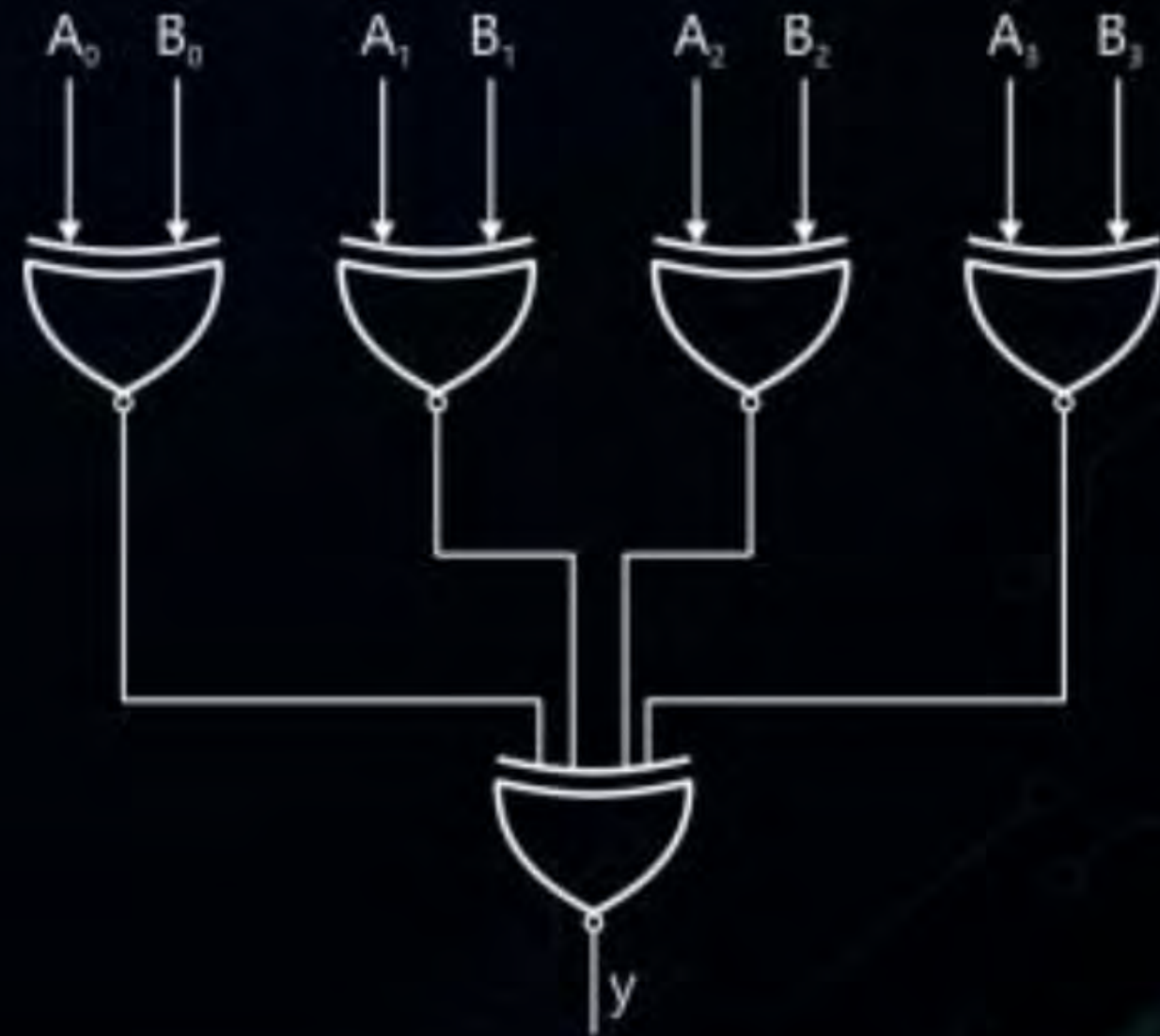
- A** 1111, 0000
- B** 1010, 0111
- C** 0101, 0101
- D** 1100, 1110



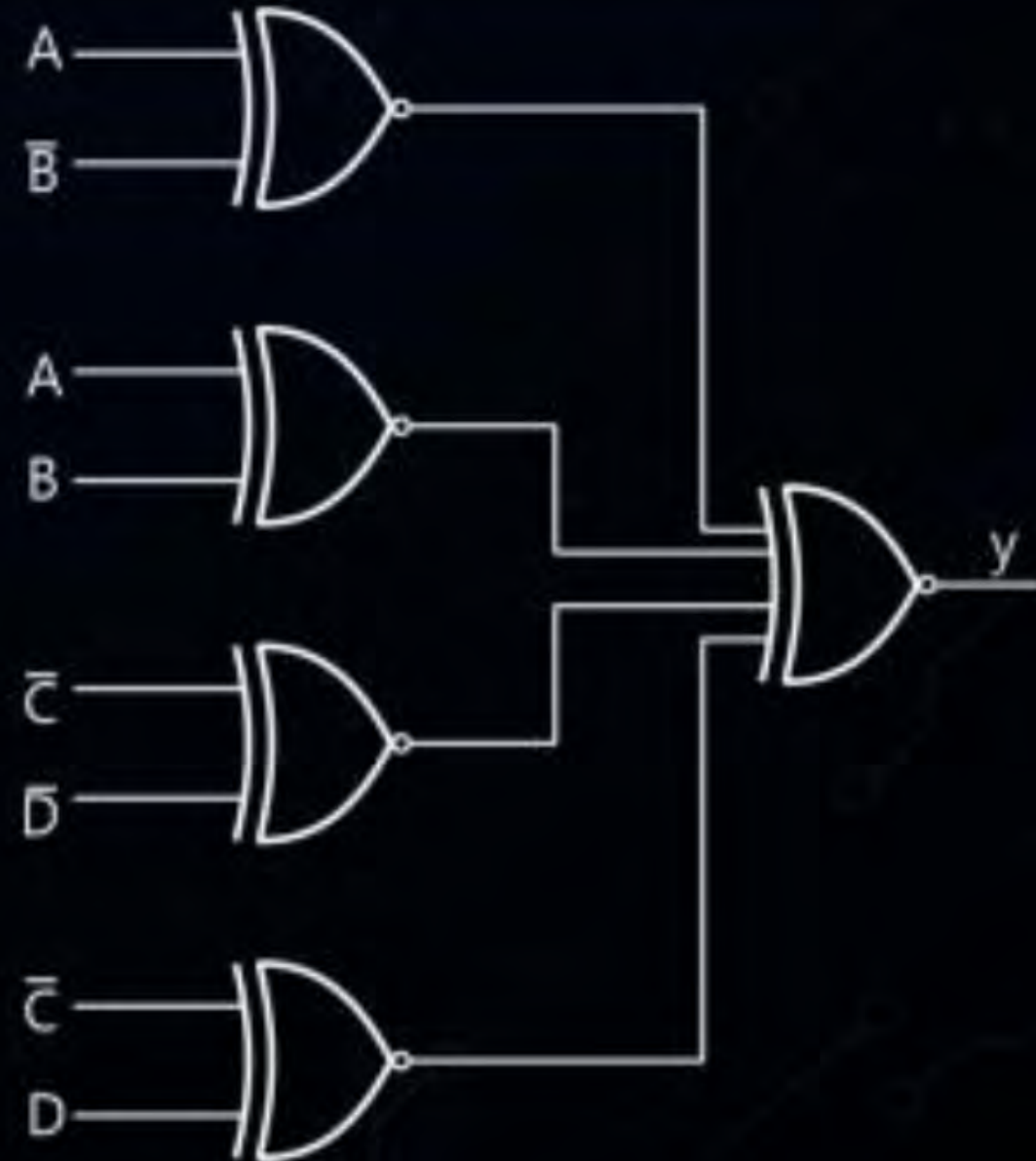Q.4

Output y will be-

- A** 0
- B** 1
- C** $A \oplus B$
- D** $A \oplus B \oplus C \oplus D$




Logic Gates



Q.5

The output f for the given logic circuit will be-

- A** 0
- B** 1
- C** $A + B$
- D** None

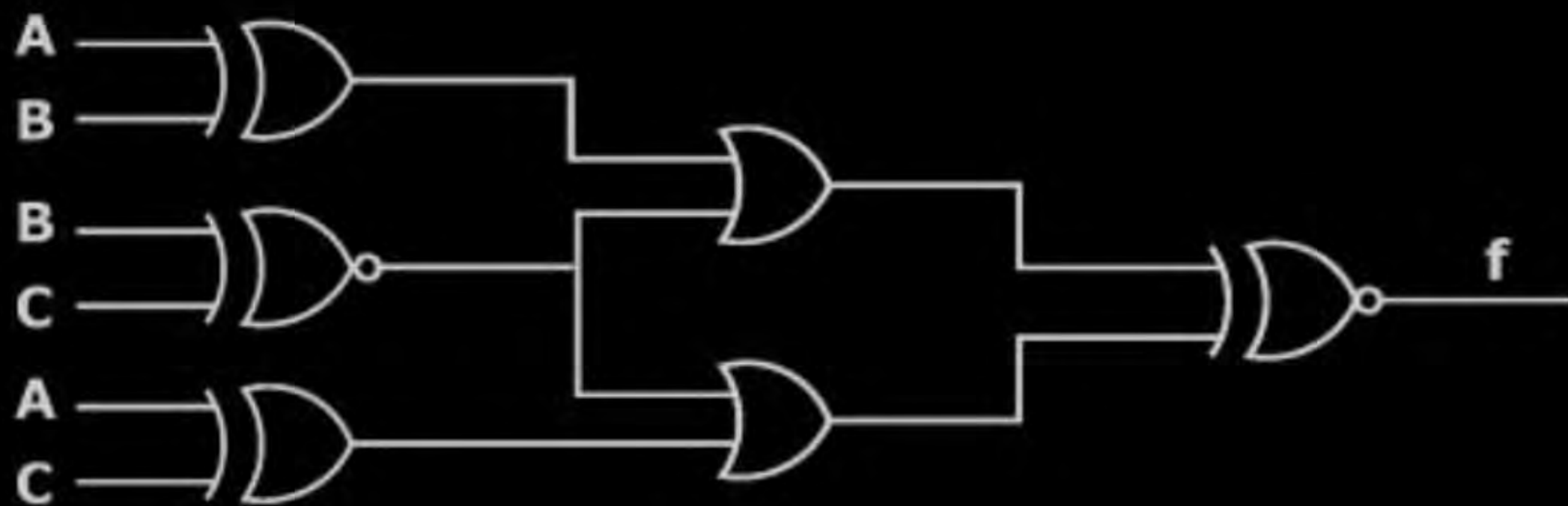

Logic Gates



Q.6


The Following logic gate circuit is equivalent to

A NAND

B OR

C XOR

D NOT

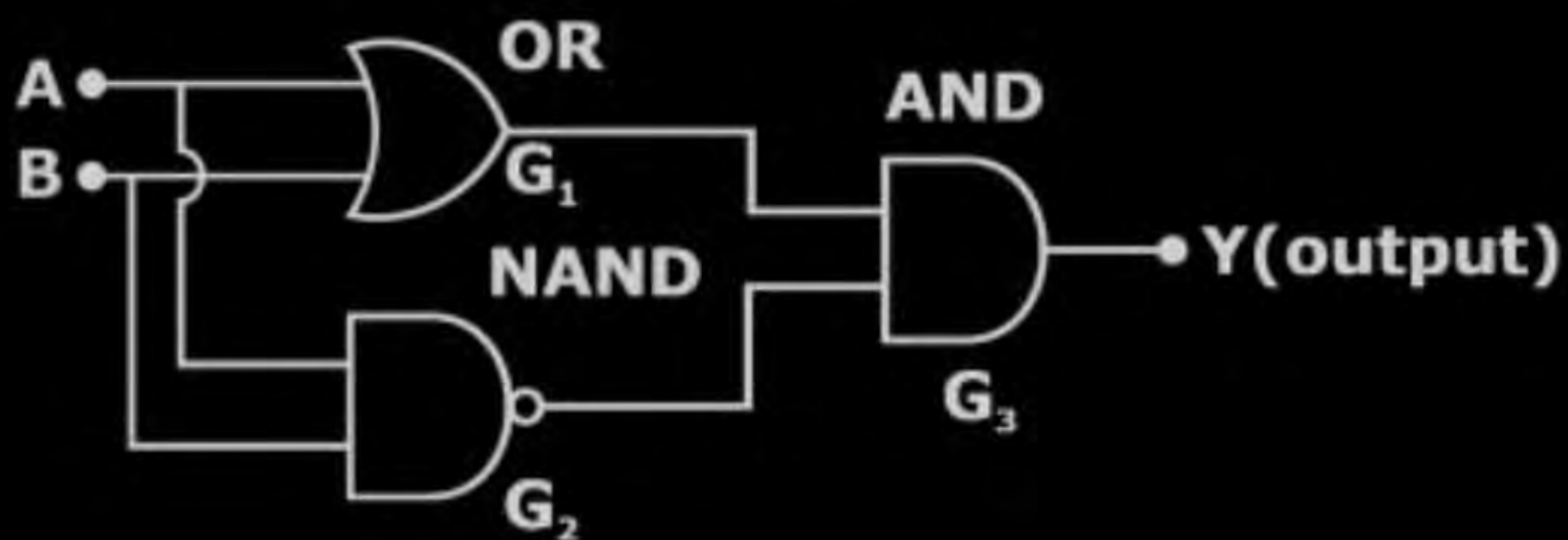

Q.7

The minimum number of two input NAND gates required to implement $y = abcd$ is

A 3

B 4

C 5

D 6


Logic Gates

MSQ

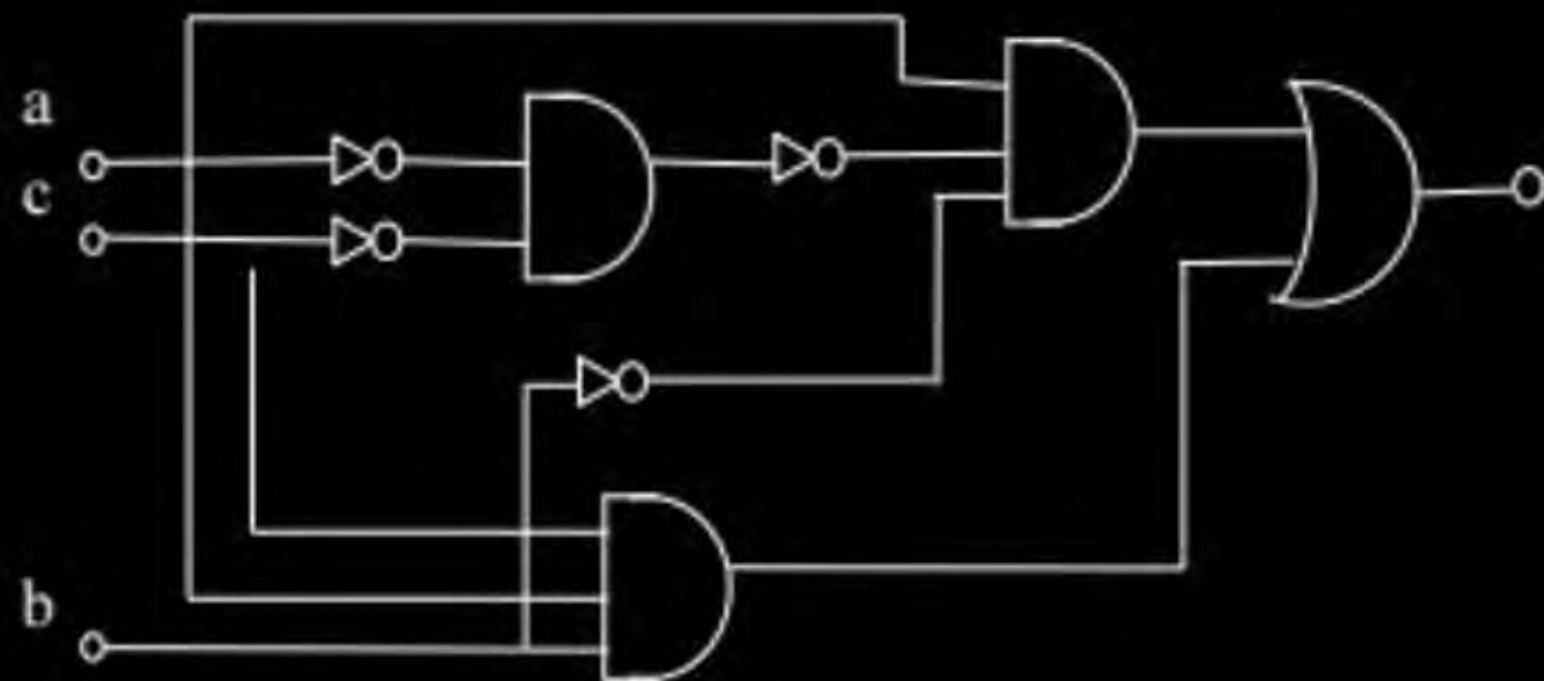Q.8

In the logic circuit shown below, how many AND, how many OR and how many NOT gates are redundant?

- A** 2 AND gates and 3 NOT gates
- B** 2 AND gates and 2 NOT gates
- C** 2 AND gates, 2 NOT gates
- D** 3 AND gates and 3 NOT gates



Q.8


The digital circuit shown below, is observed to generate output $y = 1$. Which one of the following input condition does so?

A $x_1 = x_3 = 1, x_2 = 0$

B $x_1 = 0, x_2 = x_3 = 1$


C $x_1 = x_2 = x_3 = 0$

D $x_1 = x_2 = x_3 = 1$

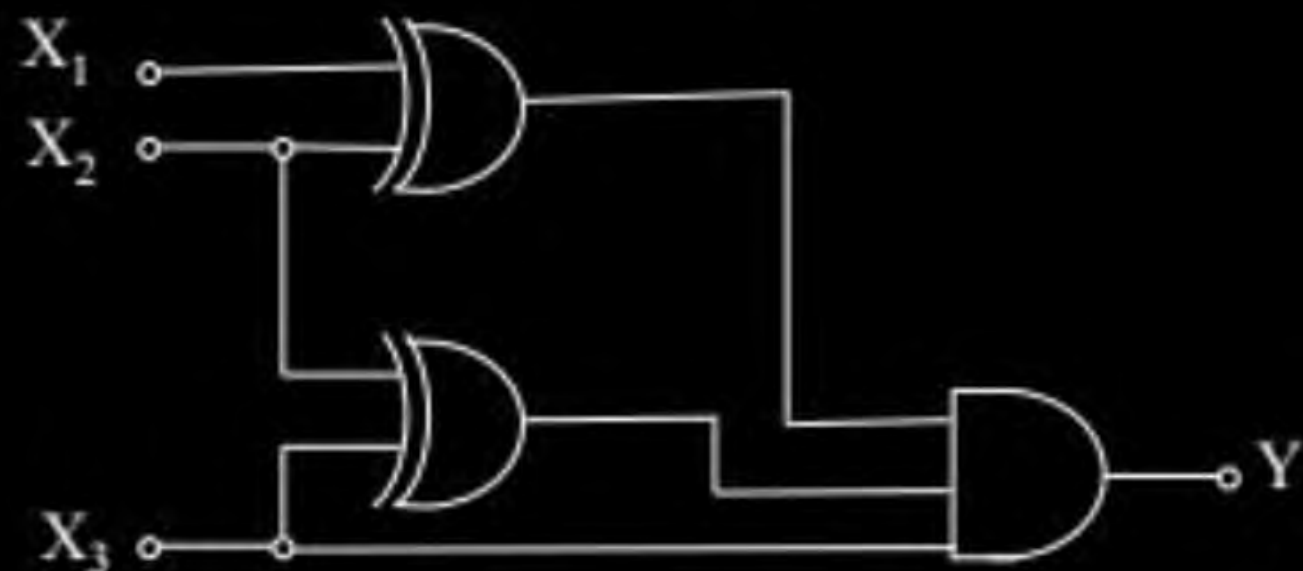

Common data for Questions Q.9 and Q.10

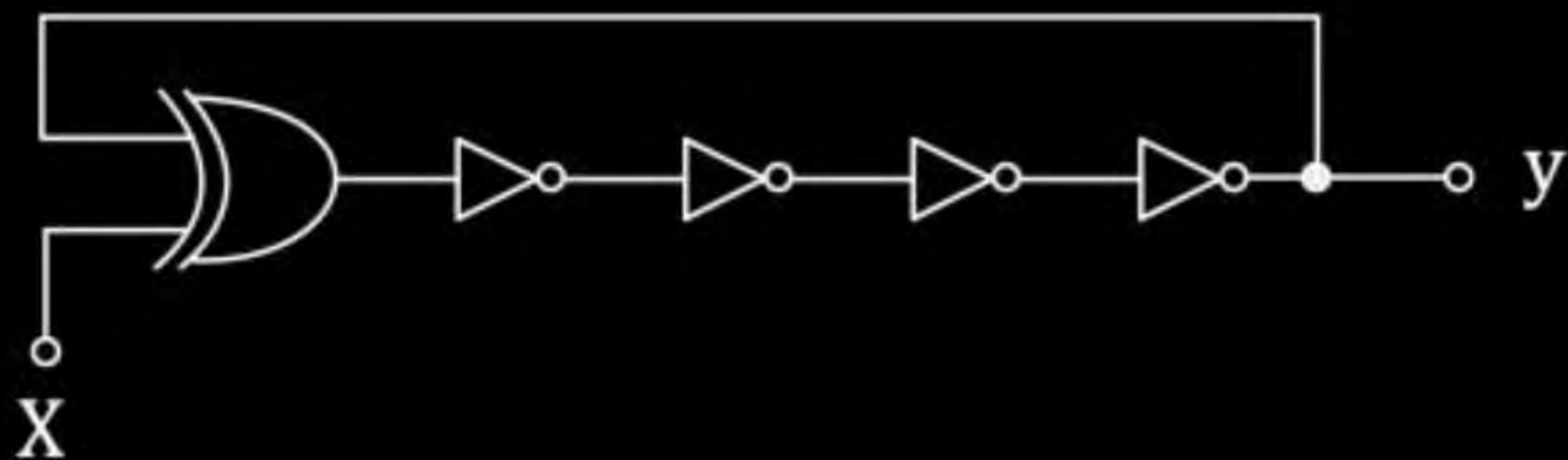All the logic gates in the circuit shown below, have equal finite propagation delay.



Q.9

The circuit can be used as clock generator, if

A $x = 0$

B $x = 1$

C $x = 0$ or 1

D $x = y$


Q.10

If the output waveform has frequency of 10 MHz, the propagation delay of each logic gate, is

- A** 5 ns
- B** 10 ns
- C** 20 ns
- D** 50 ns

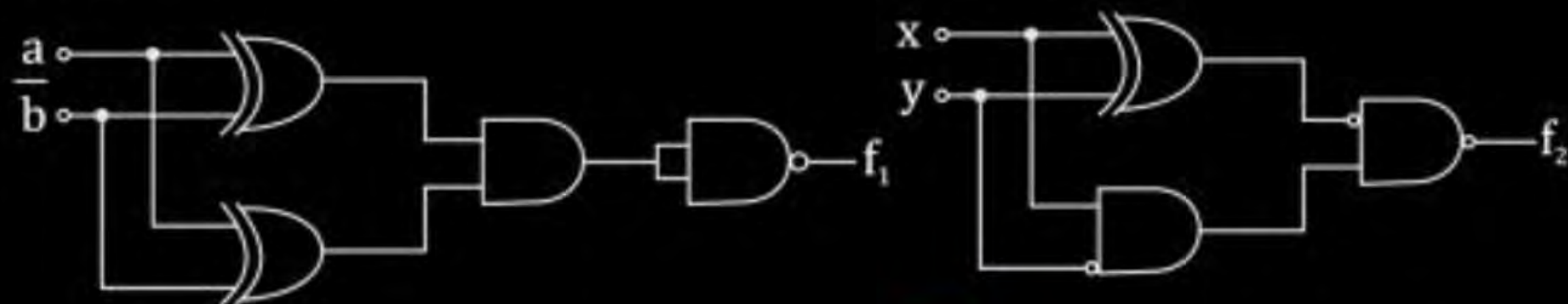Q.11

The Boolean expressions $f_1(a, b)$ and $f_2(x, y)$ in the following two circuits, are



A $f_1(a, b) = 0, f_2(x, y) = 1$

C $f_1(a, b) = a \oplus b, f_2(x, y) = 1$

B $f_1(a, b) = \overline{a \oplus b}, f_2(x, y) = x \oplus y$

D $f_1(a, b) = 1, f_2(x, y) = 0$

Thank you

GW
Soldiers !

