 


CS & IT ENGINEERING

Digital Logic

Logic Gate




Lecture No. 3



By- CHANDAN SIR



TOPICS TO BE COVERED




01 NAND GATE

02 NOR GATE


03 Discussion

Q.

Sketch the waveform of y?



 


$$f_x = \frac{1}{6\tau_{pd}}$$

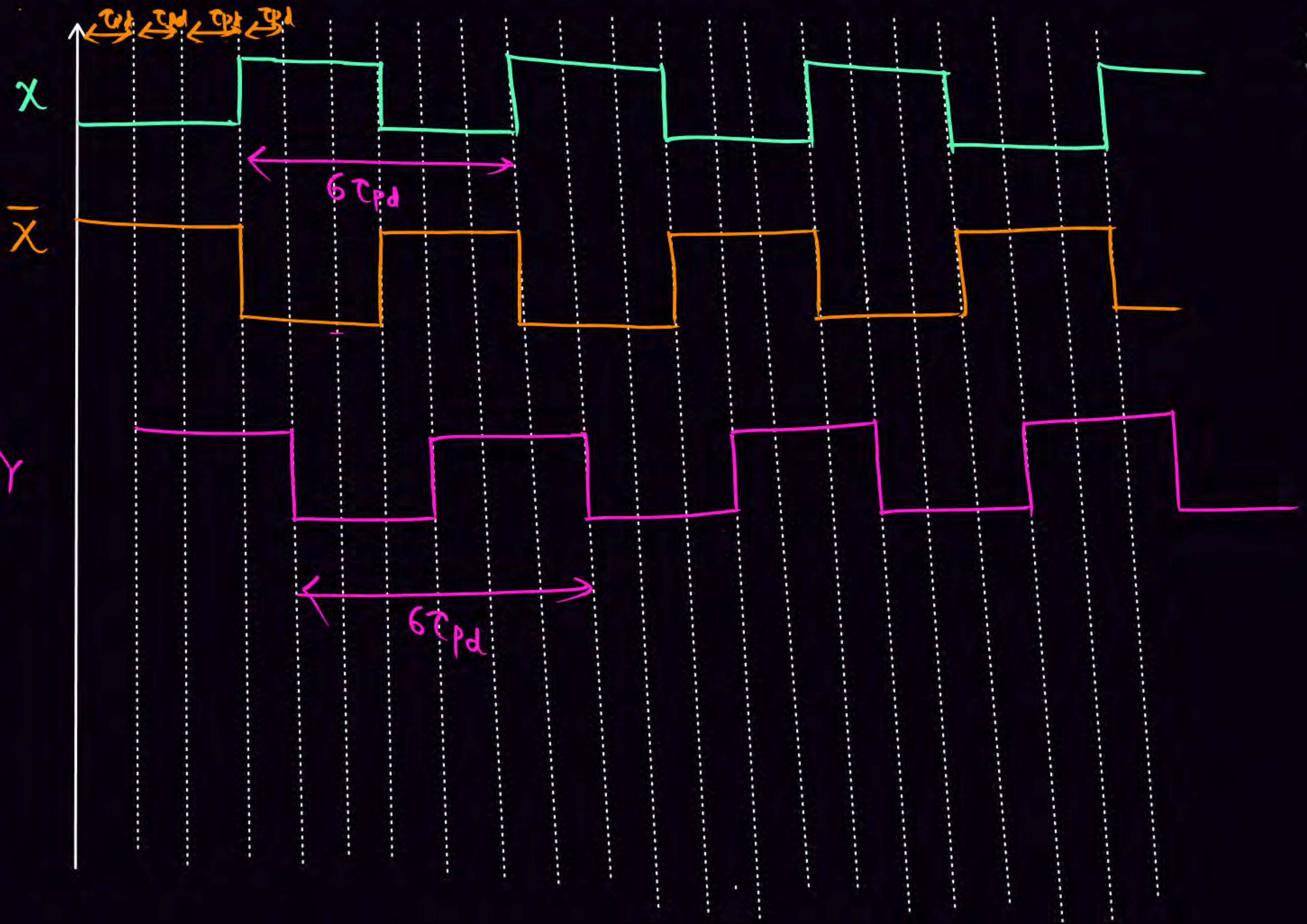

$$f_y = \frac{1}{6\tau_{pd}}$$


Q.

   

$$T = 2\tau_{pd}$$

$$f_x = \frac{1}{T} = \frac{1}{2\tau_{pd}}$$


\bar{X} after $1\tau_{pd}$ y

 


$$f = \frac{1}{2\tau_{pd}}$$

$$T = 2\tau_{pd}$$

 NOTE \Rightarrow always, for calculation of frequency consider no. of NOT GATE in Loop \rightarrow



f_1

 

f_2


$f_1 = f_2$

Q.

Toggle $\rightarrow 0 \rightarrow 1 \rightarrow 0 \rightarrow 1 \rightarrow \dots$

For the circuit given below x & y condition will be-



 
- A x stable y toggle
- B x toggle y stable
- C x & y both toggle
- D x & y both stable



Q.

HW

   
A logical circuit is as shown below, which of the following circuit can be used to get the desired expression.



Q.

HW

 The logic circuit shown below, is equivalent to



A



C



B



D






NAND, NOR GATE



■ NAND GATE

1. Symbol

   

Bubbled OR \equiv NAND


2. Truth Table

A	B	Y
0	0	1
0	1	1
1	0	1
1	1	0


NAND, NOR GATE

■ NAND GATE

3. Enable/Disable

 

CONTROL '0' DISABLE

 


CONTROL '1' ENABLE



NAND, NOR GATE

■ NAND GATE


4. Commutative Law ✓

 

  Associative Law ✗ $\overline{\overline{AB} + C}$
 $\overline{AB + C}$



 ✱ NAND, NOR follow the commutative Law But does not follow
 Associative Law




INPUT = 1


ON \rightarrow Saturation \rightarrow short ckt


INPUT = 0

 OFF \rightarrow CUTOFF \rightarrow Open ckt



A	B	T_1	T_2	y
0	0	Cutoff	Cutoff	1
0	1	Cutoff	Saturation	1
1	0	Saturation	Cutoff	1
1	1	Saturation	Saturation	0

 

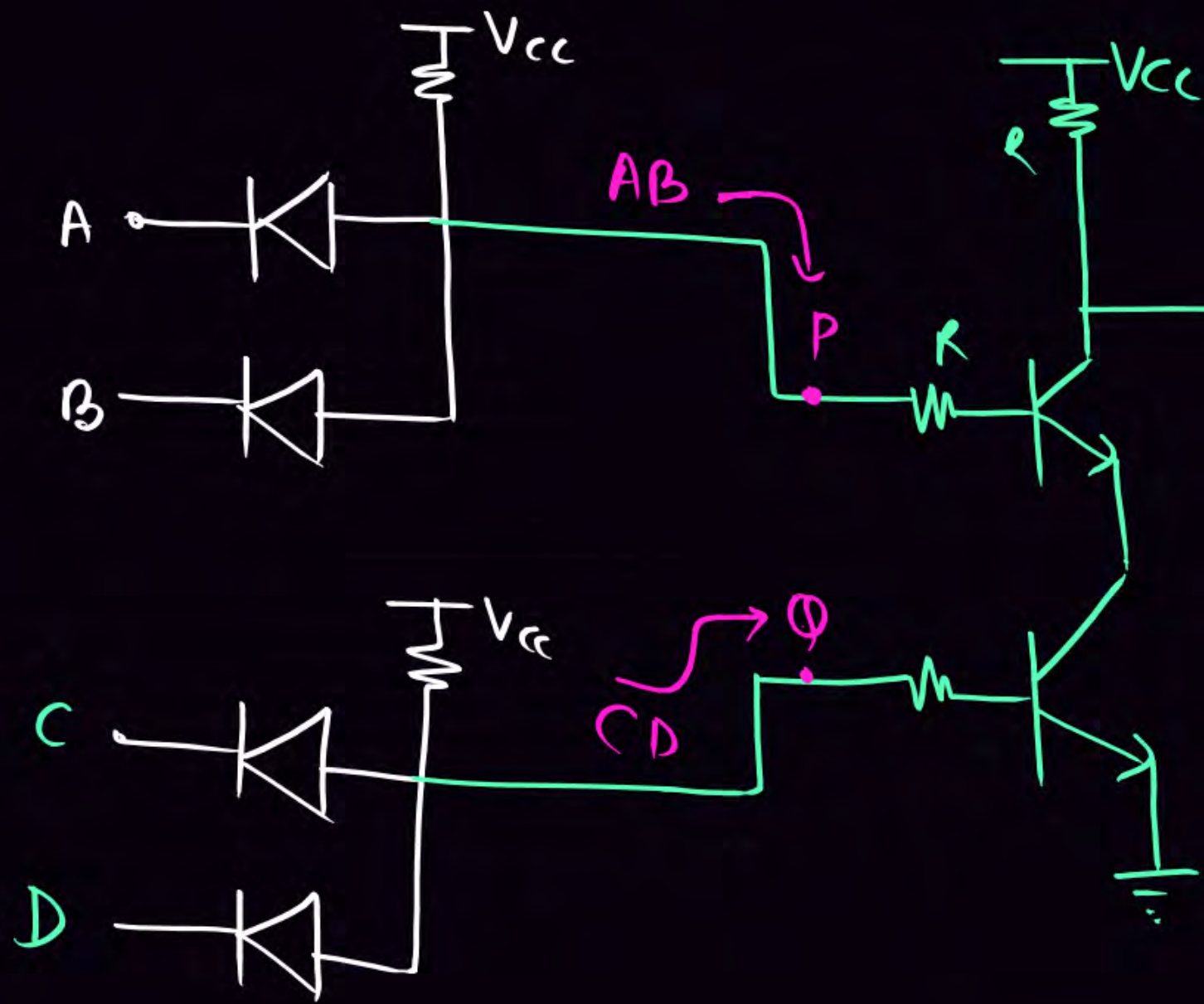

$$P = AB$$

$$Q = CD$$

$$y = \overline{P \cdot Q}$$



$$= \overline{ABCD}$$

Ans

., NAND, NOR GATE

■ NOR GATE

1. Symbol

  

Bubbled AND = NOR


2. Truth Table

A	B	Y = $\overline{A+B}$
0	0	1
0	1	0
1	0	0
1	1	0


NAND, NOR GATE

■ NOR GATE

3. Enable/Disable

 

CONTROL '0' ENABLE

 

CONTROL '1' DISABLE



NAND, NOR GATE


■ NOR GATE

4. Commutative Law ✓



Associative Law X

  


 


Rani



Raja

A	B	T ₁	T ₂	y
0	0	cutoff	cutoff	1
0	1	cutoff	saturation	0
1	0	saturation	cutoff	0
1	1	saturation	saturation	0

 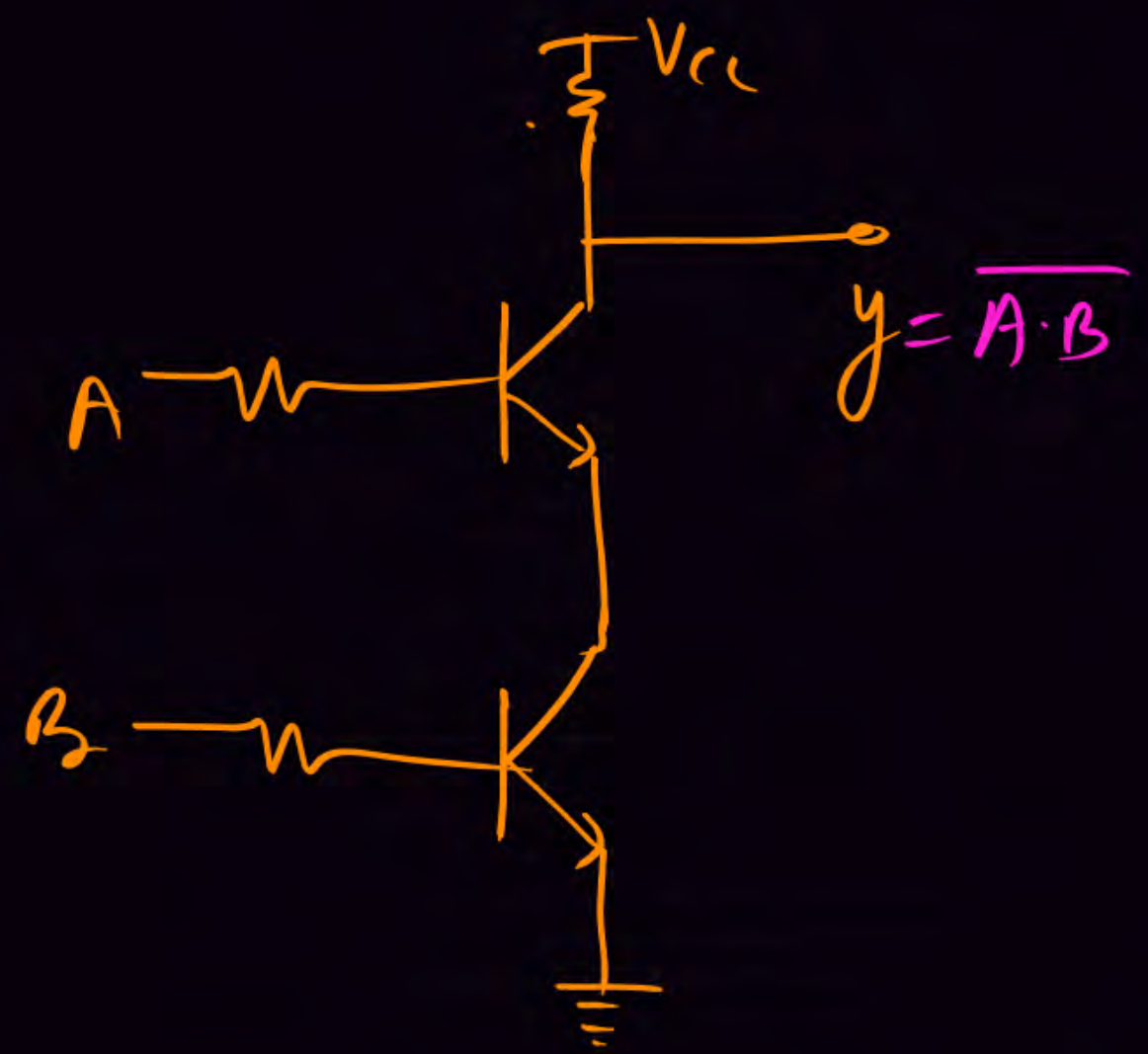

Ex 100

NOTE

$\therefore \rightarrow$ NAND, NOR are called universal Logic.

NAND, NOR GATE

▪ NAND AS UNIVERSAL LOGIC

- | | |
|-------------|--------------|
| 1. NOT GATE | 4. XOR GATE |
| 2. AND GATE | 5. XNOR GATE |
| 3. OR GATE | |

NAND, NOR GATE

- **Alternate Symbol**



Q.

MCQ



Which of the following option is called universal logic?

- ☐ A NAND
- ☐ B NOR
- ☒ C Both A & B
- ☐ D None

Q.

MCQ



Which of the following option is called universal logic?

☒ A NAND

☐ B NOR

☐ C AND

☐ D OR

Q.

MSQ



Which of the following option(s) is/are called universal logic?

☒ A $\overline{(A+B)}$

☒ B $\overline{(A \cdot B)}$

☒ C $(A + \bar{B})$

☒ D $A \cdot \bar{B}$


$\overline{A \cdot B} \rightarrow \text{NAND}$

$\overline{A+B} \rightarrow \text{NOR}$


Q.

NAT

 For the following circuit diagram minimum numbers two NAND gate required.



Thank you

 

Self confidence

GW
Soldiers !

