CS & IT



ENGINEERING



Sequential Circuit

Lecture No. 6



By- CHANDAN SIR



TOPICS TO BE COVERED 01 Registers, Basic of Counters

02 PRACTICE

03 DISCUSSION



Toggle mode of T Flip-Flop.


$$Q_{n+1} = J \oplus Q_n = \overline{Q}_n$$


$$\Rightarrow \{ q_{n+1} = \overline{q_n} \}$$

7 Toggle mode





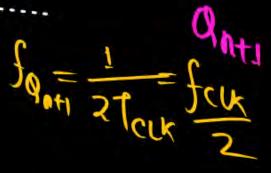

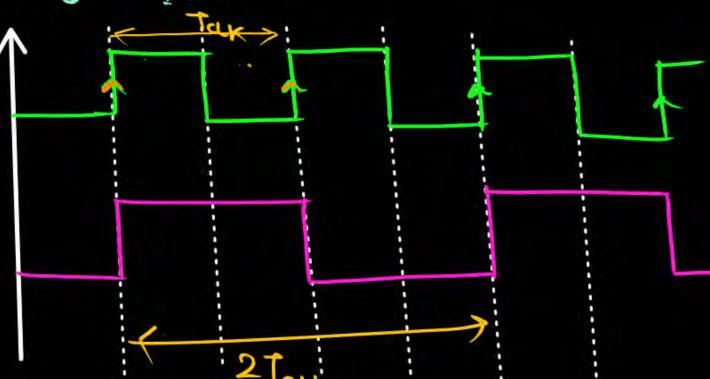

J=1 K=1




Toggle mode of J K Flip-Flop.



$$\delta^{\nu+\tau} = \underline{\delta}^{\nu}$$

Toggle mode of J K Flip-Flop.

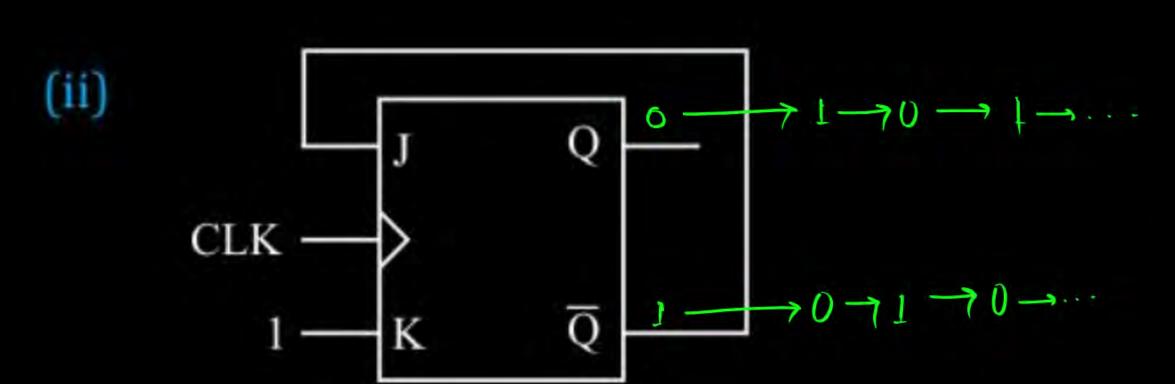




$$Q_{n+1}=\overline{Q_n}$$




K= an

J=1

Toggle mode of J K Flip-Flop.

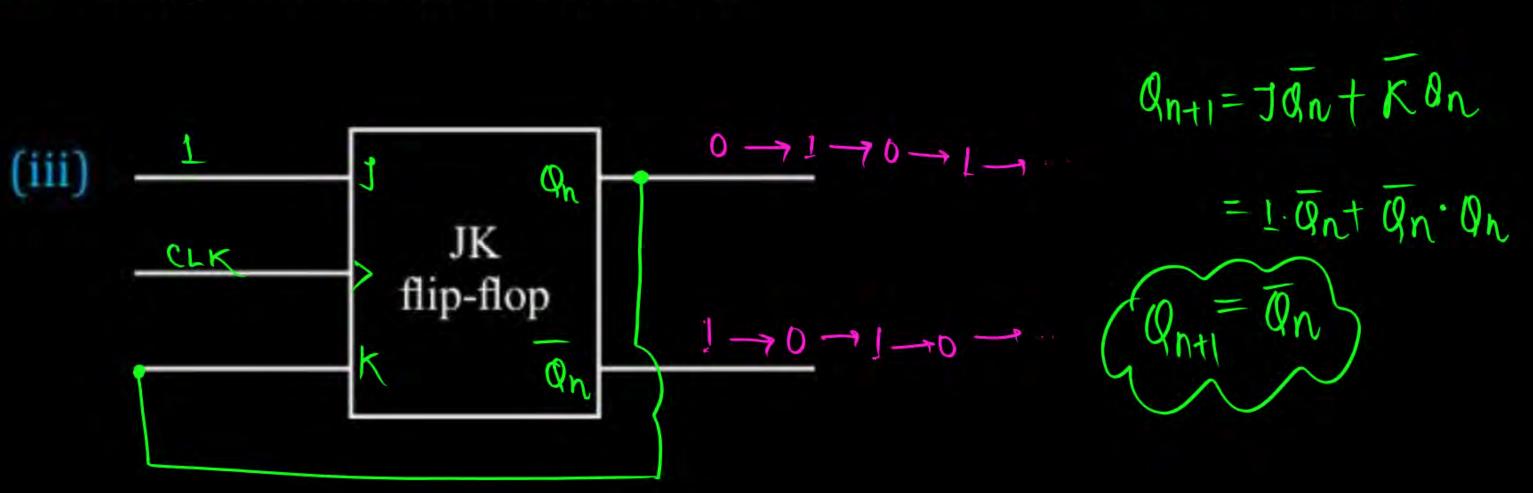

Toggle mode of J K Flip-Flop.

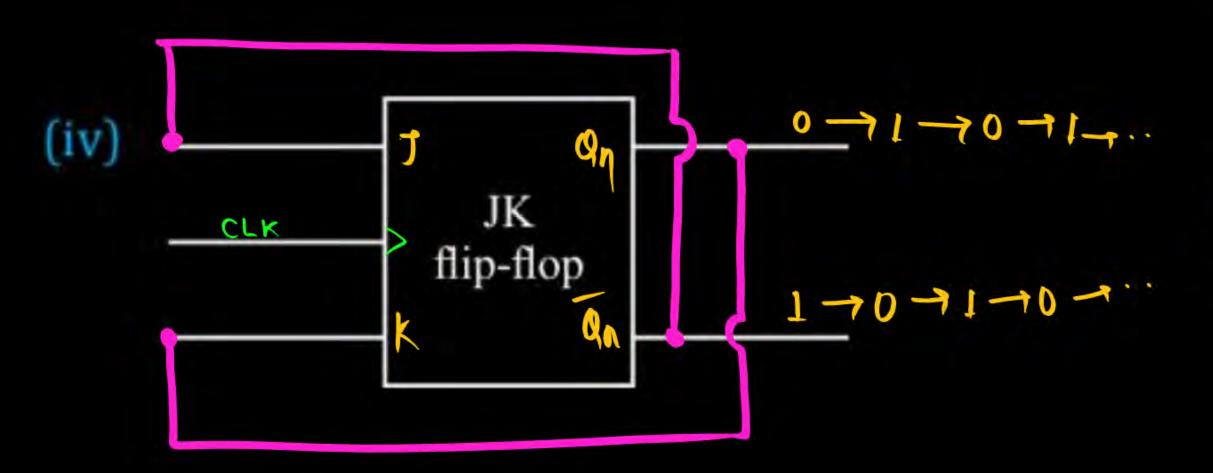


J=Qn K=Qn




5= an R=an



Toggle mode of S R Flip-Flop.

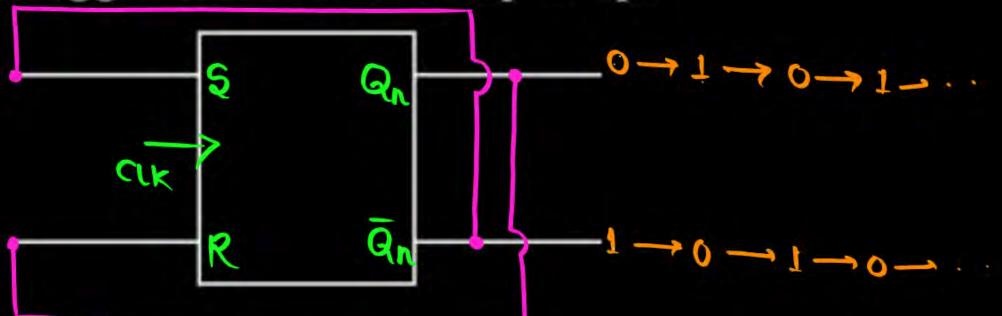

4. Toggle mode of Flip-Flop.

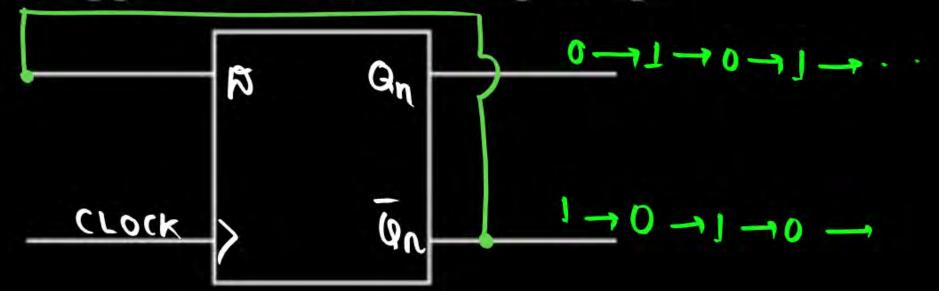



Azan

$$Q_{n+1} = R$$

$$Q_{n+1} = Q_n$$

COUNTER



- Counters are used to count Number of clock.
- Counter are used as Frequency Divider Circuit.
- 3 Counter are also used in ADC. Analog to Rigital converter.
- 4. Counters are also known as pulse stretcher circuit.
- 5. Counters also used in RADAR for detection of Range.

- Radio Wetection & Ronging

TYPES OF COUNTER


Pw

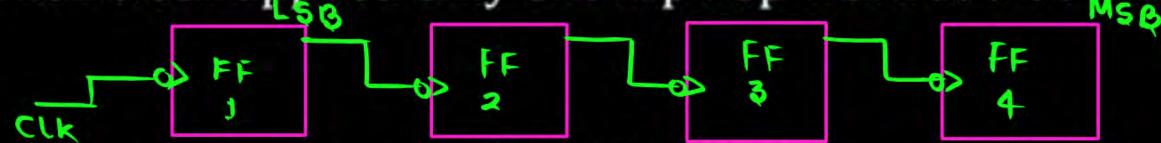- 1. Asynchronous Counter.
- Synchronous Counter.

TYPES OF COUNTER



 Asynchronous Counter: Only one flip flop having external clock and output of that flip flop will become clock for the next flip flop.
 So when clock applied only one flip flop work at that time.



2. Synchronous Counter: All Flip Flops are connected with the same clock. Hence when clock is applied all the flip flops work simultaneously.

COUNTER



Zynchronous counter

Asynchronous counter

- 1) All the FF's are connected with the same clock.
- 3 Faster
- 3) All type of counting are possible.
- 1 No Transition Error.
- (5) Ex. Ring counter Johnson counter

- 1) Only one FF having external clock and olp of that FF will be clock for the next FF.
- 3 Slower
- 3) Only increasing and decreasing counting are possible.
- (4) Yes, Transition error.
- 5) Ex. Ripple counter





Thank you

Soldiers!

