


Digital Logic Combinational Circuit

DPP-05

[MCQ]

☆☆☆

 
1. The circuit shown below, is a controlled half adder/ half subtractor. The inputs to half adder/ half subtractor are x and y while z is a control. The outputs are y_1 and y_2 .



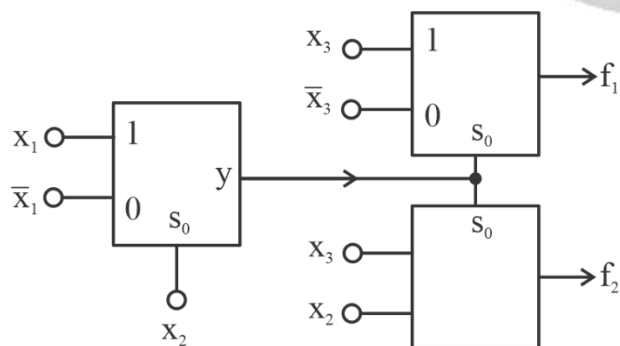- (a) Half adder for $z = 0$
 (b) Half subtractor for $z = 1$
 (c) Half adder for $z = 1$ and half subtractor for $z = 0$
 (d) Half adder regardless of whether $z = 0$ or $z = 1$ due to design defect.

Statement for question 2 & 3.

Three multiplexer of size 2×1 , are interconnected as shown below:



[MCQ]

☆☆☆

2. The function f_1 and f_2 are
- (a) $f_1 = (x_1 \oplus x_2)x_3$ and $f_2 = x_1\bar{x}_2 + x_1\bar{x}_3 + x_2x_3$
 (b) $f_1 = x_1 \oplus x_2 \oplus x_3$ and $f_2 = \bar{x}_1x_2 + \bar{x}_1x_3 + x_2x_3$
 (c) $f_1 = \overline{(x_1 \oplus x_2 \oplus x_3)}$ and $f_2 = x_1x_2 + x_1x_3 + x_2x_3$
 (d) $f_1 = x_1(x_2 \oplus x_3)$ and $f_2 = x_1x_2 + x_1x_3 + \bar{x}_2\bar{x}_3$

[MCQ]


☆☆☆

3. What is this circuit?
 (a) Full adder (b) Full subtractor
 (c) Magnitude comparator (d) Priority encoder

[MCQ]

☆☆☆

 4. The output of the following circuit diagram represents



- (a) Borrow of half subtractor
 (b) Carry of Half Adder
 (c) Sum of half adder
 (d) None of them

[MCQ]

☆☆☆

5. The design of a combinational logic circuit with three inputs x, y, z and three outputs A, B, C is attempted. The constraint is that designer has only HA, HS, FA and FS units only in his inventory.
- When the binary input is 0, 1, 2 or 3 the binary output is same as input and when binary input is 4, 5, 6 or 7 the binary output is 2 less than binary input. What completes the design?

- (a) One FA and one HS
 (b) One HA and one HS
 (c) One HA only
 (d) One FA only

[NAT]


☆☆☆

6. A serial adder is operating with a clock frequency of 10 MHz. The time required to sum 1011011 and 10110 is _____ (in μsec)

[MCQ]

☆☆☆

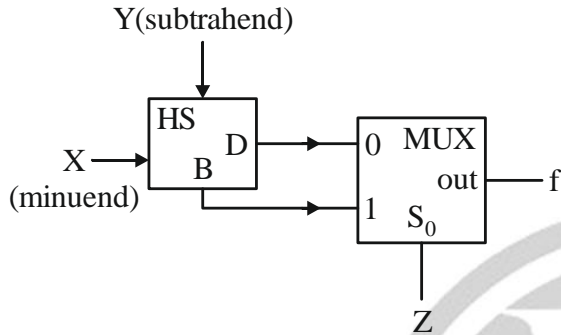7. A half subtractor (HS) and 2×1 MUX are interconnected as demonstrated below. What is NOT correct about this circuit?



- (a) For $Z = 0$, $f = 1$ indicates that the minuend and the subtrahend bits are different.
 (b) For $Z = 0$, $f = 0$ indicates that minuend and subtrahend bits are same, that is, $X = Y = 0$ or $X = Y = 1$.
 (c) For $Z = 1$, $f = 1$ indicates that $X < Y$.
 (d) For $Z = 1$, $f = 0$ indicates that subtrahend bit is definitely 0.

[MCQ]

☆☆☆

8. What does minuend and subtrahend denotes in a subtractor?

- (a) Their corresponding bits of input
 (b) Its output
 (c) Its input
 (d) Borrow bits

[MCQ]

☆☆☆

9. What is the expression for difference, borrow of full subtractor circuit

- (a) $\text{Diff} = A \oplus B \oplus C$,
 $\text{Borrow} = \bar{A}C + (A \odot B)C$
 (b) $\text{Diff} = A \oplus B \oplus C$,
 $\text{Borrow} = \bar{A}B + (\bar{A} \oplus B) \cdot C$
 (c) $\text{Diff} = A \odot B \odot C$,
 $\text{Borrow} = \bar{A}B + (\bar{A} \odot B)C$
 (d) $\text{Diff} = A \odot B \odot C$,
 $\text{Borrow} = \bar{A}C + (A \odot B)C$

[MCQ]

☆☆☆


10. A D flip-flop is used in a 4-bit serial adder, why?

- (a) It is used to invert the input of the full adder
 (b) It is used to store the output of the full adder
 (c) It is used to store the carry output of the full adder
 (d) It is used to store the sum output of the full adder

[MCQ]

☆☆☆

 11. The circuit shown in the given figure represents a/an:




- (a) decoder
 (b) equality detector
 (c) full adder
 (d) full subtractor

[MCQ]



 12. Consider the following circuit diagram



A 4-bit subtractor, four 4-bit three-state buffers (with bus input and output), and one inverter is used to subtract two numbers ($Y - X$), $X = 0101$ and $Y = 0010$. If $A = 0$, then D and B_{out} are respectively

- (a) 0011 and 0
 (b) 1101 and 0
 (c) 0011 and 1
 (d) 1101 and 1

Answer Key

1. (c)
2. (b)
3. (b)
4. (a)
5. (c)
6. (0.7)

7. (d)
8. (c)
9. (b)
10. (c)
11. (d)
12. (d)



Any issue with DPP, please report by clicking here:- <https://forms.gle/t2SzQVvQcs638c4r5>

For more questions, kindly visit the library section: Link for web: <https://smart.link/sdfez8ejd80if>



PW Mobile APP: <https://smart.link/7wwosivoicgd4>