

CS & IT

ENGINEERING

DIGITAL LOGIC

Combinational circuit



Lecture No. 1



By- CHANDAN SIR



TOPICS TO BE COVERED

Dual

01 Comparator

02 Question Practice


03 Discussion

$1 \rightarrow 10V$
 $0 \rightarrow 5V$ } +ve Logic

$1 \rightarrow 5V$
 $0 \rightarrow 0V$ } +ve Logic

$1 \rightarrow 0V$
 $0 \rightarrow -5V$ } +ve Logic

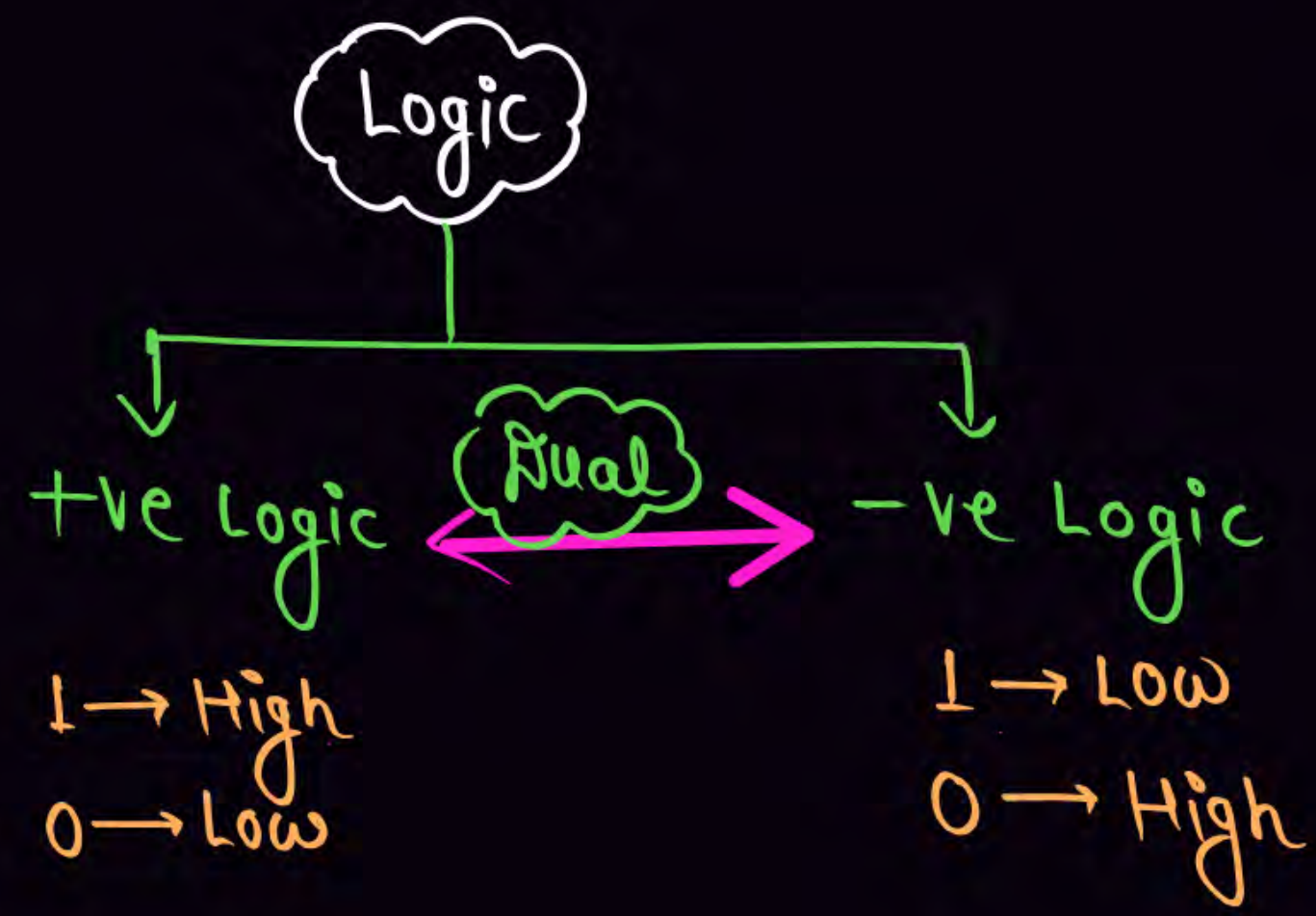$1 \rightarrow -5V$
 $0 \rightarrow -10V$ } +ve Logic



$1 \rightarrow 5V$
 $0 \rightarrow 10V$ } -ve Logic

$1 \rightarrow 0V$
 $0 \rightarrow 5V$ } -ve Logic

$1 \rightarrow -10V$
 $0 \rightarrow -5V$ } -ve Logic

AND GATE (+ve)

A	B	Y
0	0	0
0	1	0
1	0	0
1	1	1

A	B	Y
1	1	1
1	0	1
0	1	1
0	0	0



Dual \rightarrow +ve Logic $\xleftrightarrow{\text{Dual}}$ -ve Logic.

① 1 $\xleftrightarrow{\text{Dual}}$ 0

② AND $\xleftrightarrow{\text{Dual}}$ OR

③ \cdot $\xleftrightarrow{\text{Dual}}$ +

④ NAND $\xleftrightarrow{\text{Dual}}$ NOR

⑤ X-OR $\xleftrightarrow{\text{Dual}}$ X-NOR

⑥ Buffer $\xleftrightarrow{\text{Dual}}$ Buffer

⑦ INVERTER $\xleftrightarrow{\text{Dual}}$ INVERTER

$$0 \xleftrightarrow{\text{Dual}} 1$$

$$A \xleftrightarrow{\text{Dual}} A$$

$$\overline{A} \xleftrightarrow{\text{Dual}} \overline{A}$$

$$f = A \cdot 1$$

$$f^D = A + 0 = A$$

$$A \xleftrightarrow{\text{Dual}} A$$

Ex 1. $f = AB + CD + \bar{E}F$

t.me/cj51R

$$f^D = (A+B) \cdot (C+D) \cdot (\bar{E}+F)$$

Ex. 2. $f = \overline{ABC + D\bar{E}F}$

$$f^D = \overline{(A+B+C) \cdot (D+\bar{E}+F)}$$

$$f = \overline{A+B} \quad \text{NOR}$$

$$f^D = \overline{A \cdot B} \quad \text{NAND}$$

$$f^{D^D} = f$$

Ex

$$f = AB + CD$$

$$f^D = (A+B) \cdot (C+D)$$

$$f^{D^D} = AB + CD$$

← = ←

$$f = A$$

$$f^D = A$$

$$f^D = f$$

Self Dual

$n=1$

$$\left\{ \begin{array}{c} A \\ \bar{A} \\ 0 \\ 1 \end{array} \right\}$$


Self Dual = 2

$n=2$

$\bar{A}\bar{B}$	$\bar{A}+\bar{B}$	A	0
$\bar{A}B$	$\bar{A}+B$	\bar{A}	1
$A\bar{B}$	$A+\bar{B}$	B	$\bar{A}B + A\bar{B}$
AB	$A+B$	\bar{B}	$\bar{A}\bar{B} + AB$

Self Dual = 4

Ex 0.25

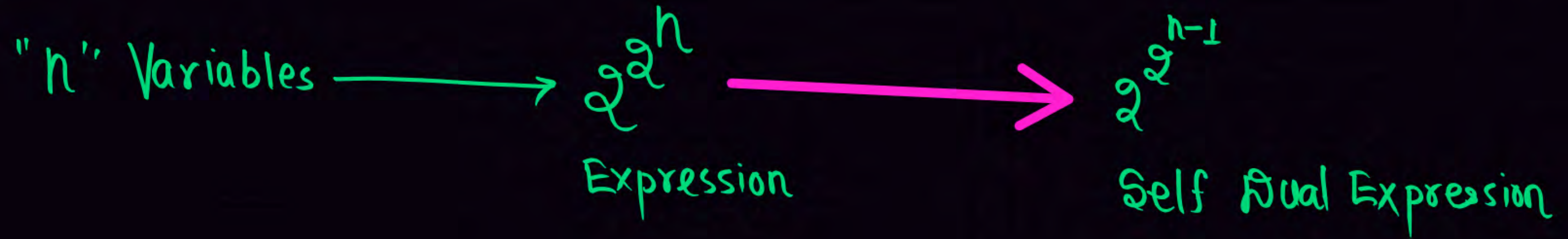

COMBINATIONAL CIRCUIT

↳ A circuit without feedback or memory are called Combinational circuit.

↳ Static circuit


DESIGNING OF COMBINATIONAL CIRCUIT

- Step 1. Find the number of inputs and outputs.
- Step 2. Write the truth table.
- Step 3. Write the logical expression.
- Step 4. Minimize the logical expression.
- Step 5. Hardware implementation.

Magnitude COMPARATOR



1. Design a one-bit comparator

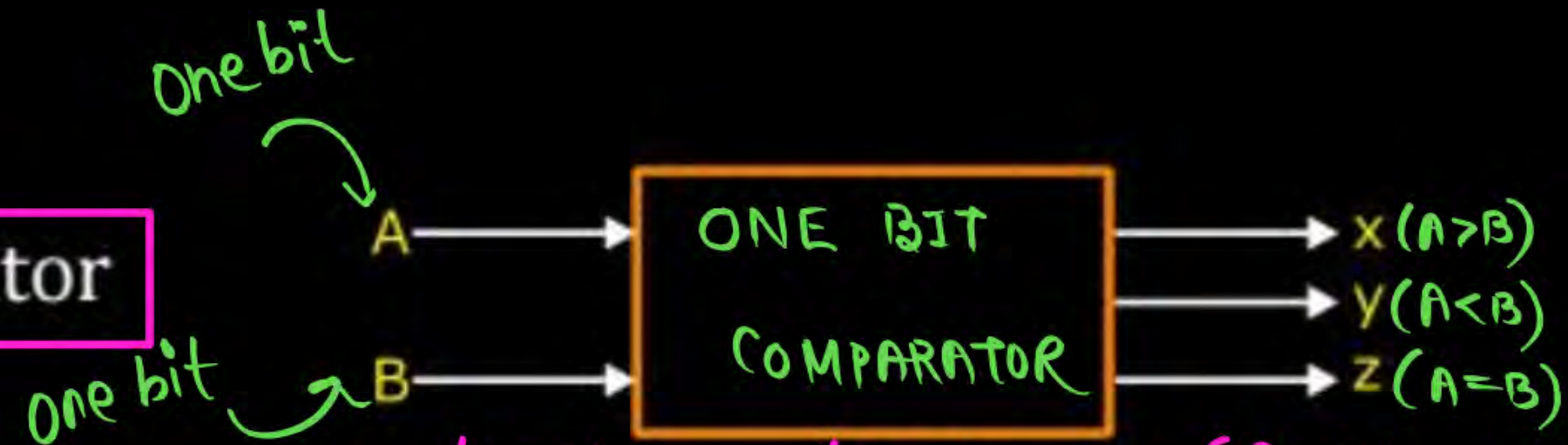

Step 1.

Step 2. Truth Table

A	B	X ($A > B$)	Y ($A < B$)	Z ($A = B$)
0	0	0	0	1
0	1	0	1	0
1	0	1	0	0
1	1	0	0	1

COMPARATOR

DESIGNING OF COMBINATIONAL CIRCUIT

Step 3. Logical expression


$$X(A > B) = A\bar{B}$$

$$Y(A < B) = \bar{A}B$$


$$Z(A = B) = \bar{A}\bar{B} + AB = A \odot B$$

Step 4. Minimization \rightarrow Already minimize.

Step 5. Hardware implementation

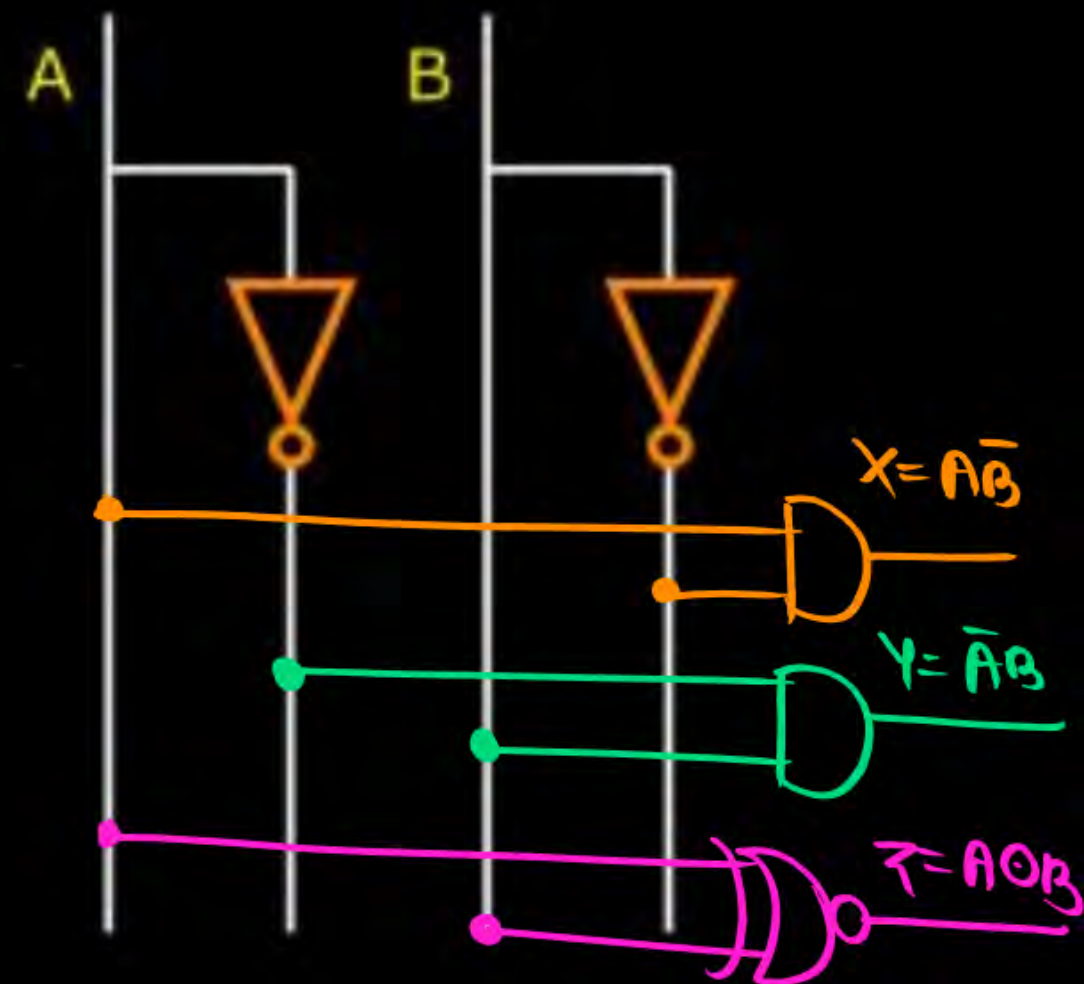


Step 5.

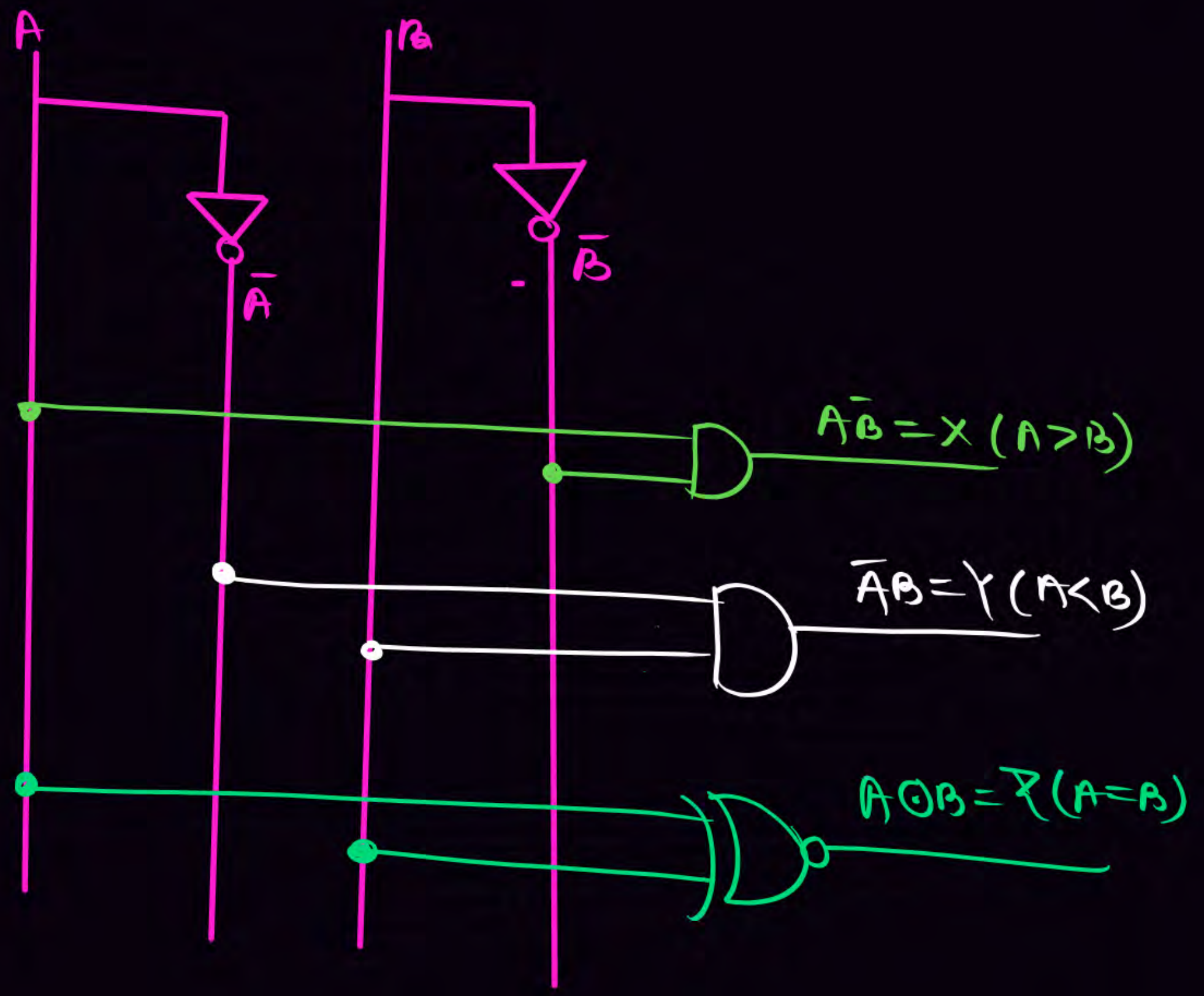

TWO BIT COMPARATOR



Decimal	Binary
0	0000
1	0001
2	0010
3	0011
4	0100
5	0101
6	0110
7	0111
8	1000
9	1001
10	1010
11	1011
12	1100
13	1101
14	1110
15	1111

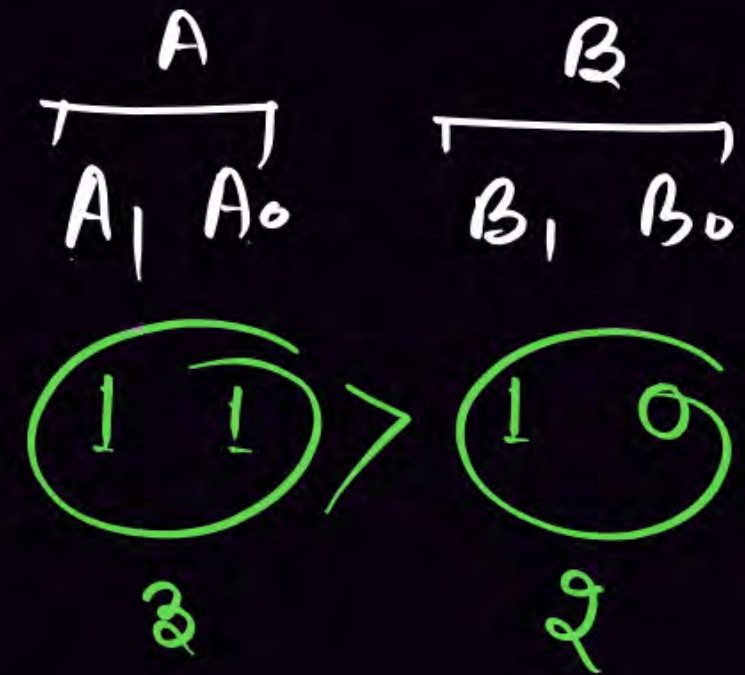

COMPARATOR

2. Design a two-Bit comparator?

Step 1.



Step 2. Truth table

	A		B		$A > B$	$A < B$	$(A=B)$
	A_1	A_0	B_1	B_0	x	y	z
0 →	0	0	0	0			
1 →	0	0	0	1			
2 →	0	0	1	0			
3 →	0	0	1	1			
4 →	0	1	0	0			
5 →	0	1	0	1			
6 →	0	1	1	0			
7 →	0	1	1	1			
8 →	1	0	0	0			
9 →	1	0	0	1			
10 →	1	0	1	0			
11 →	1	0	1	1			
12 →	1	1	0	0			
13 →	1	1	0	1			
14 →	1	1	1	0			
15 →	1	1	1	1			

COMPARATOR

DESIGNING OF COMBINATIONAL CIRCUIT

Step 3. Logical expression

$$X(A > B) = \sum m($$

$$Y(A < B) = \sum m($$

$$Z(A = B) = \sum m($$

COMPARATOR

DESIGNING OF COMBINATIONAL CIRCUIT

Step 4. Minimization

For X

$A_1A_0 \backslash B_1B_0$	00	01	11	10
00				
01				
11				
10				

For Y

$A_1A_0 \backslash B_1B_0$	00	01	11	10
00				
01				
11				
10				

COMPARATOR

DESIGNING OF COMBINATIONAL CIRCUIT

Step 4. Minimization

For Z

$A_1A_0 \backslash B_1B_0$	00	01	11	10
00				
01				
11				
10				

Thank you

GW
Soldiers!

