CS & IT



ENGINEERING





Lecture No.



By- CHANDAN SIR



TOPICS TO BE COVERED 01 ASYNCHRONOUS COUNTER


02 PRACTICE

03 DISCUSSION


Pw

MOD-5UP O_C AP QB 10 Qc Clr CLK dr= Q, QBQn AND Logic

Pw

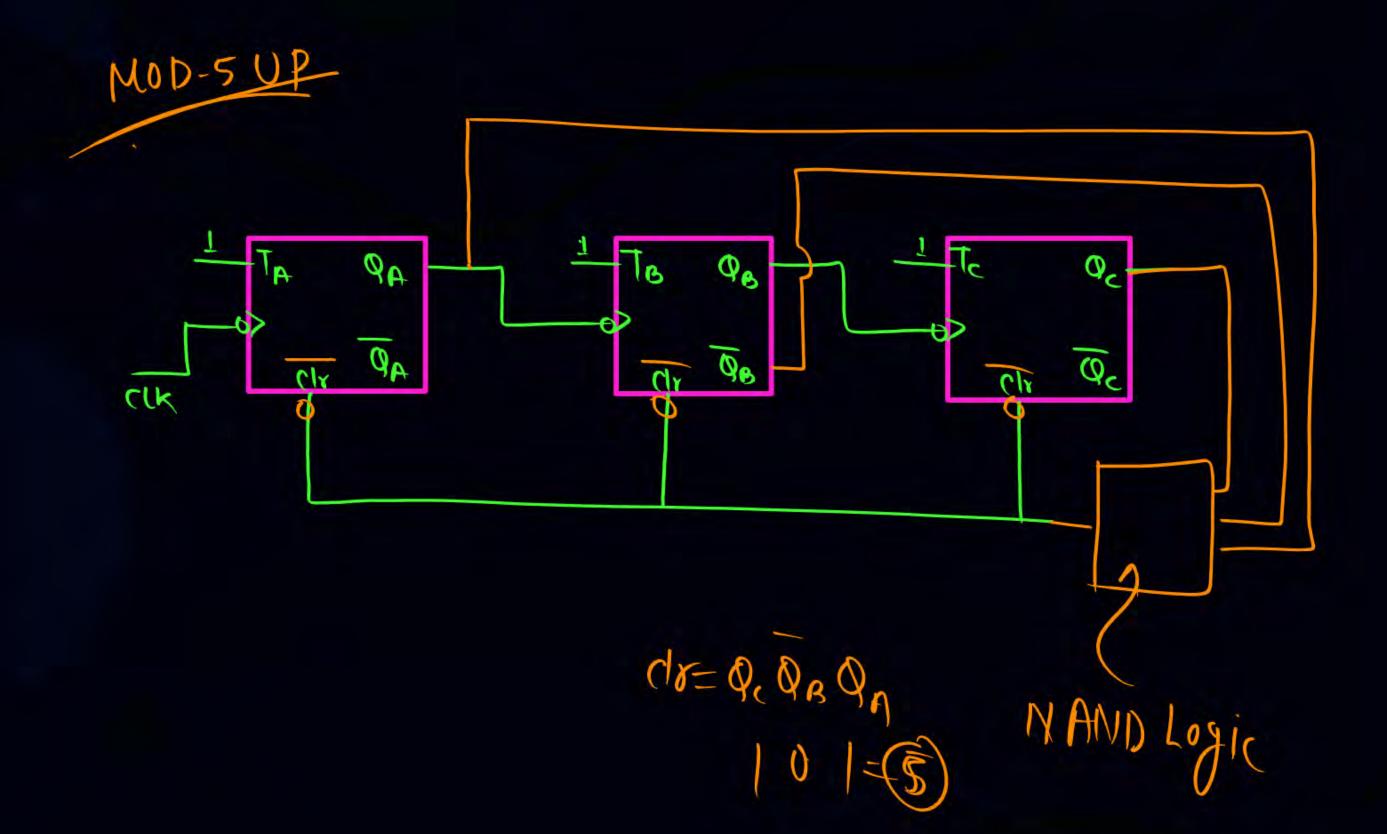


PW

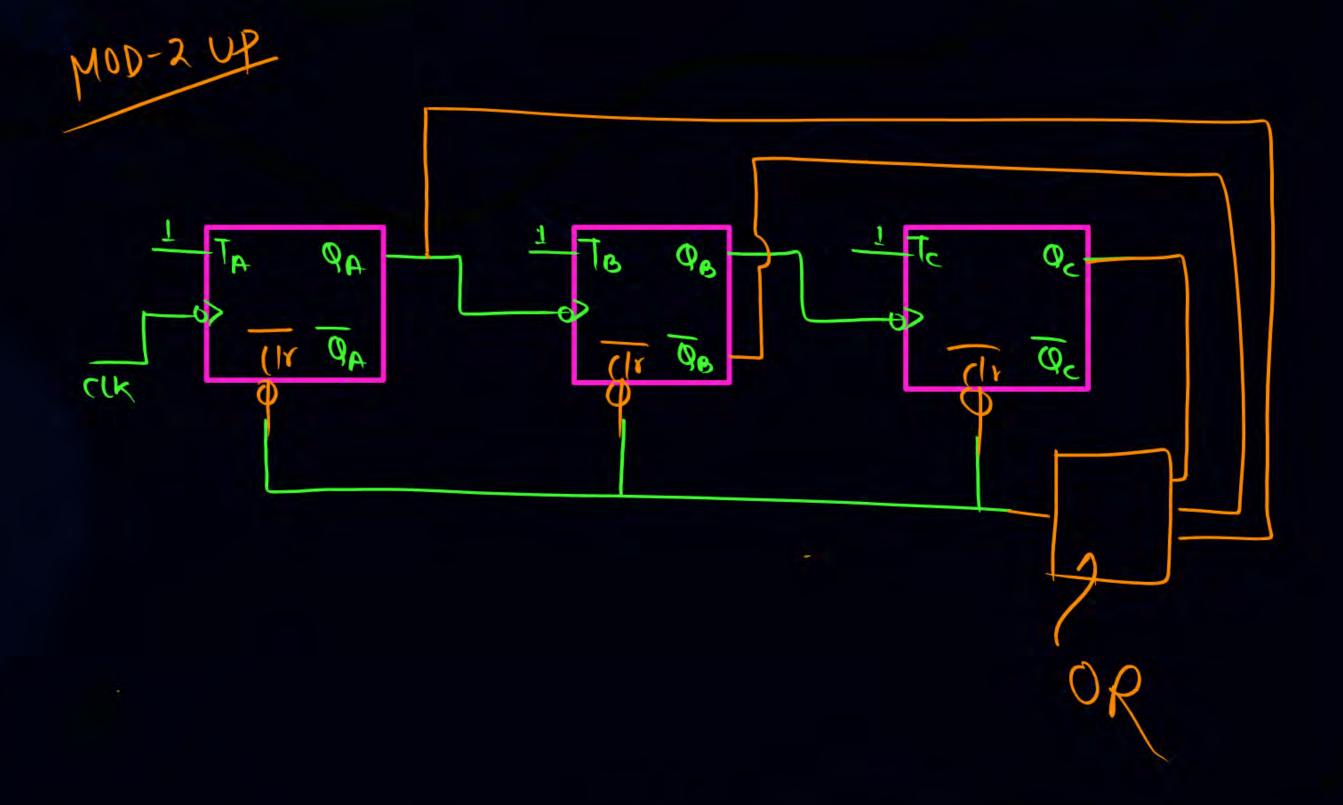

MOD 3) DOWN REPPLE COUNTER




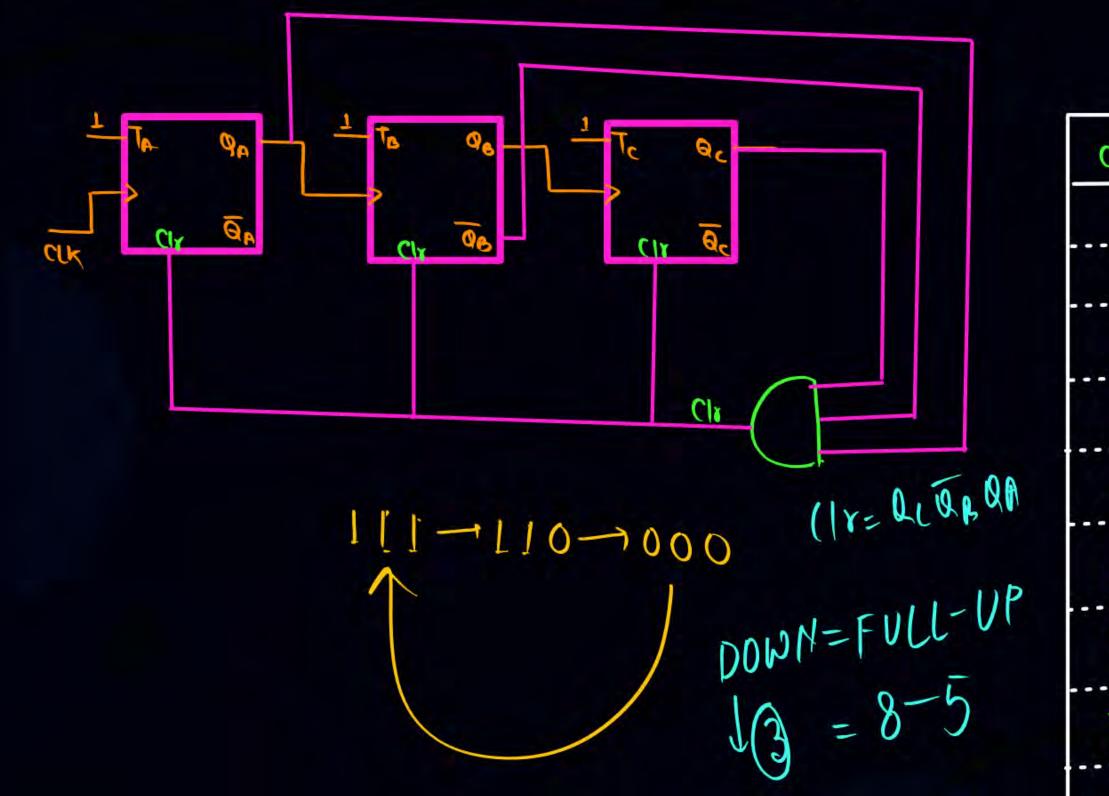

CLOCK	Q	QQ	Q _A	Clr=Q.Qo	31
0		0		0	
Ţ	T	1	1	0	
2	1	L	0	٥.	
3	30	100	No	20	
4	1	L	l	D	
5,	L	T.	0	0	
6	X	Nº 0	70	M	
7					
8					


MOD-4 DOWN. RIPPLE COUNTER



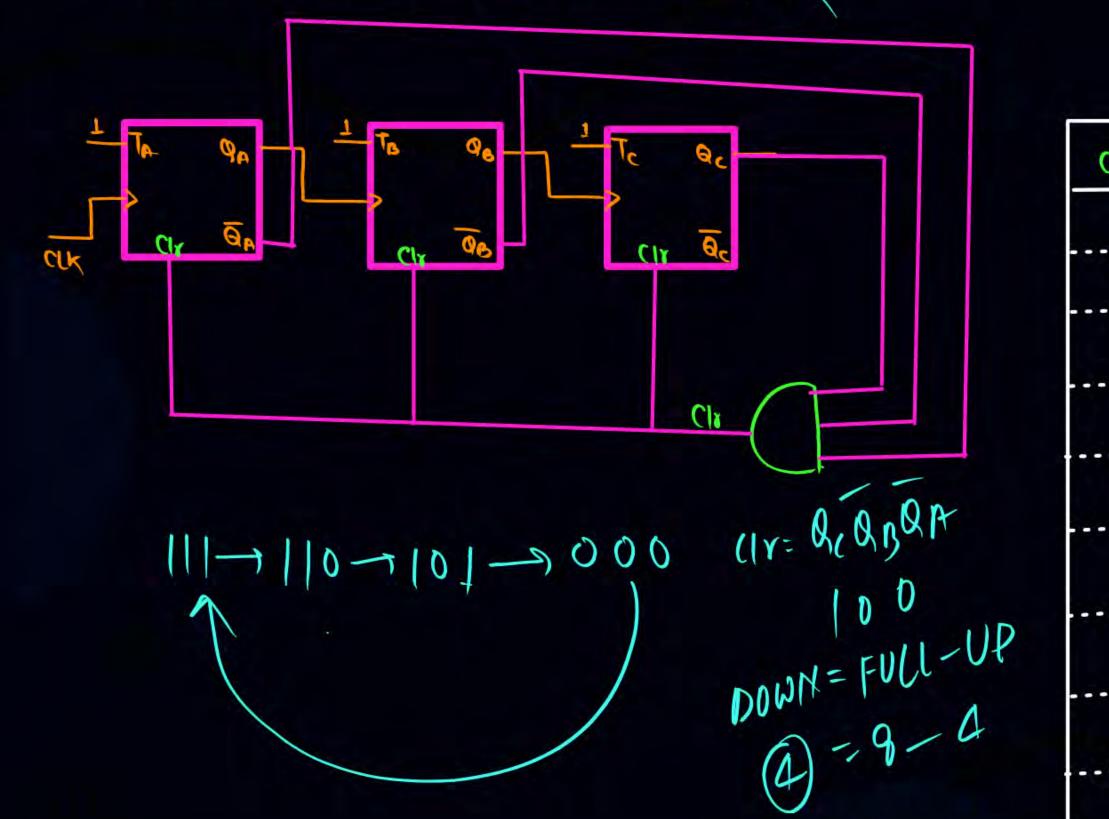

CLOCK	Q	Qe	Q _A	Clr= Qcan	9A
0	0	0	D	0	
1	1	1	1	0	
2	1	l,	0.	0	
3	1	0	1	0	
4	9	8	N°	X	
5					
6					
7					

MOD-5 DOWN RIPPLE COUNTER

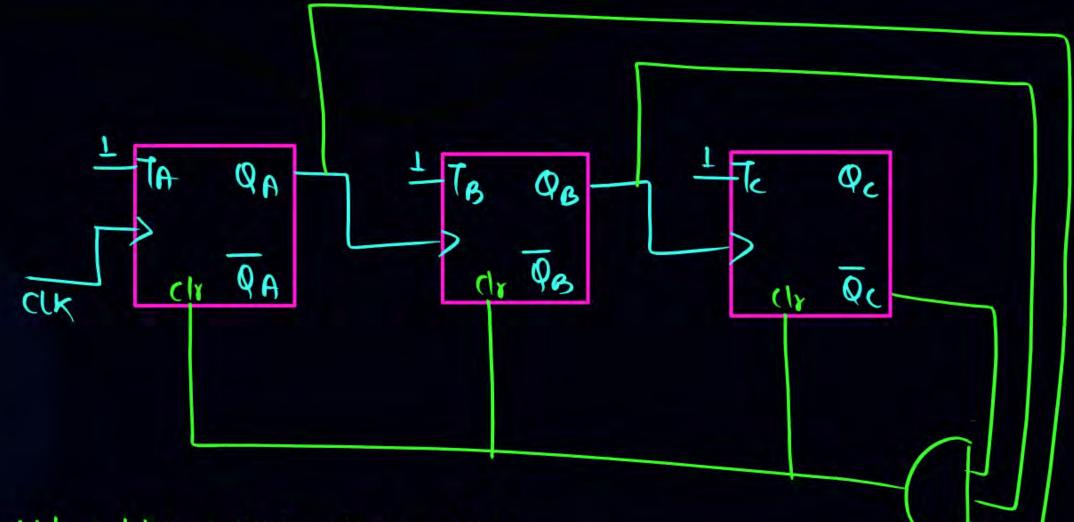

111-110-	00000000
1	


DOWN=FULL-UP

	1	= 9-9
1	(5)	= 4
	()	

	CIR	Qc QB QA	(14
	0	000	0
	1	111	0
	2.	(0	0
	3	101	0
	4	100	0
	ý	200	1
Clr- Quasha	, 7		




Q Besign a MOD-13 Rown Ripple counter?

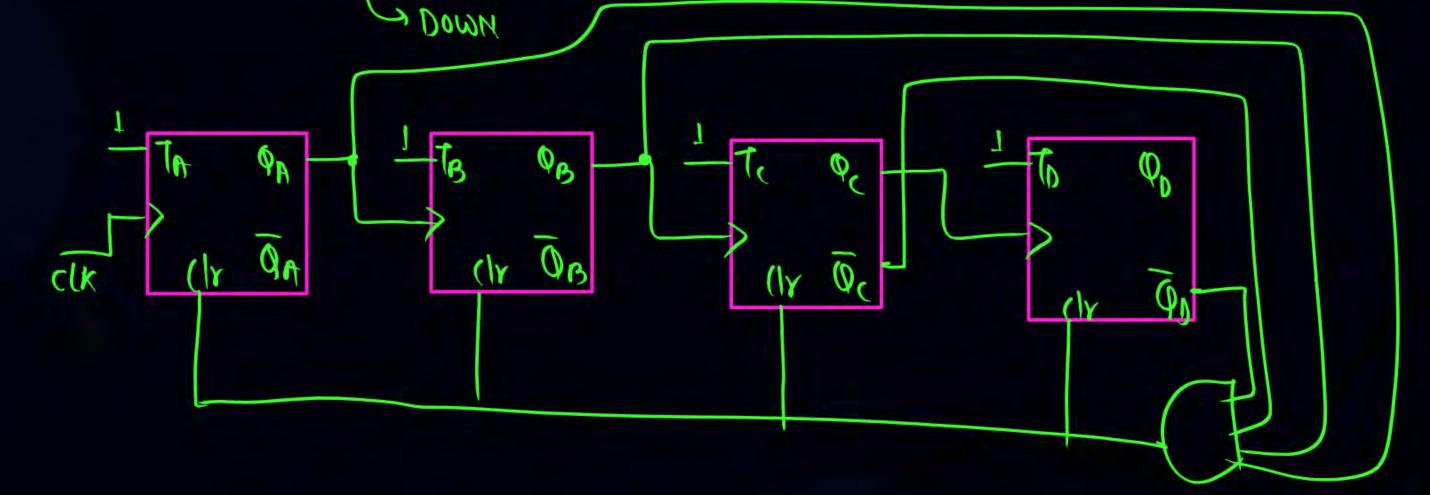


Q pesign a Mod-9 Down Ripple counter?




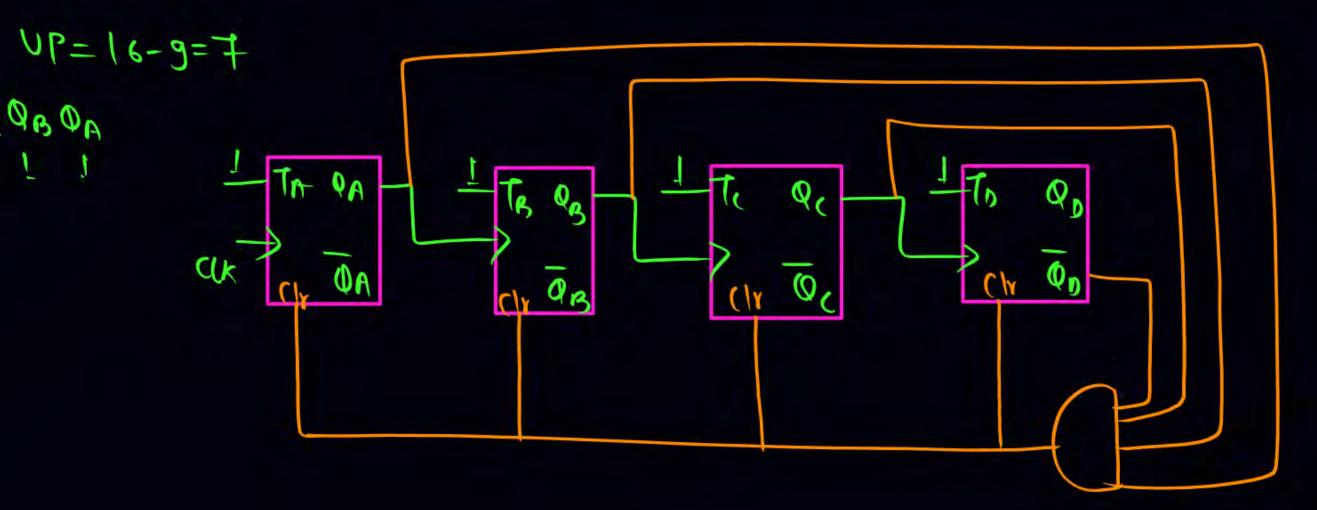



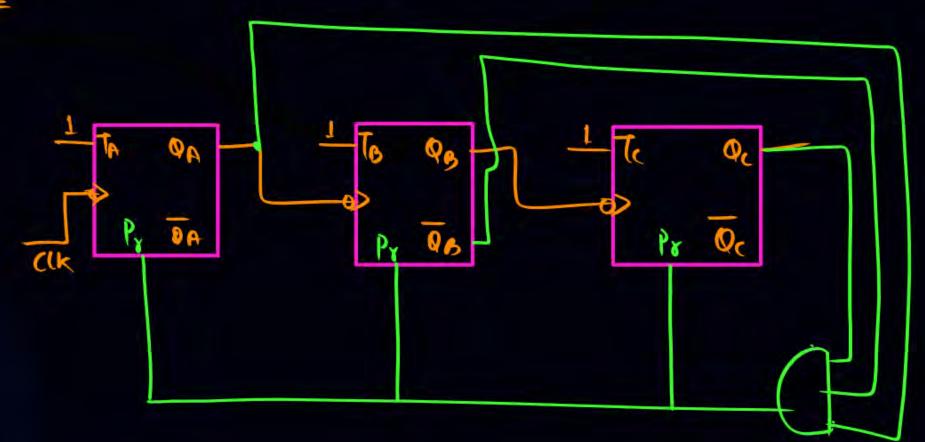- a Beign a MoD-19 Down Ripple counter?
- a Resign a Mad-23 Down Ripple counter?
- 9 Design a MoD-11 Rown Ripple counter.



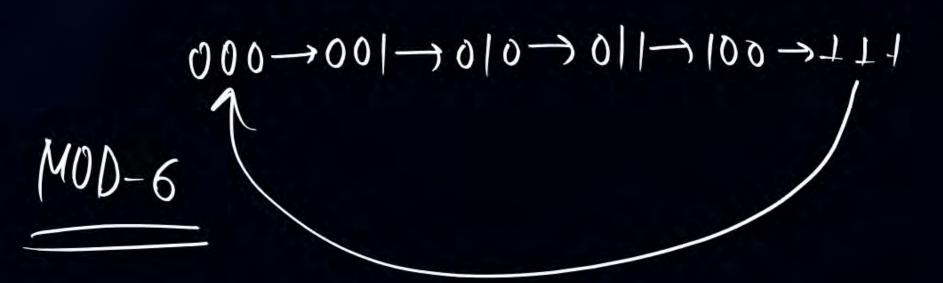




CLK		QB		Pr= QcQ	QA
0	0	D	0	0	
1	0	0	1	0	
2	0	1	0	0	
3	0	1	1	0	
4	ı		Ò	0	E
5	1	D	À	X10	
6	0		0	0	
7	0	0	1	0	



CLK P.	QA DA	To QB	Te Oc
MOD-2	000	111-) 110	

CLK	Q _L	Q _B	99	Pr=uc	RBUA
0	0	0	O	0	
1	1	L	1	0	
2	1	1	0	0	
3	N	N	1	NO	
4	1	1	0	0	
5	X	&	1	KO	
6	1	1	0	0	
7		A	-11	1	
		l		0	



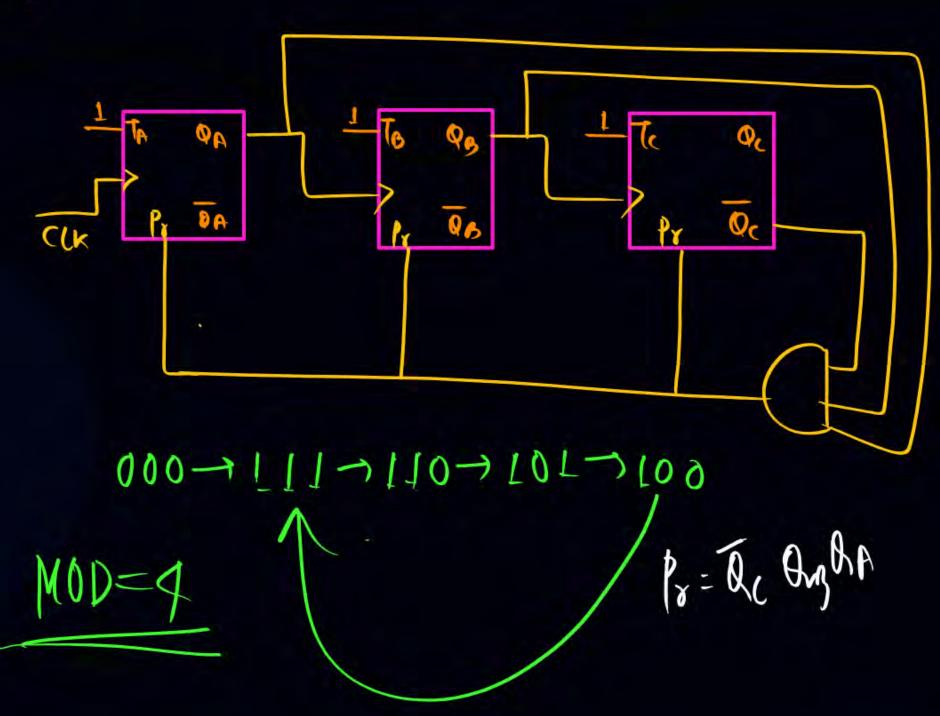

CLK	Qc	QB	Qa	Pr
0	0	D	0	0
L	1	t	t	0
2	1	1	0	0
3	1	0	1	0
4	1	0	0	0
5	D	か	M	N.
6	1	1	0	0
7	1	0	0	0



Thank you

Seldiers!

