

CS & IT ENGINEERING

DIGITAL LOGIC



Sequential Circuit
Lecture No. 08



By- CHANDAN SIR



TOPICS TO BE COVERED

01 ASYNCHRONOUS COUNTER


02 PRACTICE

03 DISCUSSION

+ve \rightarrow down
-ve \rightarrow UP

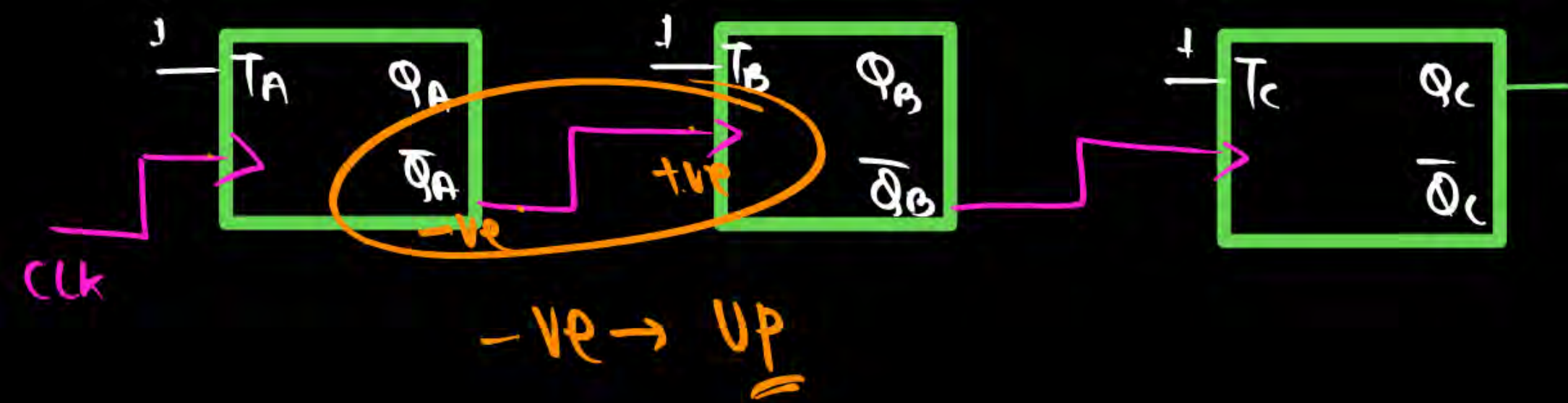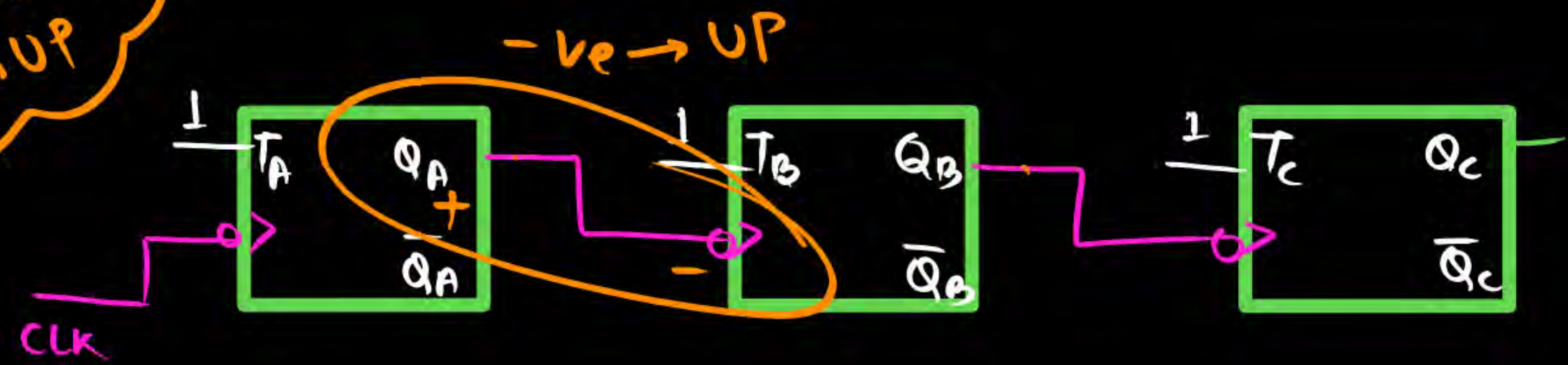

UP
COUNTER

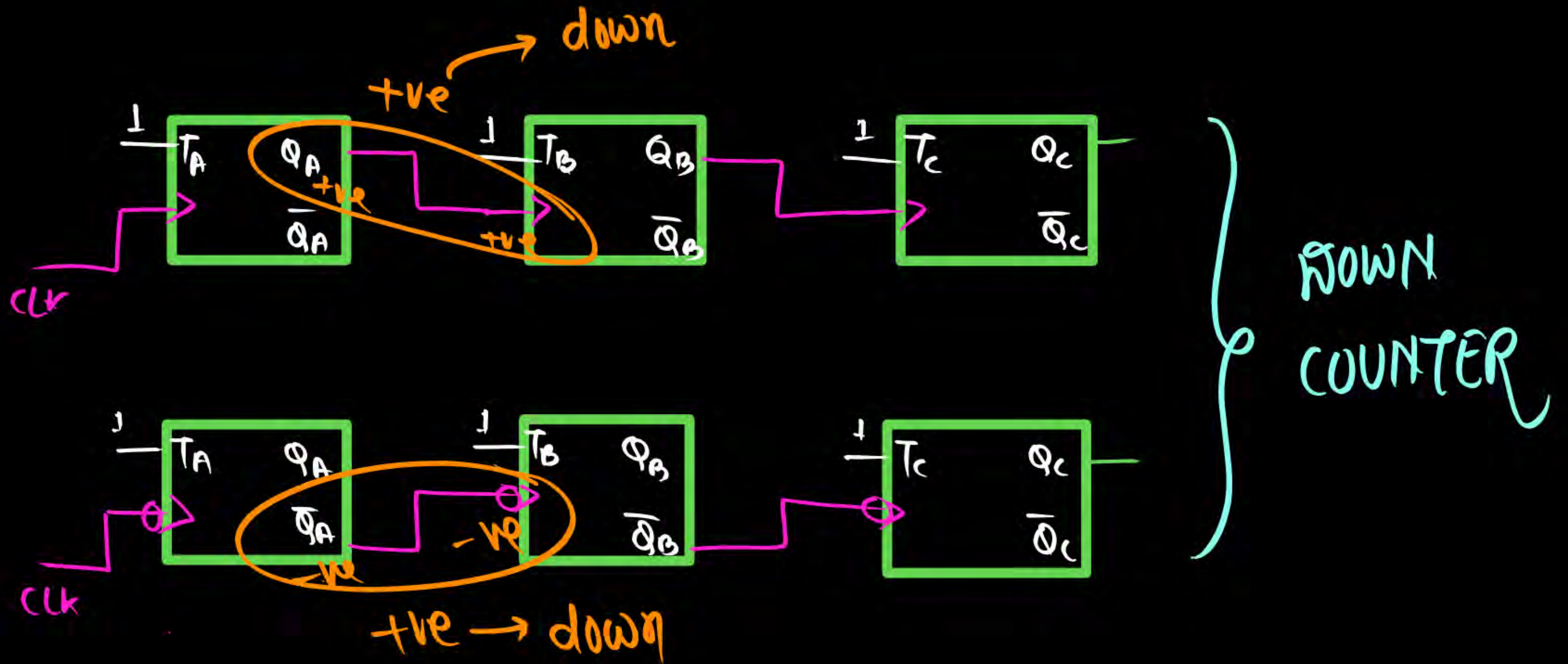

Full Mode counter \Rightarrow when all the states are used by the counter.

$$n=3$$

$$\text{MOD} = 8$$


$$n=4$$

$$\text{MOD} = 16$$

$$n=5$$



$$\text{MOD} = 32$$

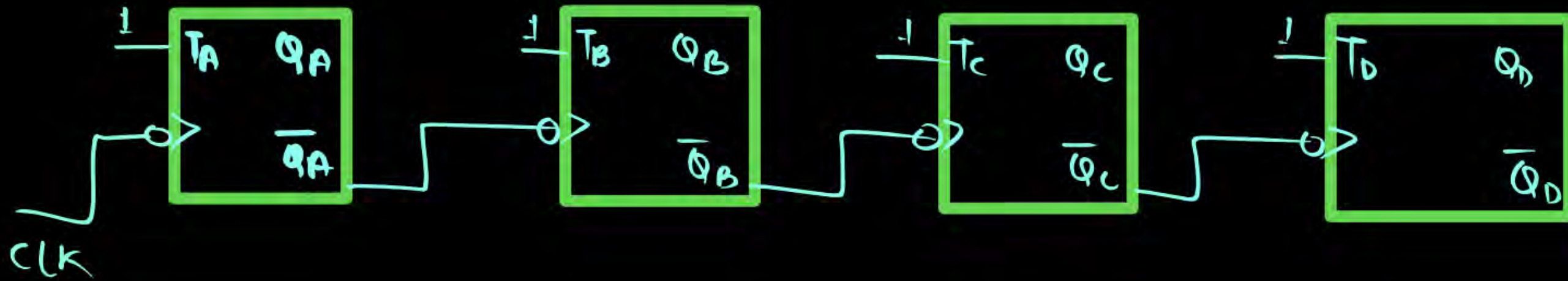Q Design a Mod 16 down counter in which \overline{Q}_3 is taken as clock?





⇒ Feedback Reduces the number of States.

RESET clear

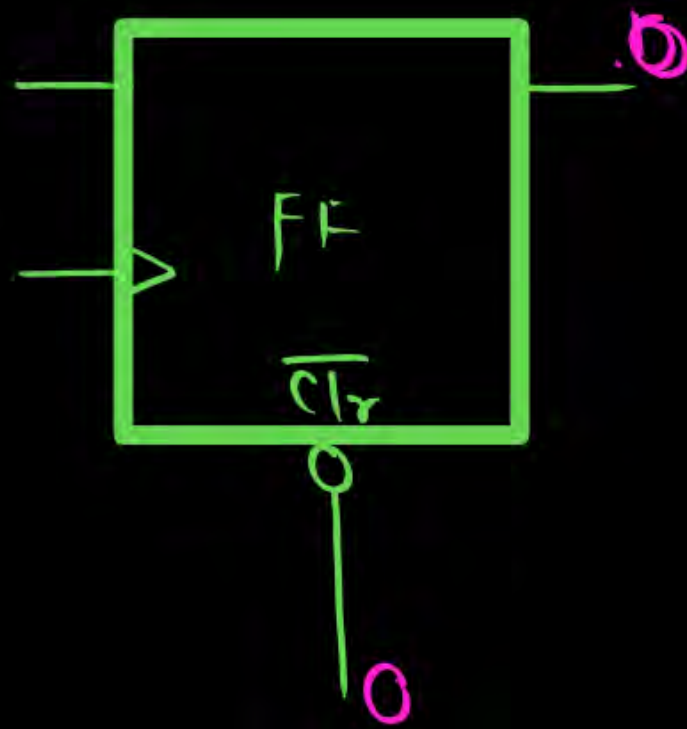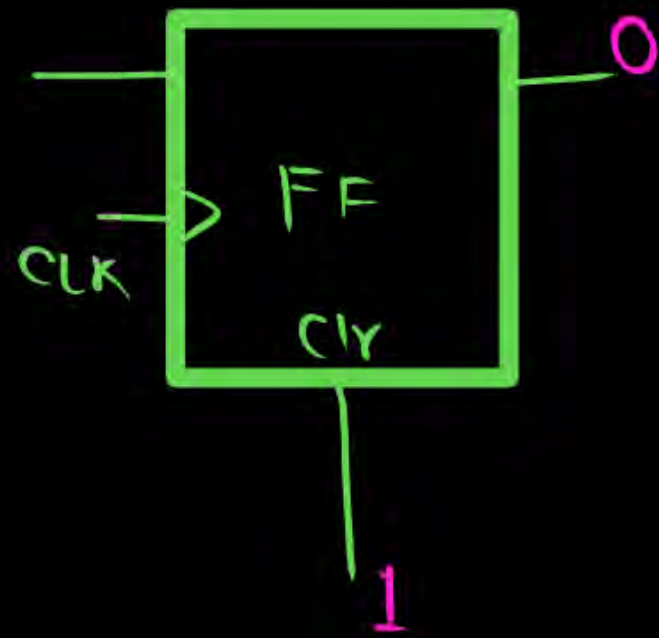


PRESET

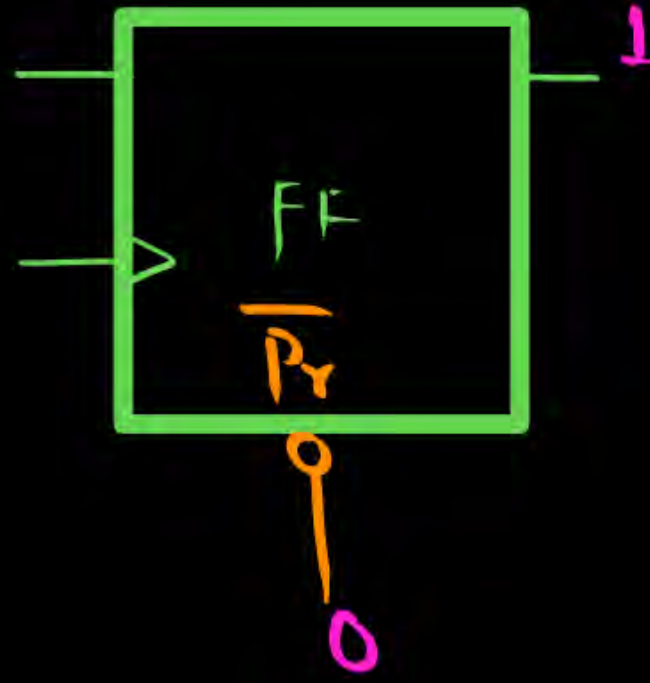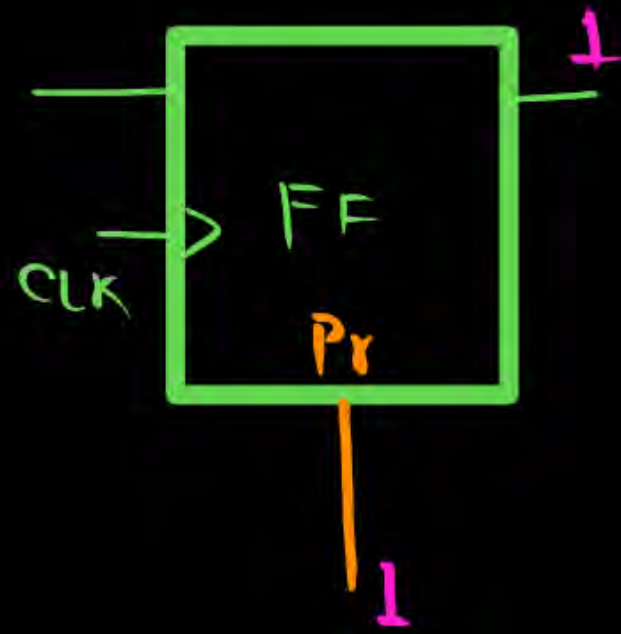

FEEDBACK REDUCES THE NUMBER OF STATES

Ex.

MOD 5 UP Ripple counter.

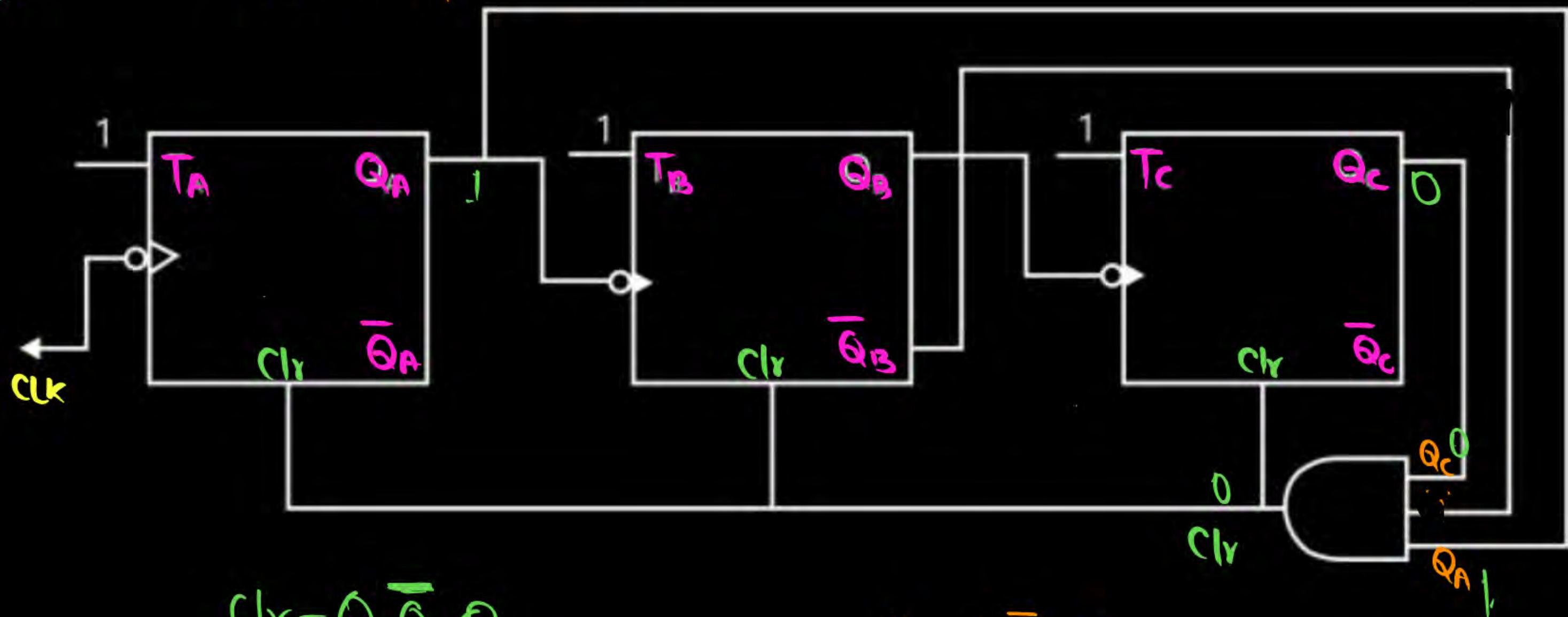

$$\text{Clr} = Q_C \bar{Q}_B Q_A$$

1 0 1 = 5

$$\text{Clr} = Q_C \bar{Q}_B Q_A$$

1 0 1 = 5 ✓

FEEDBACK REDUCES THE NUMBER OF STATES



000 ←
001
010
011
100

CLK	Q_C	Q_B	Q_A	$CLR = Q_C \bar{Q}_B Q_A$
0	0	0	0	0
1	0	0	1	0
2	0	1	0	0
3	0	1	1	0
4	1	0	0	0
5	1 0	0 1	1 0	1 0
6	0	0	1	0
7	0	1	0	0
8	0	1	1	0



$$C/r = Q_C Q_B \overline{Q_A}$$


$$C18 = Q_C Q_B \bar{Q}_A$$

$$1 \cdot 1 \cdot 0 = 6$$

000 → 001 → 010 → 011 → 100 → 101

CLK	Q _C	Q _B	Q _A	Clr
0	0	0	0	0
1	0	0	1	0
2	0	1	0	0
3	0	1	1	0
4	1	0	0	0
5	1	0	1	0
6	1 0	1 0	0 0	1 0
7	0	0	1	0
8	0	1	0	0

11Q

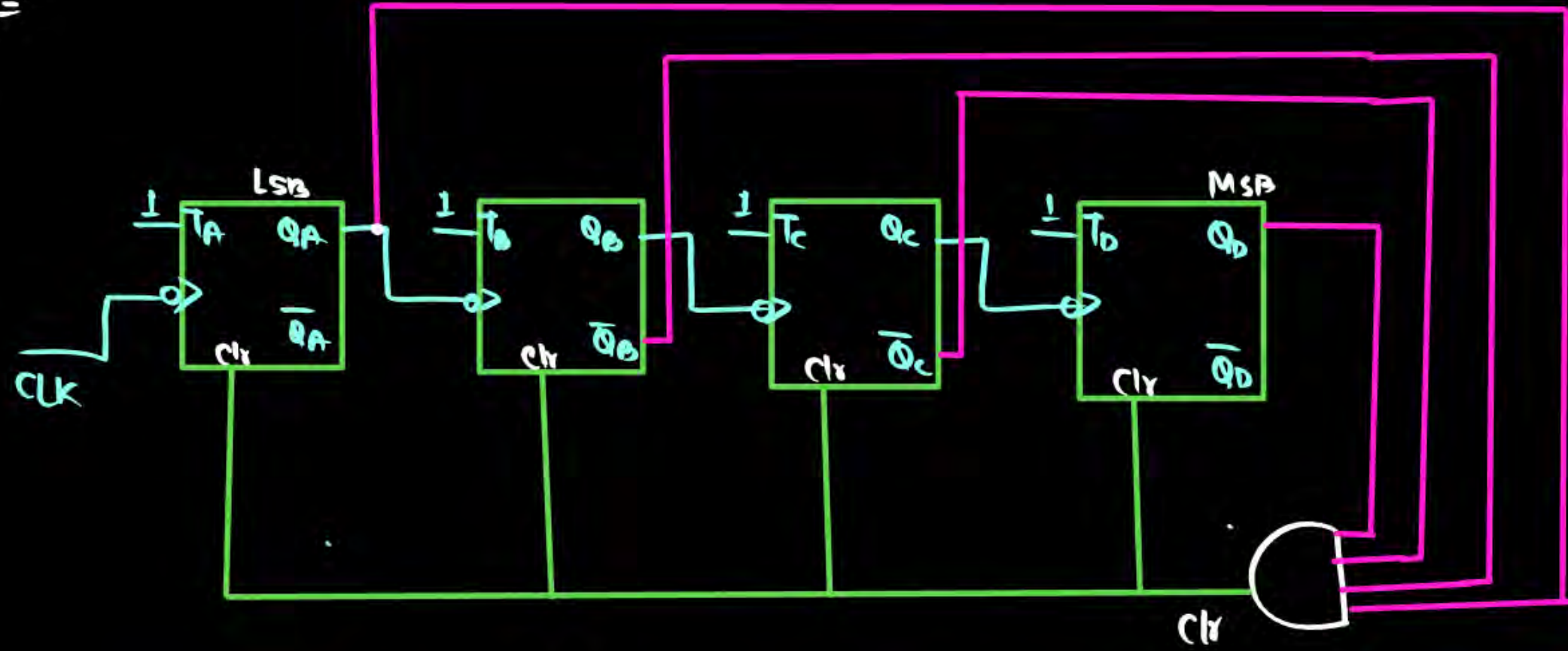


MOD-9 UP Ripple counter.

$$clr = Q_D \bar{Q}_C \bar{Q}_B Q_A$$

$$1001 = 9$$

CLK	Q_D	Q_C	Q_B	Q_A	clr
0	0	0	0	0	0
1	0	0	0	1	0
2	0	0	1	0	0
3	0	0	1	1	0
4	0	1	0	0	0
5	0	1	0	1	0
6	0	1	1	0	0
7	0	1	1	1	0
8	1	0	0	0	0
9	1	0	0	1	0
10	0	0	0	1	
11	0	0	1	0	


Design a BCD Ripple Carry counter?

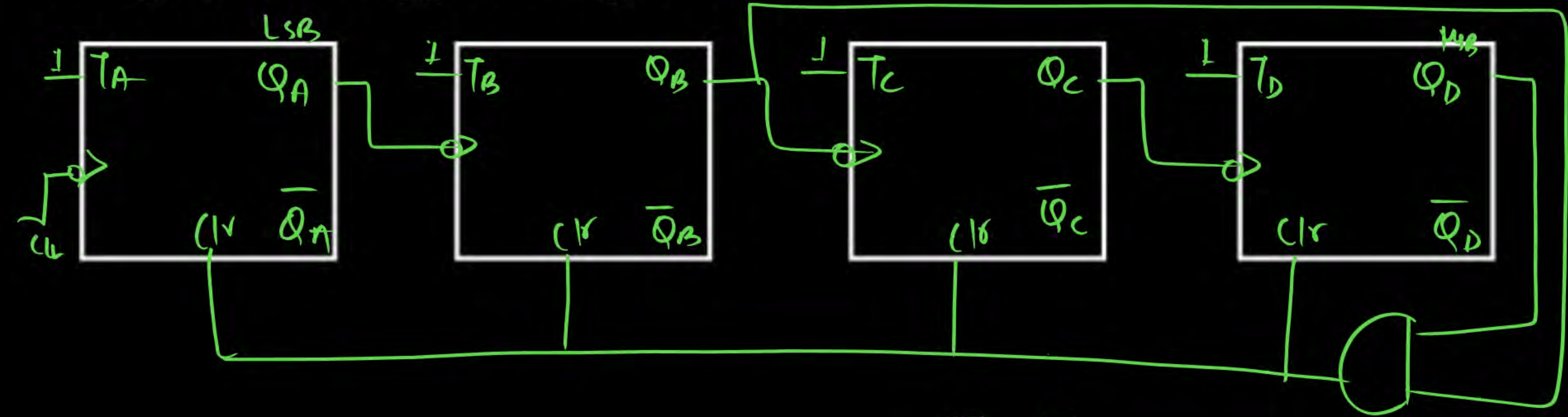

$$C1r = Q_D \overline{Q_C} Q_B \overline{Q_A}$$

Q.

Which type of counter is shown below?

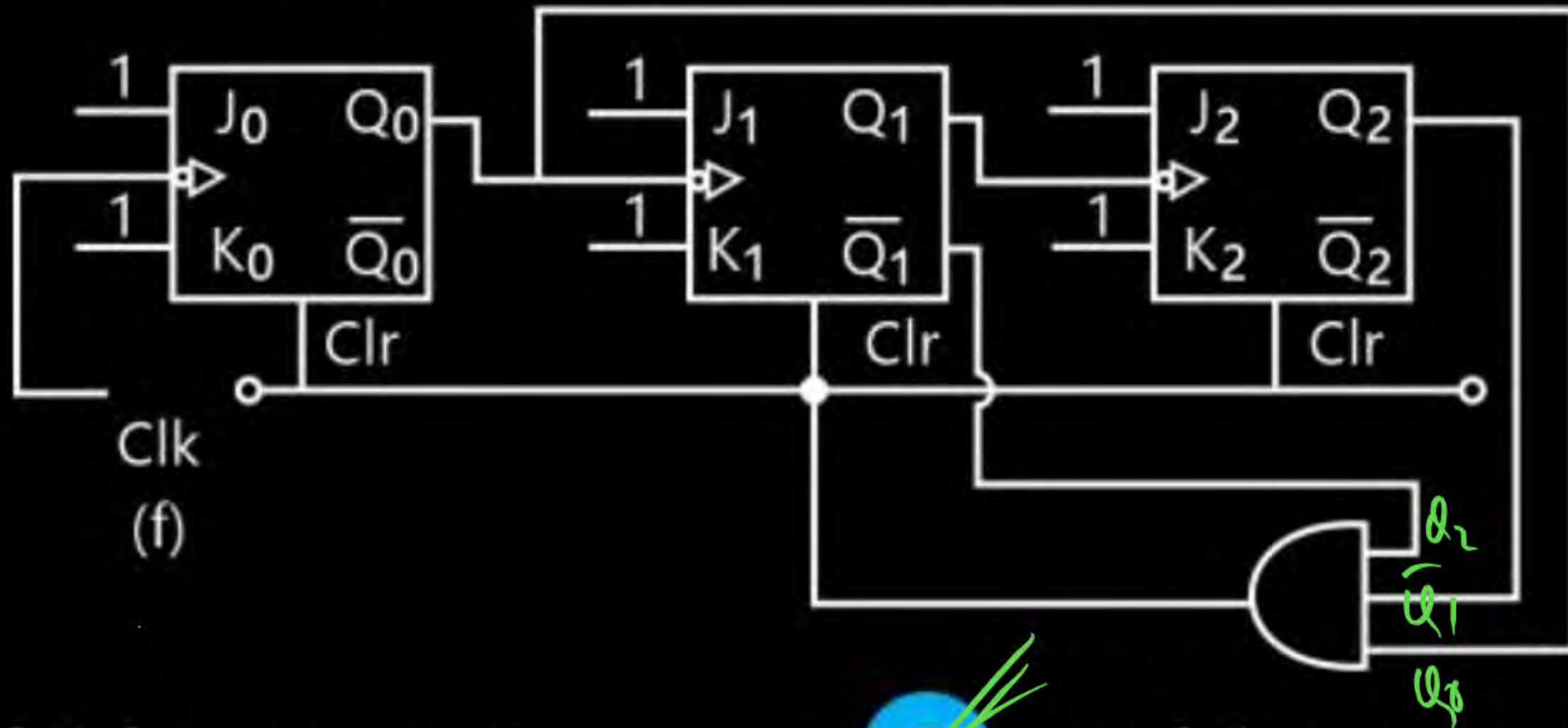

$$Clr = Q_2 \bar{Q}_1 Q_0$$

(011)

A

mod 5 down counter

~~B~~

mod 5 up counter

C

mod 6 up counter

D

mod 6 down counter

Q.

Consider the following counter

If counter starts at 000, what will be the count after 13 clock pulses?


A 100

146

B 101

C 110

D 111

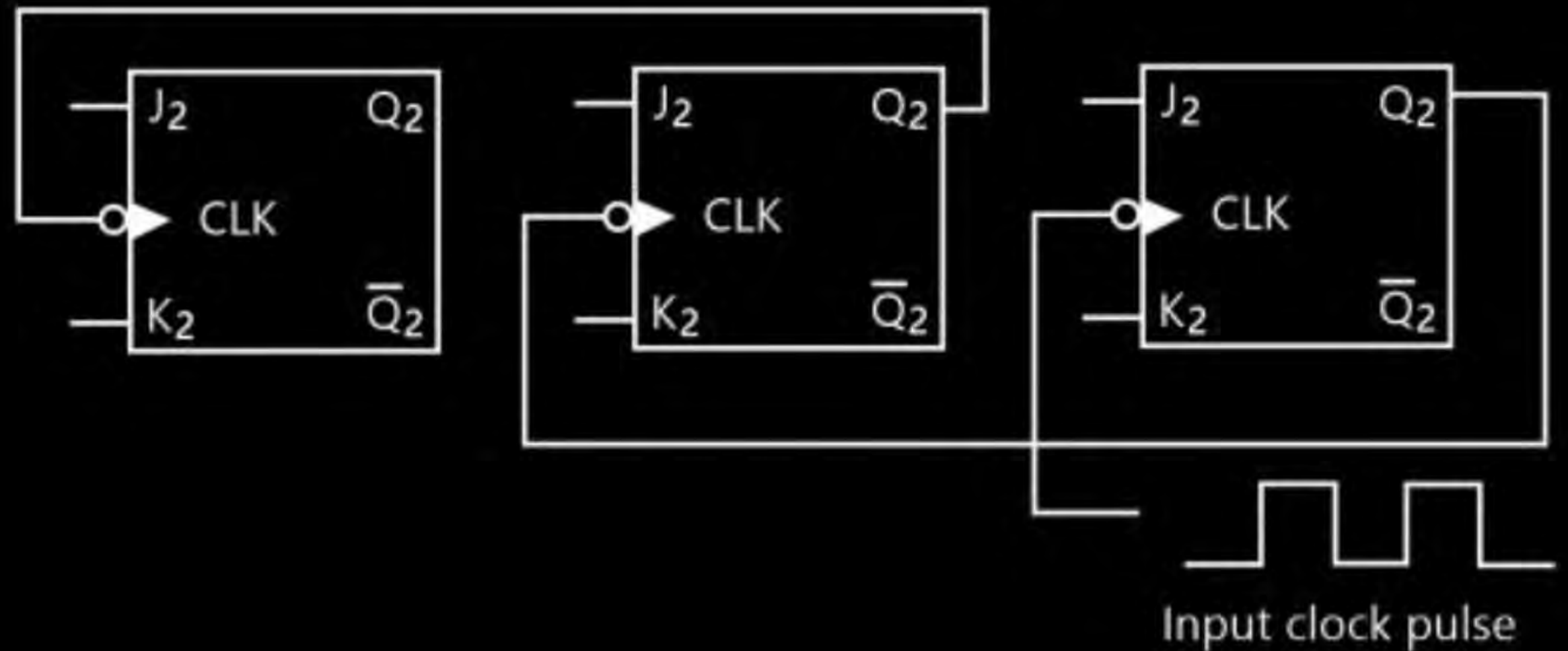

- Q Design a MOD-13 UP Ripple counter.
- Q Design a MOD-21 UP Ripple counter.
- Q Design a MOD-27 UP Ripple counter.
- Q Design a MOD14 UP Ripple counter.

Thank you

GW
Soldiers !

