

CS & IT ENGINEERING

DIGITAL LOGIC

Logic Gate

Lecture No. 1



By- CHANDAN SIR

AIR-23
26

ISRO

TOPICS TO BE COVERED

✓ 01 Syllabus

✓ 02 Weightage

✓ 03 Reference Books ✗

✓ 04 NOT GATE

Connect me on Telegram-



t.me/CJSIR

"Jack kielby"



Gordon E. Moore



Flip Flop



JK - FLIP-FLOP

→ Jack Keilby

IC

Integrated circuit

papa of IC

Gordon E. Moore

INTEL

दुकान (shop)

1962

1965

Statement

Nobel prize

Moore's Law

1 element → 1958

2 element → 1960

4 element → 1962

8 element → 1964

CS & IT ENGINEERING

Digital Logic

" Boolean algebra. Combination and sequential circuits. Minimization. Number representations and computer arithmetic (fixed and floating point).

CS & IT ENGINEERING

DIGITAL LOGIC

Number of Questions 2 to 4

Marks 4 to 6

Frequently Asked Topics Boolean algebra. Combinational and sequential circuits. Minimization. Number representation.

Reference Books



CJ sir ke
Notes



Book Name: Digital Design
Author: M. Morris Mano &
Michael D. Ciletti
Publisher: Pearson Publisher


Book Name: Digital
fundamental
Author: Thomas L. Floyd
Publisher: Pearson Publisher

Guidelines to Attend Live Class

- ✓ Attend the class with positive attitude.
- ✓ Punctuality is necessary.
- ✓ Follow the day-wise study plan.
- ✓ Attempt DPP daily as per the schedule.
- ✓ Hold chat while attending the class. We will allow you to ask and put your questions in the comment box.

DPP → 13 question

S.N.	Chapter	Topic
1	Logic Gate	NOT, AND, OR, NAND, NOR, X-OR, X-NOR, Inhibition.
2	Minimization	<div> <div>Boolean algebra</div> <div>K-MAP</div> </div>
3	Combination Circuit	Comparator, MUX, DE-MUX, Encoder, Decoder Half adder, Full adder, Half subtractor, Full subtractor. Serial adder, parallel adder, LACA, Multiplier. complement subtractor.
4	Sequential Circuit	Latches, Flip-Flops, Registers, counters, state Diagram Representation
5	Number System	<div> <div>Base conversion</div> <div>Magnitude Representation</div> </div>

 

t.me/cjsir

Chapter-1

└─ 20 pages

└─ 4 pages


INVERTER

NOT GATE, NEGATION, COMPLEMENT LOGIC



1. NOT GATE


"Propagation delay" [τ_{pd}]

 




INVERTER

"BUFFER"

 

 

$N \rightarrow \text{Even}$


BUFFER

$N \rightarrow \text{Odd}$


INVERTER

"Multivibrator"

Count

 

INVERTER

 

HIGH


$2\tau_{pd} \quad 2\tau_{pd} \quad 2\tau_{pd} \quad 2\tau_{pd}$
 $1 \rightarrow 1 \rightarrow 1 \rightarrow 1 \rightarrow \dots$




$2\tau_{pd} \quad 2\tau_{pd} \quad 2\tau_{pd} \quad 2\tau_{pd}$
 $0 \rightarrow 0 \rightarrow 0 \rightarrow 0 \rightarrow \dots$

LOW

Whenever EVEN no. of NOT GATE in Loop \rightarrow

- 1> Basic Memory element
- 2> Bistable Multivibrator
- 3> Dc generator ($f=0\text{Hz}$)

   When  no. of NOT GATE in Loop \rightarrow



- 1> Astable Multivibrator
- 2> Square wave generator
- 3> Clock generator
- 4> Free Running circuit
- 5> Ring oscillator

$$T = 2\tau_{pd}$$


$$f = \frac{1}{T}$$

$$f = \frac{1}{2\tau_{pd}}$$

INVERTER



 $3\tau_{pd}$ $3\tau_{pd}$ $3\tau_{pd}$ $3\tau_{pd}$ $3\tau_{pd}$
 $0 \rightarrow 1 \rightarrow 0 \rightarrow 1 \rightarrow 0 \rightarrow 1 \rightarrow \dots$



$$T = 2 \times N \times \tau_{pd}$$

$$f = \frac{1}{2N \times \tau_{pd}}$$

$N \rightarrow$ No. of NOT
 GATE in Loop.
(odd)

$$T = 6\tau_{pd}$$

$$T = 2 \times 3 \times \tau_{pd}$$

Q.1



For the circuit given below, all NOT Gates are identical to each other and having propagation delay 10 ps. Find the frequency of generated wave form?

10^{-12}



$N \rightarrow 5$ $\tau_{pd} \rightarrow 10 \times 10^{-12}$

$$f = \frac{1}{2N \times \tau_{pd}}$$

$$f = \frac{1}{2 \times 5 \times 10 \times 10^{-12}} \text{ 1/sec}$$

$$f = \frac{10^{12}}{10 \times 10} \text{ Hz}$$

$$f = \frac{10 \cancel{0} \cancel{0} \times 10^9}{1 \cancel{0} \times 1 \cancel{0}} \text{ Hz}$$


$$f = 10 \text{ GHz}$$

☒ A. 10 GHz
C. 1 GHz

B. 100 GHz
☒ D. None

Q.2

Circuit given below are called.

 


- ☒ A. Astable Multivibrator
- ☐ B. Bistable Multivibrator

 Q.3

Hw



Sketch the waveform of y if all NOT GATES are identical and having propagation delay of 1 microsecond ?




Q.3

HW




For the circuit given below x & y condition will be-

 - A** x stable y toggle
- B** x toggle y stable
- C** x & y both toggle
- D** x & y both stable




INVERTER

- Revision

 

AC

 

Tesla
AC



Thank you

GW
Soldiers !

