

# CS & IT ENGINEERING

## DIGITAL LOGIC

### Combinational Circuit



Lecture No. 3



By- CHANDAN SIR




# TOPICS TO BE COVERED

01 MULTIPLEXER

02 QUESTION PRACTICE

03 DISCUSSION

# MULTIPLEXER

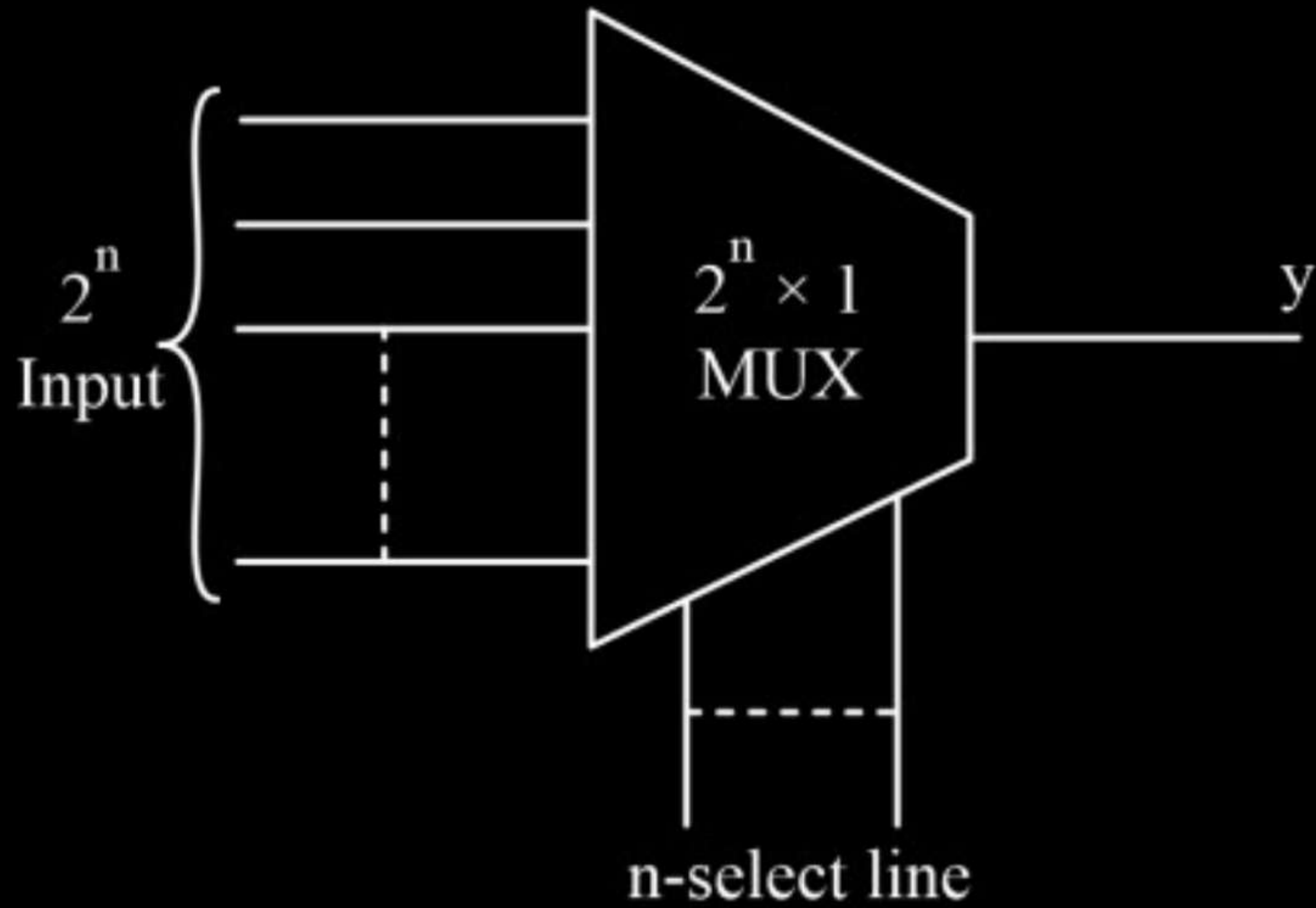



# Type 1. Designing of higher order MUX by using Lower order MUX



Ex

2x1 MUX

$$\frac{4}{2} + \frac{2}{2}$$

$$2 + 1 = 3$$

4x1 MUX

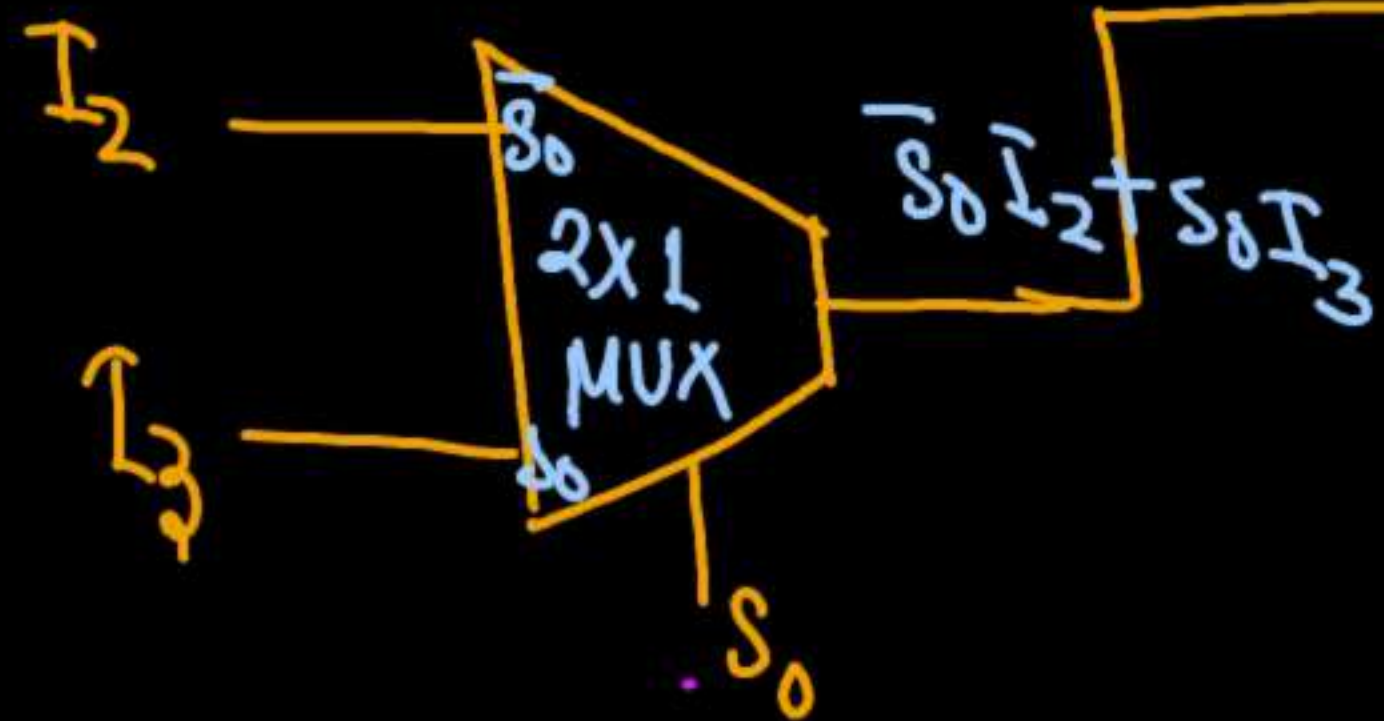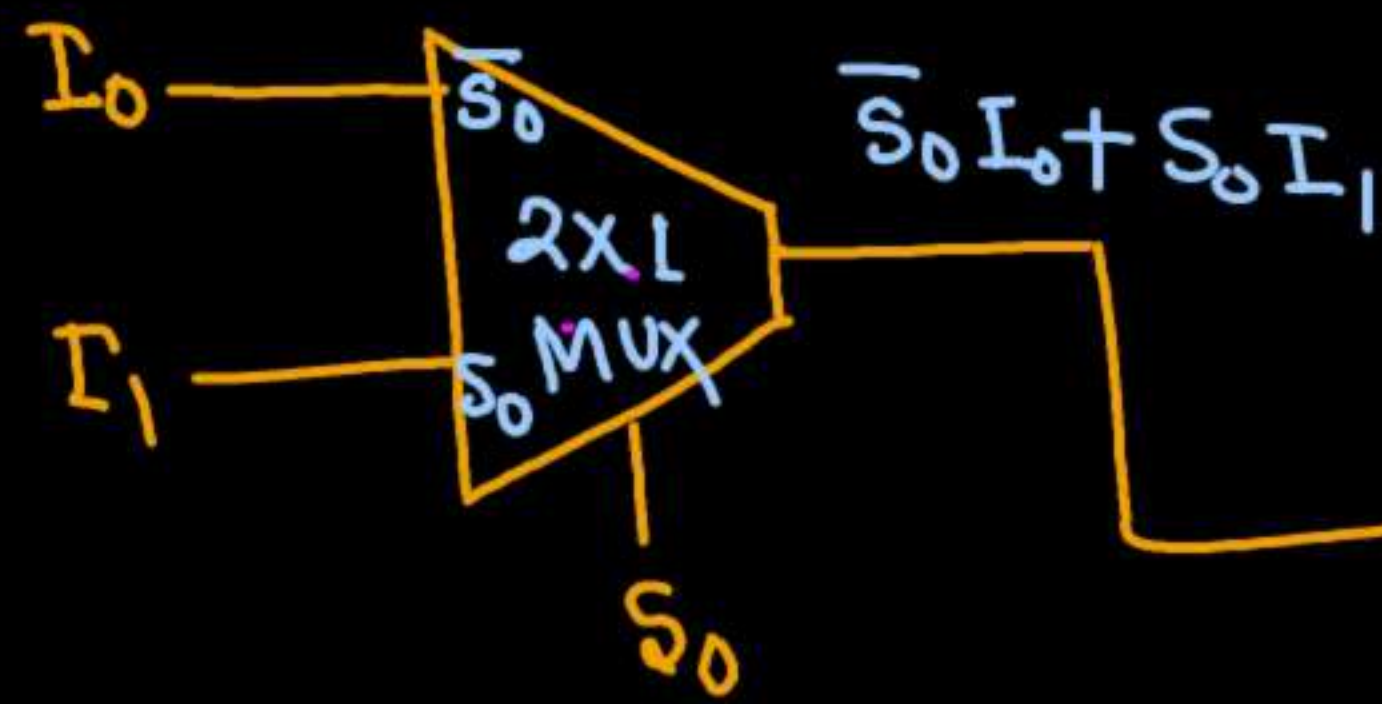

$$Y = \bar{S}_1 \bar{S}_0 I_0 + \bar{S}_1 S_0 I_1 + S_1 \bar{S}_0 I_2 + S_1 S_0 I_3$$

2  
4  
6  
8  
10  
12  
14  
16  
18  
20


Ex. 2.

2x1 MUX

$$\frac{8}{2} + \frac{4}{2} + \frac{2}{2}$$

$$4 + 2 + 1 = \textcircled{7} \text{ Ans}$$

8x1 MUX

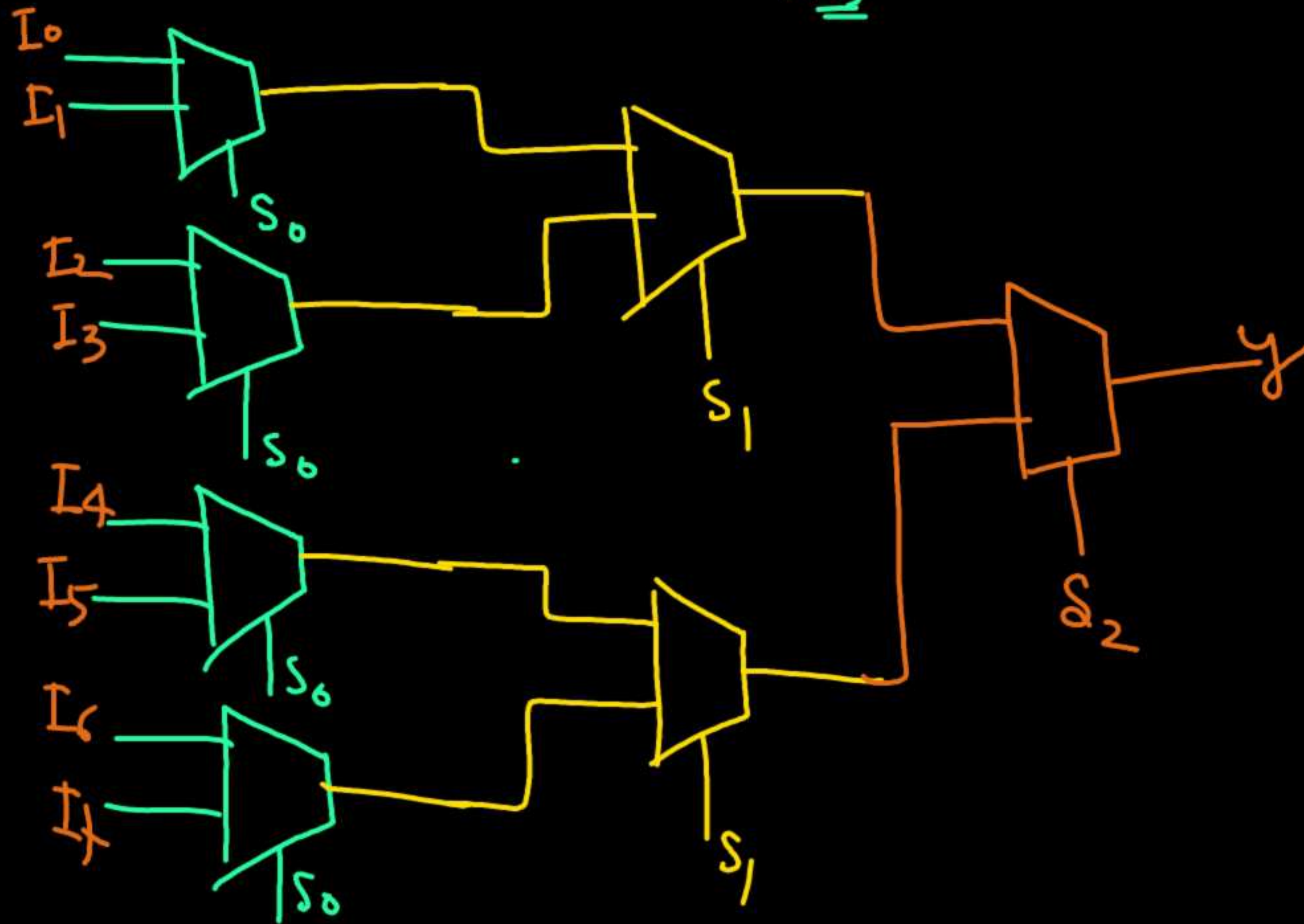




$$\textcircled{3} \quad 2 \times 1 \text{ MUX} \xrightarrow[\substack{8+4+2+1=15 \\ = \underline{15}}]{\frac{16}{2} + \frac{8}{2} + \frac{4}{2} + \frac{2}{2}} 16 \times 1 \text{ MUX}$$

$$\textcircled{4} \quad 2 \times 1 \text{ MUX} \xrightarrow[\underline{63}]{\text{Ans}} 64 \times 1 \text{ MUX}$$

$$\star \quad 2 \times 1 \xrightarrow[\underline{2^n - 1}]{\text{Ans}} 2^n \times 1 \text{ MUX}$$

Q
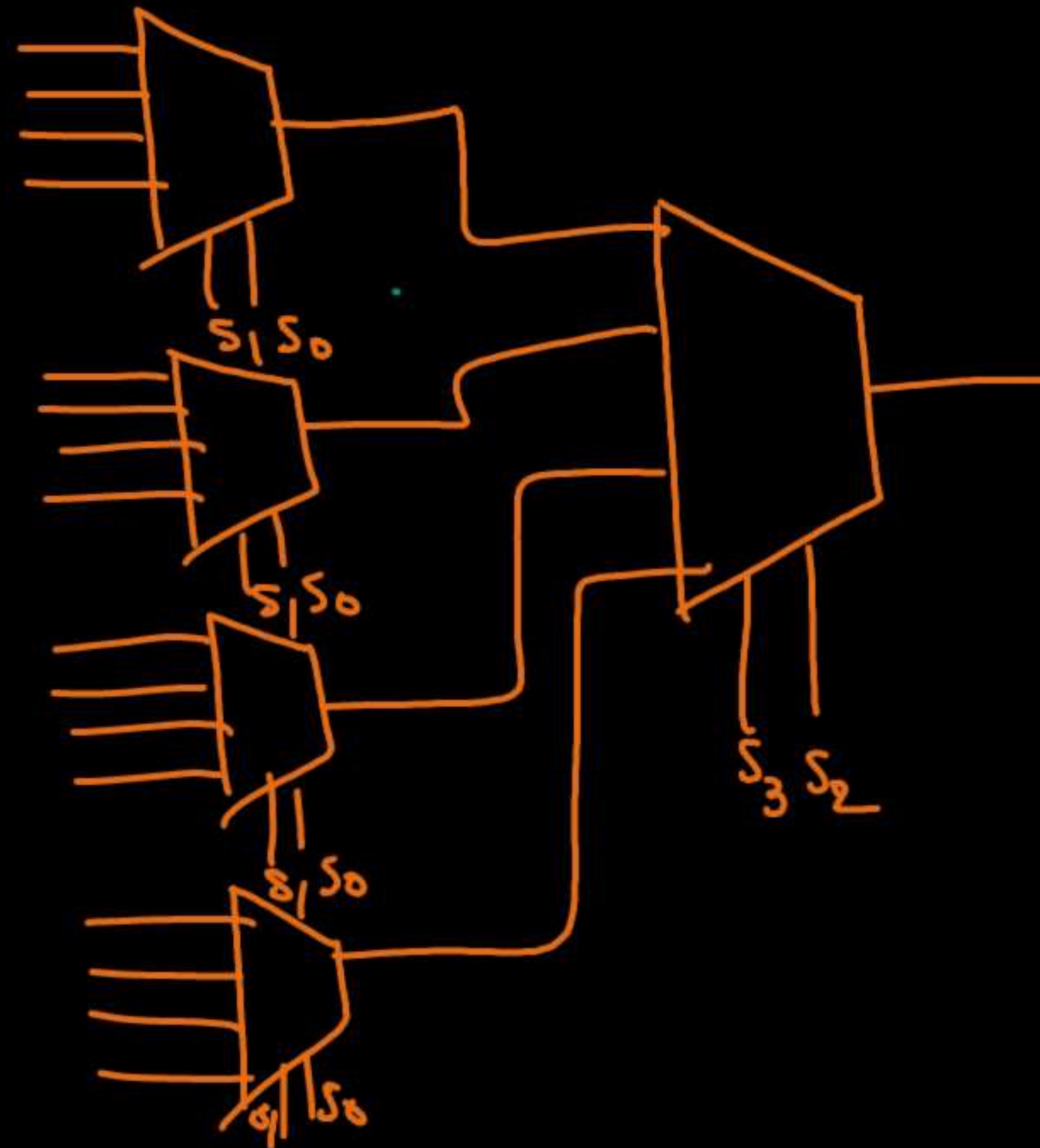
$$\underbrace{4 \times 1 \text{ MUX}}_{2 \text{ select line}} \xrightarrow[\substack{4 + 1 = \textcircled{5} \text{ Avr}}]{\frac{16}{4} + \frac{4}{4}} \underbrace{16 \times 1 \text{ MUX}}_{\text{Select line} = 4}$$




$$\underline{Q} \quad 4 \times 1 \text{ MUX} \xrightarrow[\substack{16 + 4 + 1 = 21}]{\substack{\frac{64}{4} + \frac{16}{4} + \frac{4}{4}}} 64 \times 1 \text{ MUX}$$




$$Q = \underbrace{4 \times 1 \text{ MUX}}_{2 \text{ select line}} \xrightarrow[2+1=\textcircled{3}]{\frac{8}{4} + \frac{2}{4}} \underbrace{8 \times 1 \text{ MUX}}_{3 \text{ select line}} \quad \underline{\underline{Ans}}$$

Method 1.


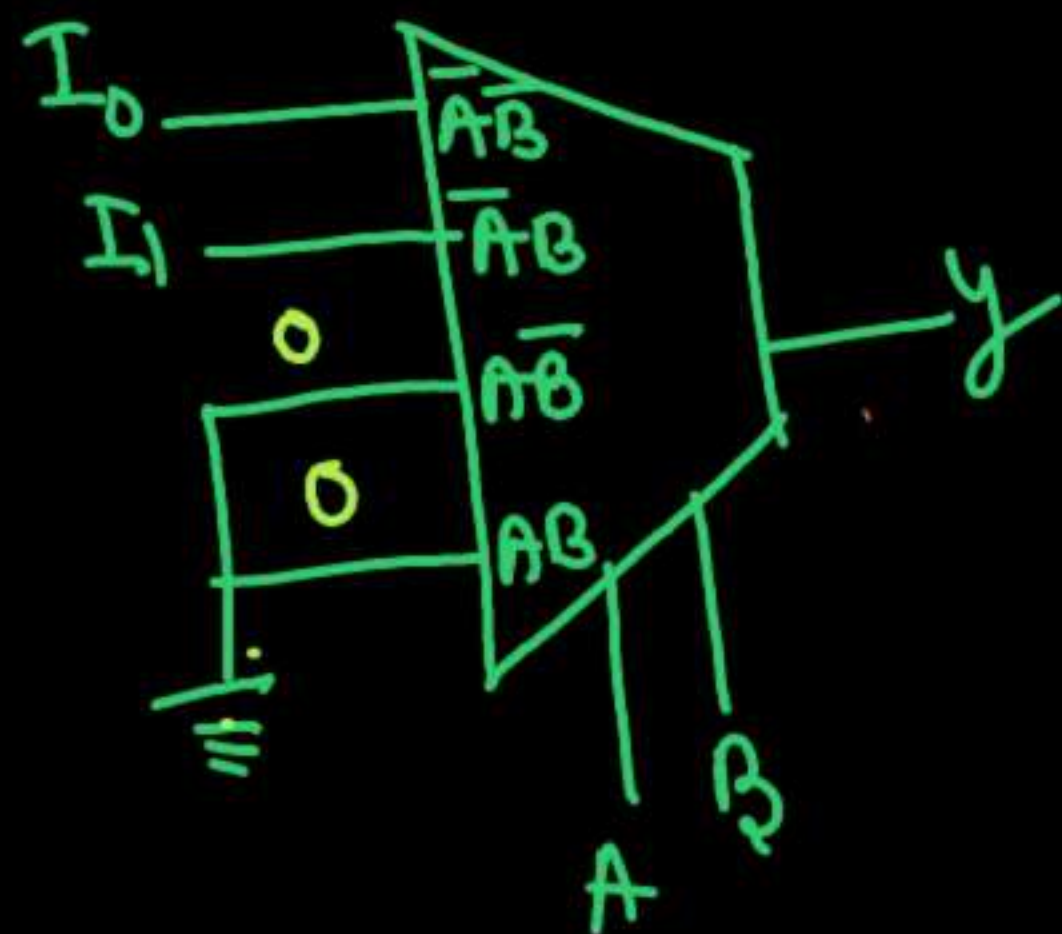


select line=2

Method 2.

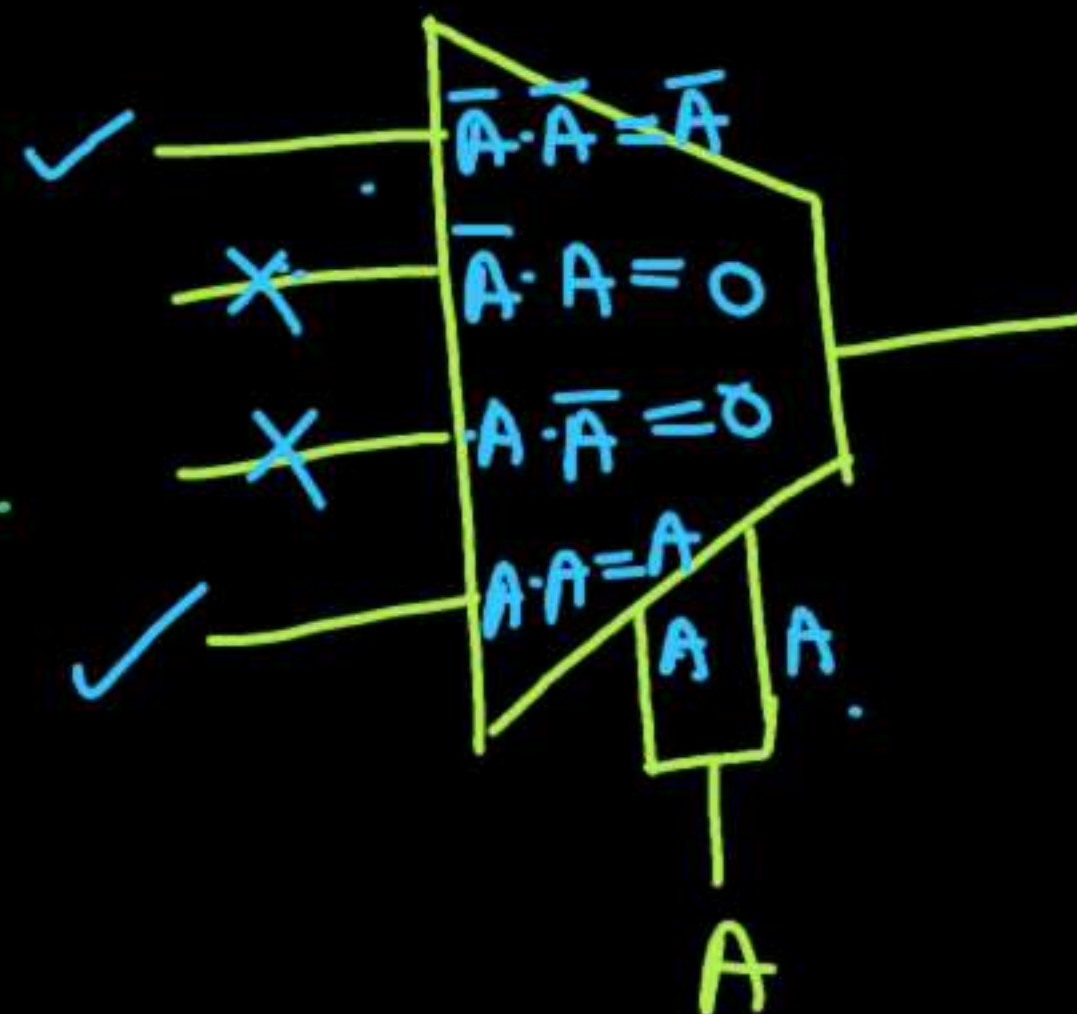

Select Variable=1

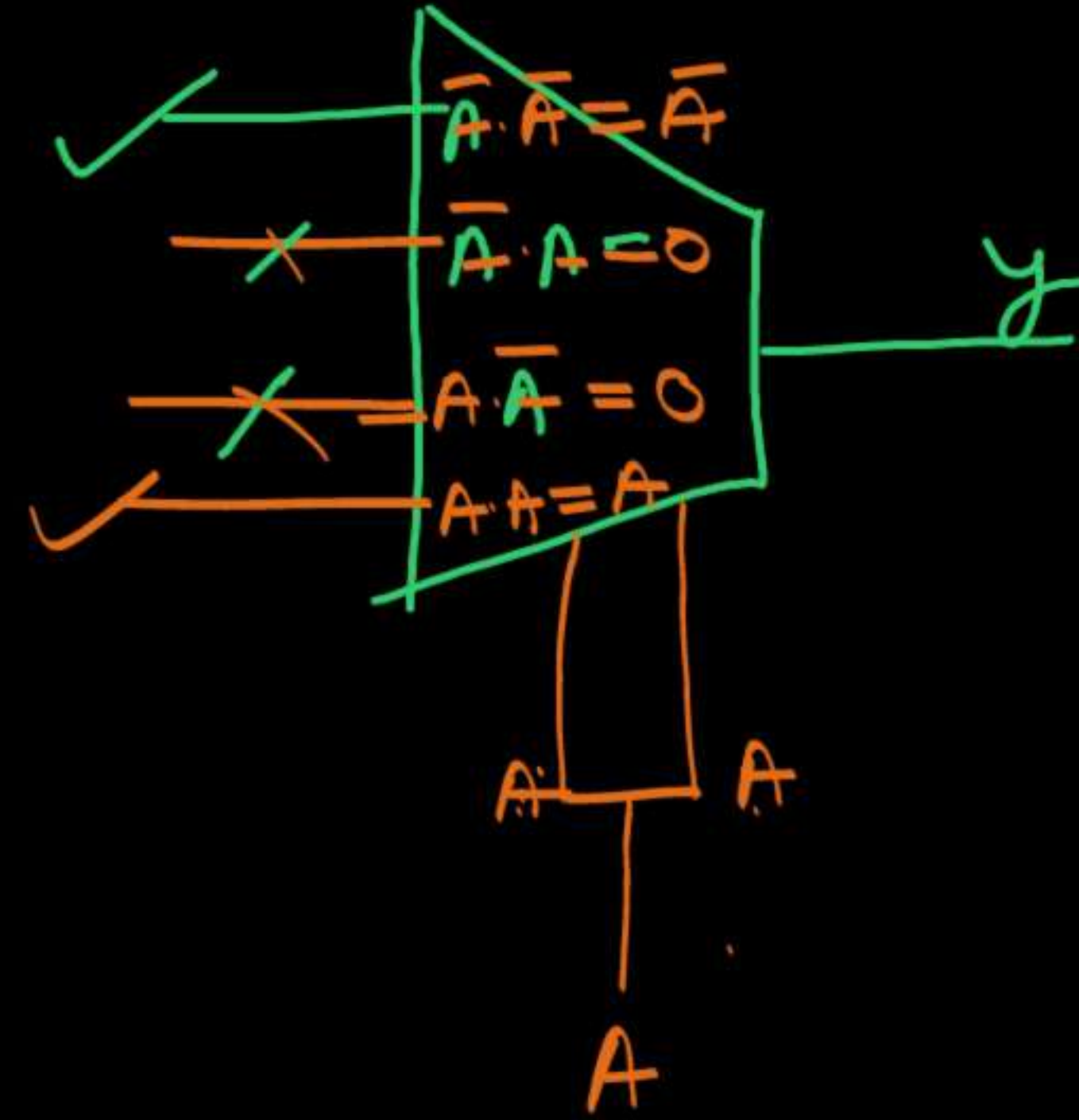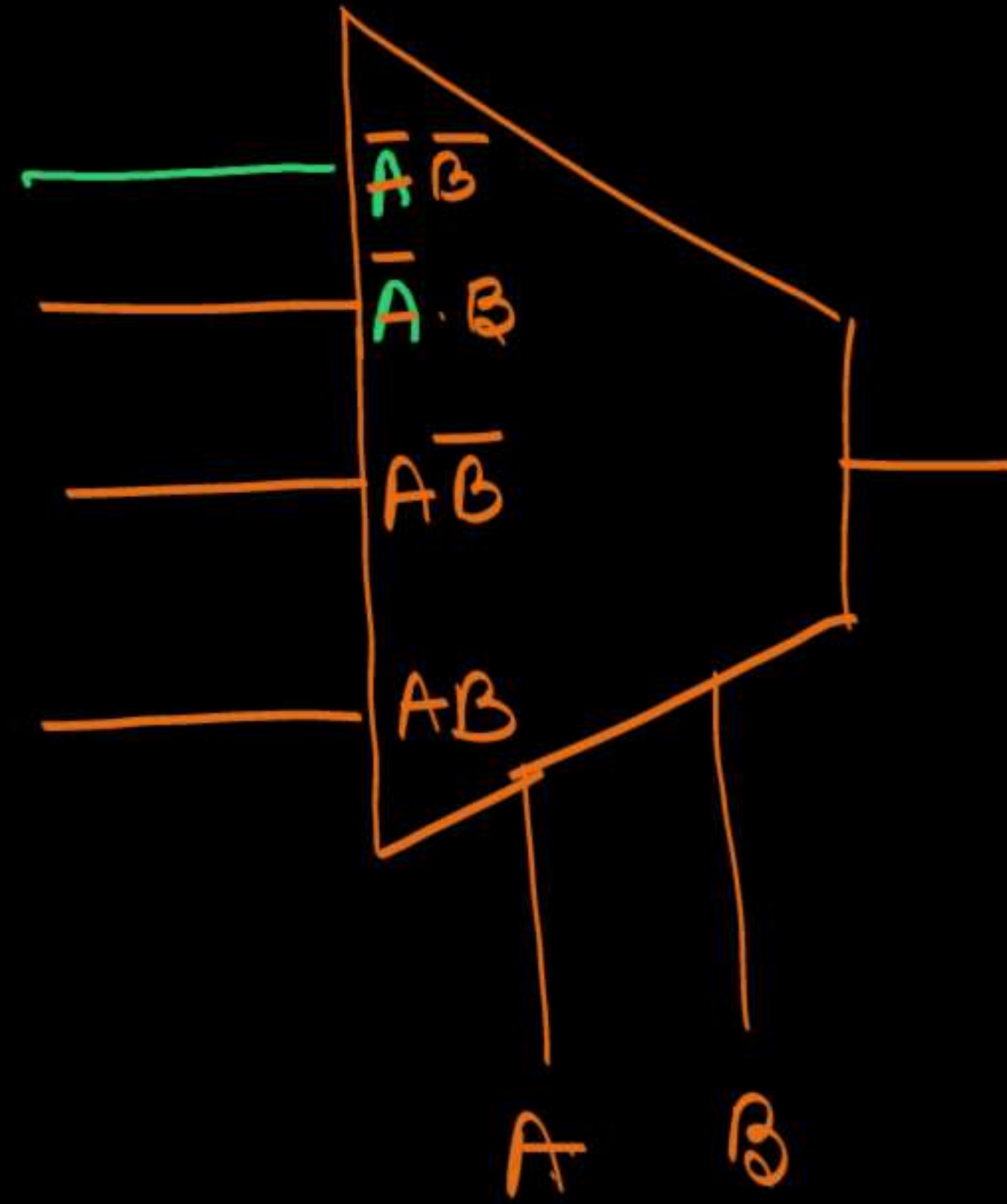




$A \cdot \bar{B} = 1 \cdot \bar{B} = \bar{B}$
$\bar{A} \cdot B = 1 \cdot B = B$
$A \bar{B} = 0 \cdot \bar{B} = 0$
$A B = 0 \cdot B = 0$
$\bar{A}$
$B$

### Method ③

NOTE →

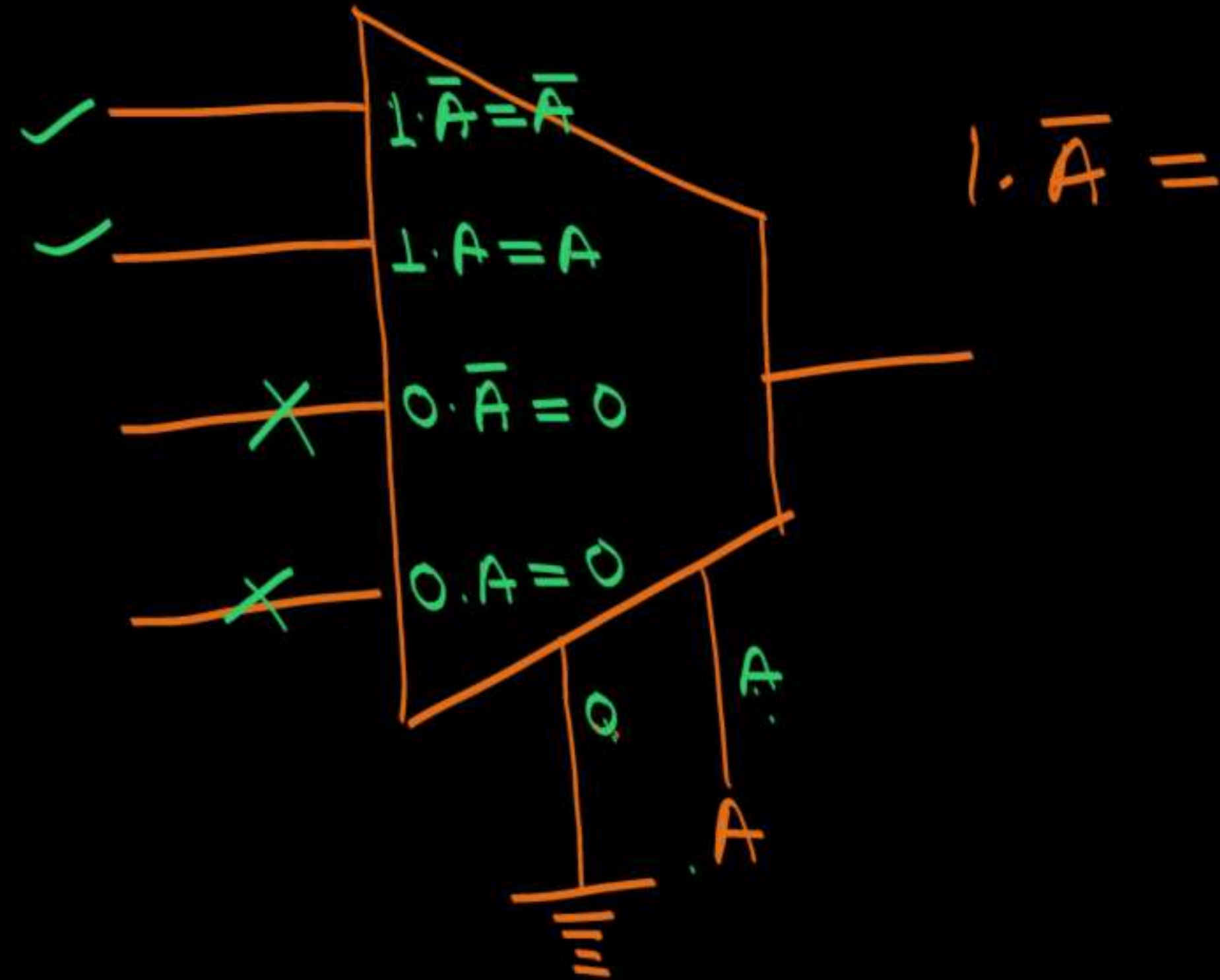



select Variable = one



$$4 \times 1 \xrightarrow[\substack{2+1=3}]{\substack{\frac{8}{4} + \frac{2}{4}}} 8 \times 1 \text{ MUX}$$


Select Variables = 3

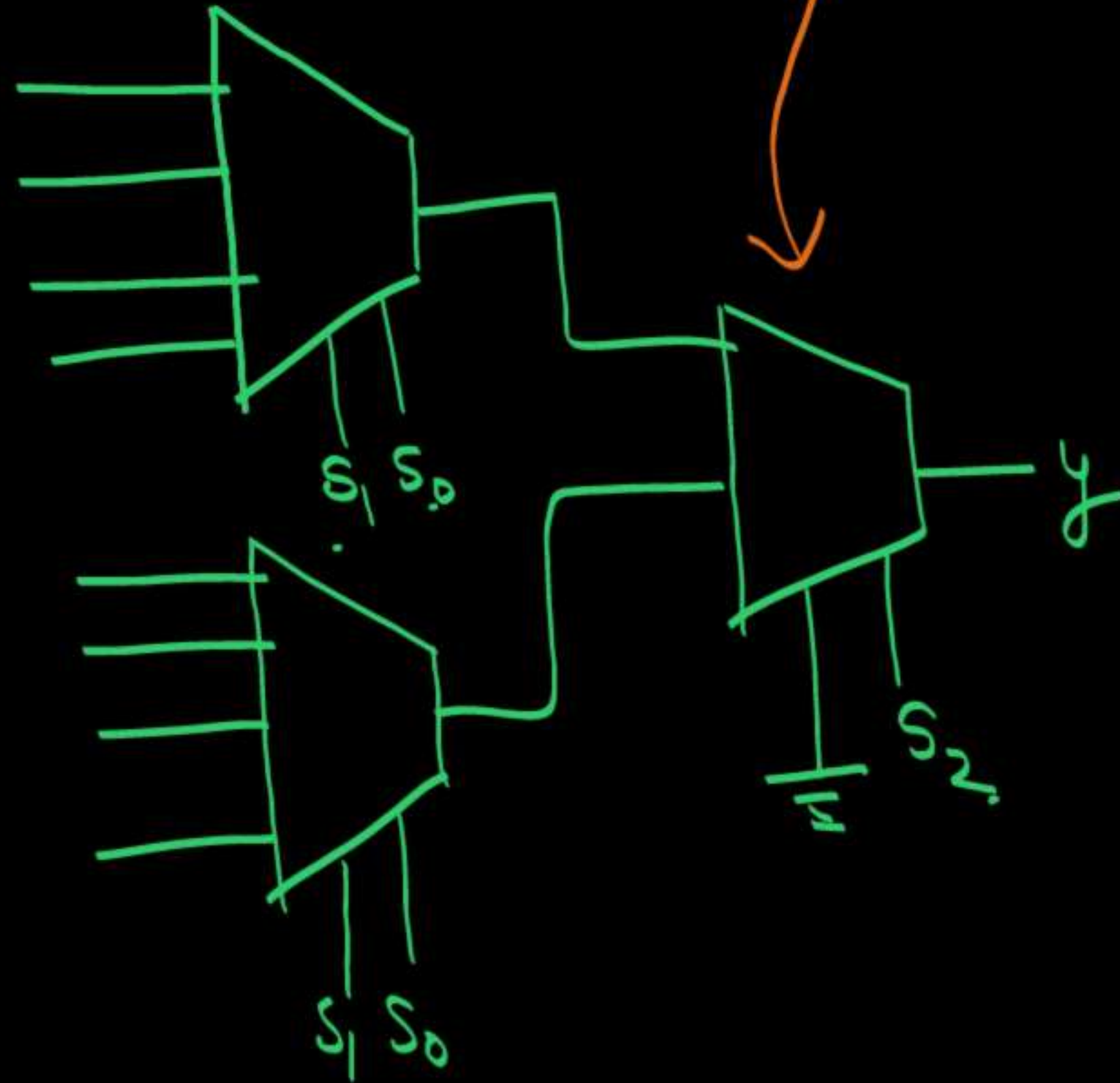

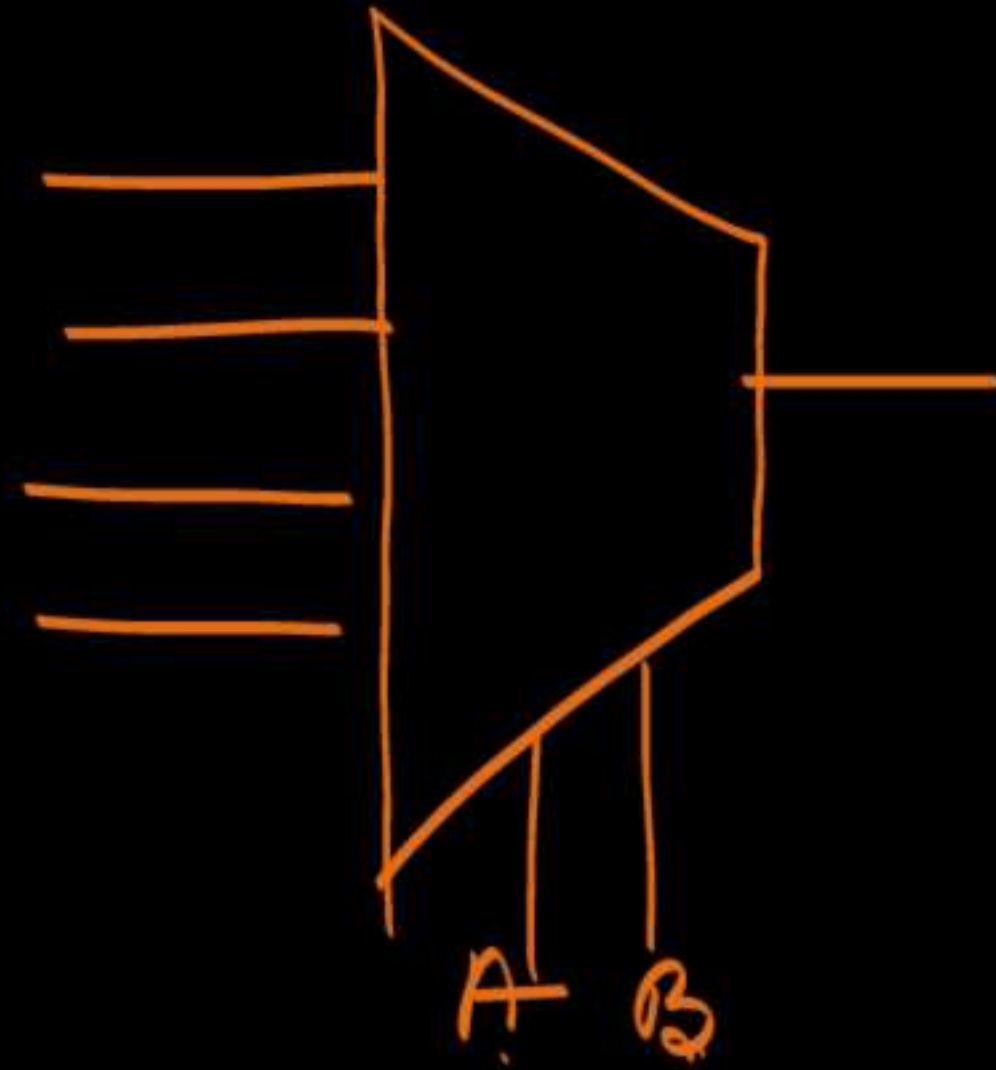

Select line = 2

Select Variable = 2

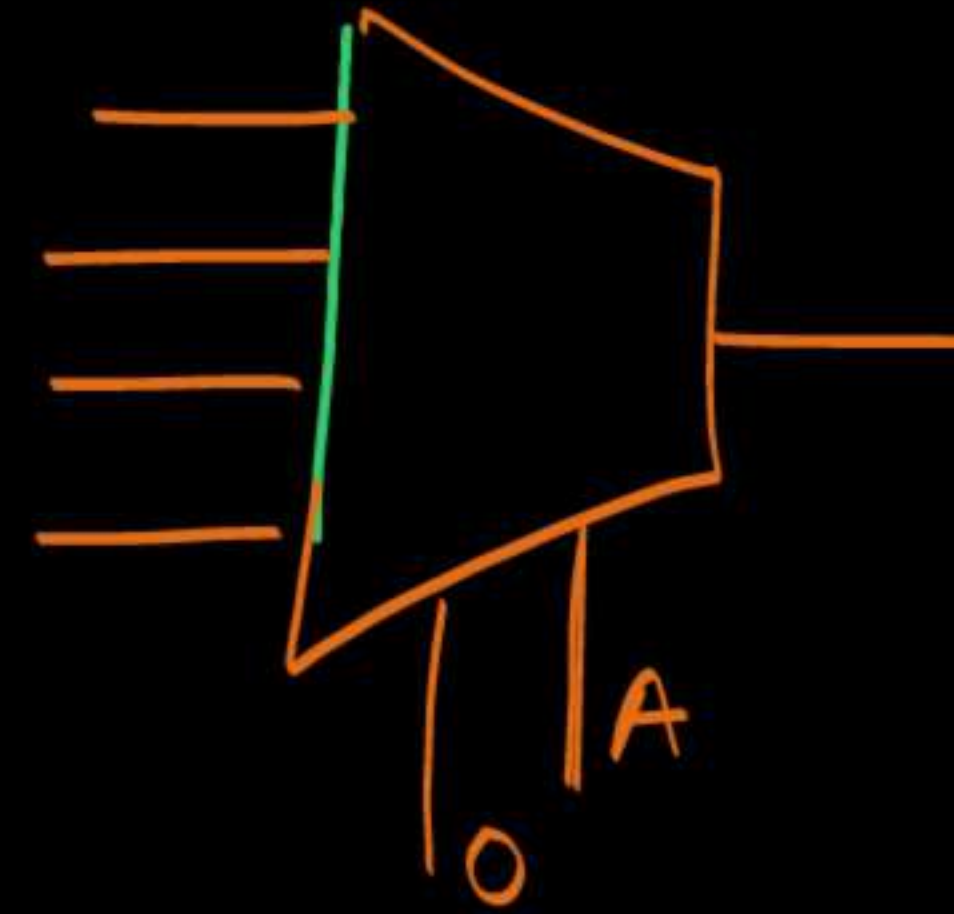

Select line

Select Variable = 1

==



Q  
2

$$4 \times 1 \text{ MUX} \xrightarrow{\frac{32}{4} + \frac{8}{4} + \frac{2}{4}} 32 \times 1 \text{ MUX}$$
$$8 + 2 + 1 = 11$$

Q


$$8 \times 1 \text{ MUX} \xrightarrow[\substack{\frac{64}{8} + \frac{8}{8} \\ 8 + 1 = 9}]{} 64 \times 1 \text{ MUX}$$

Q


$$16 \times 1 \text{ MUX} \xrightarrow[\substack{\frac{256}{16} + \frac{16}{16} \\ 16 + 1 = 17 \\ //}]{} 256 \times 1 \text{ MUX}$$



## Type(2) MUX As a universal Logic.

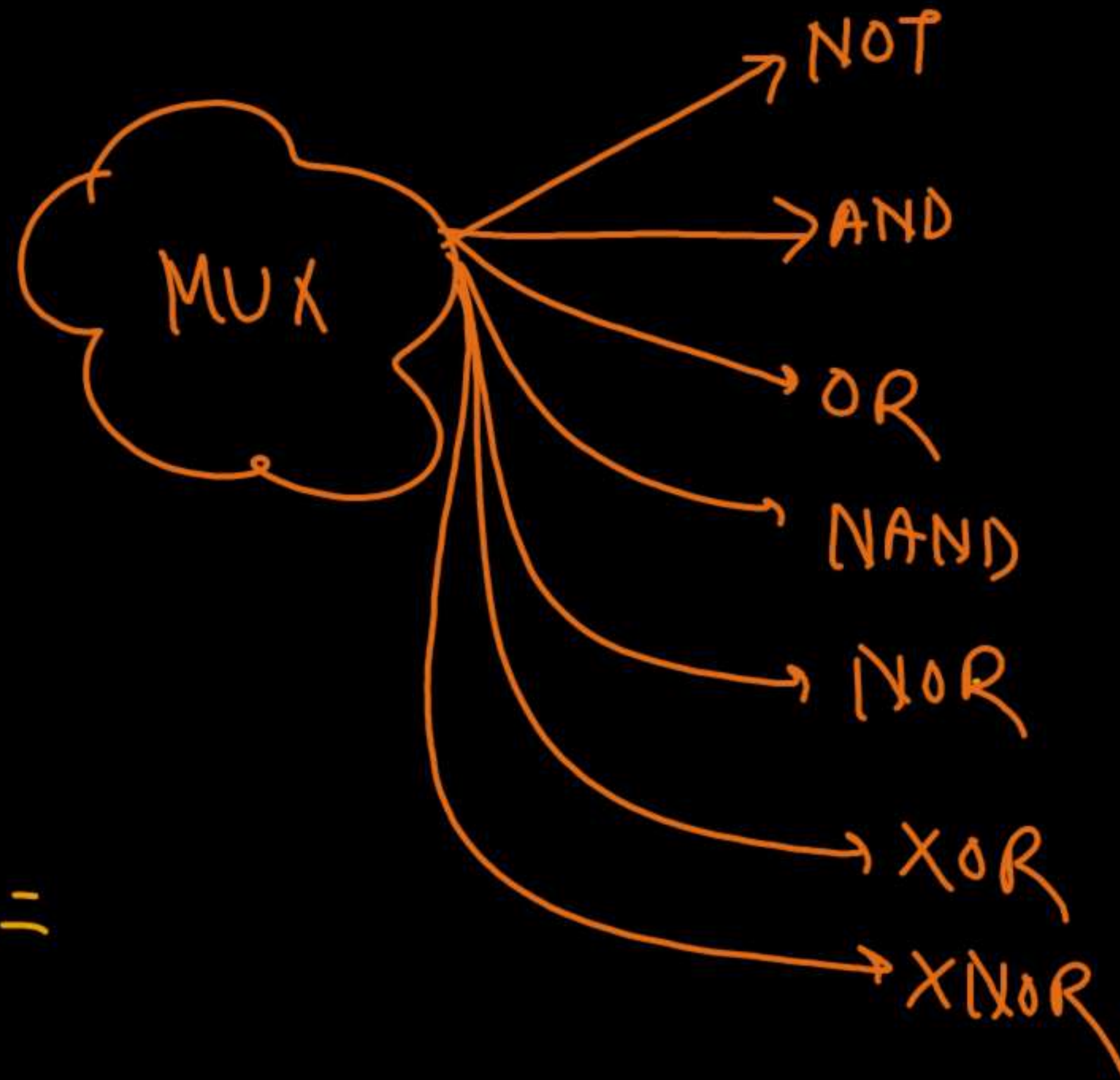



==

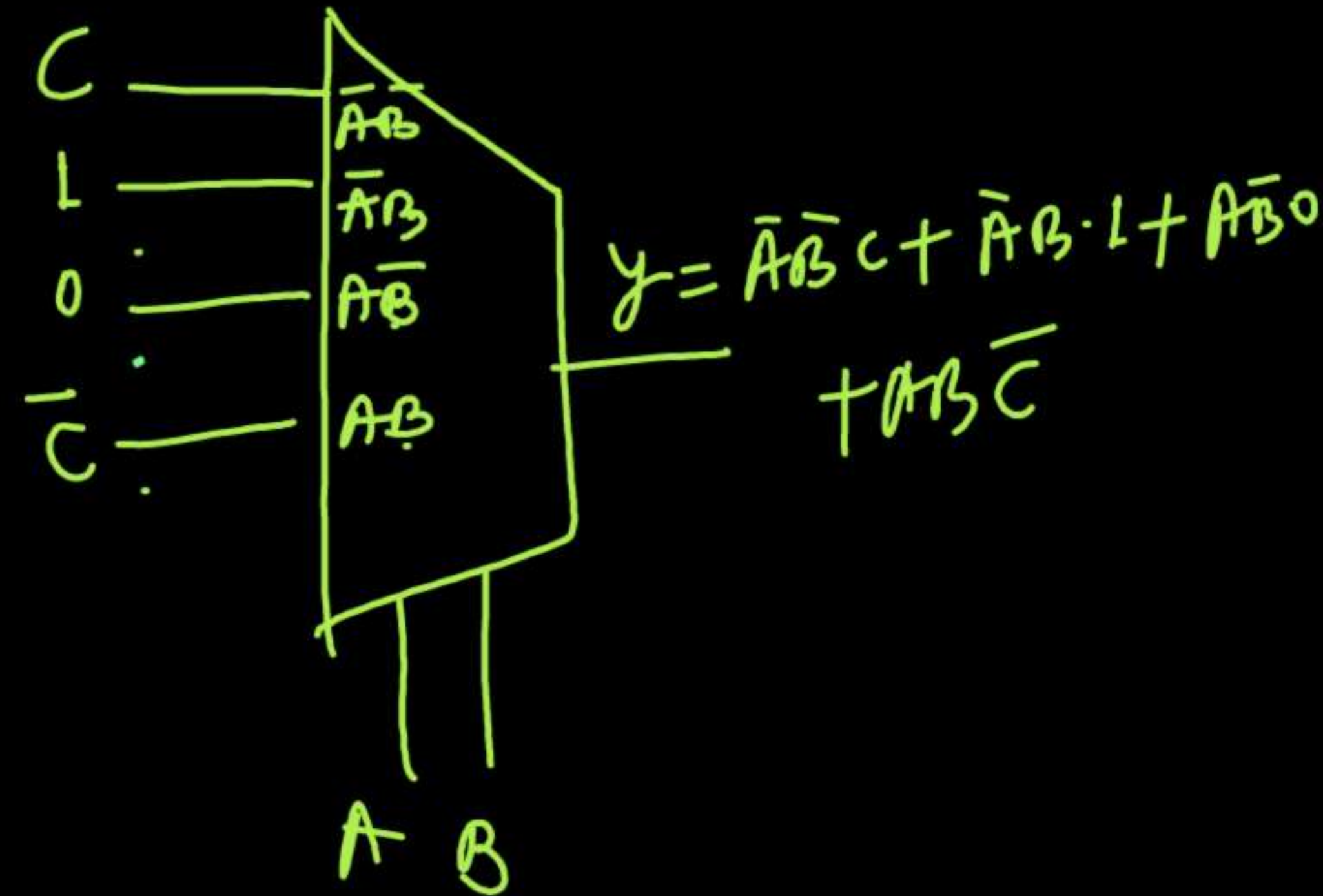

## Type-2 MUX as a Universal Logic





### 1. Not GATE

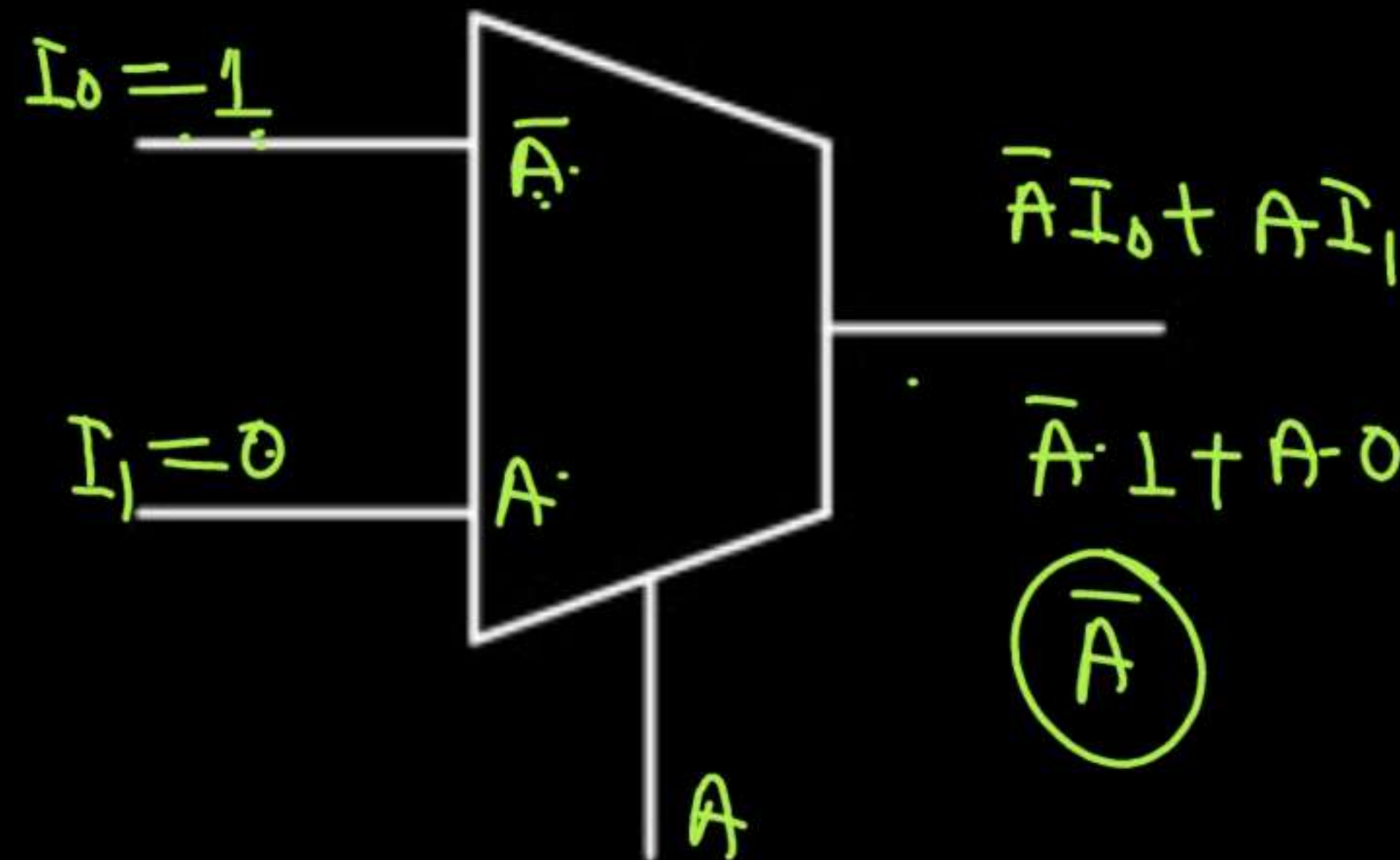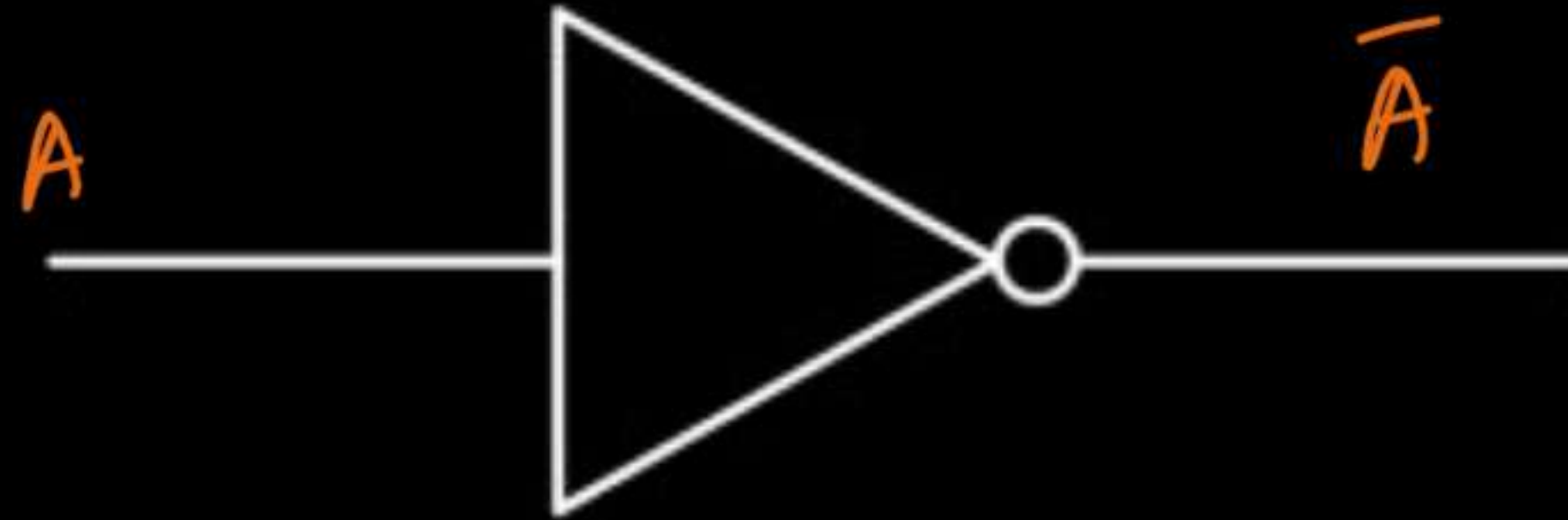

# MULTIPLEXER



## 2. AND GATE

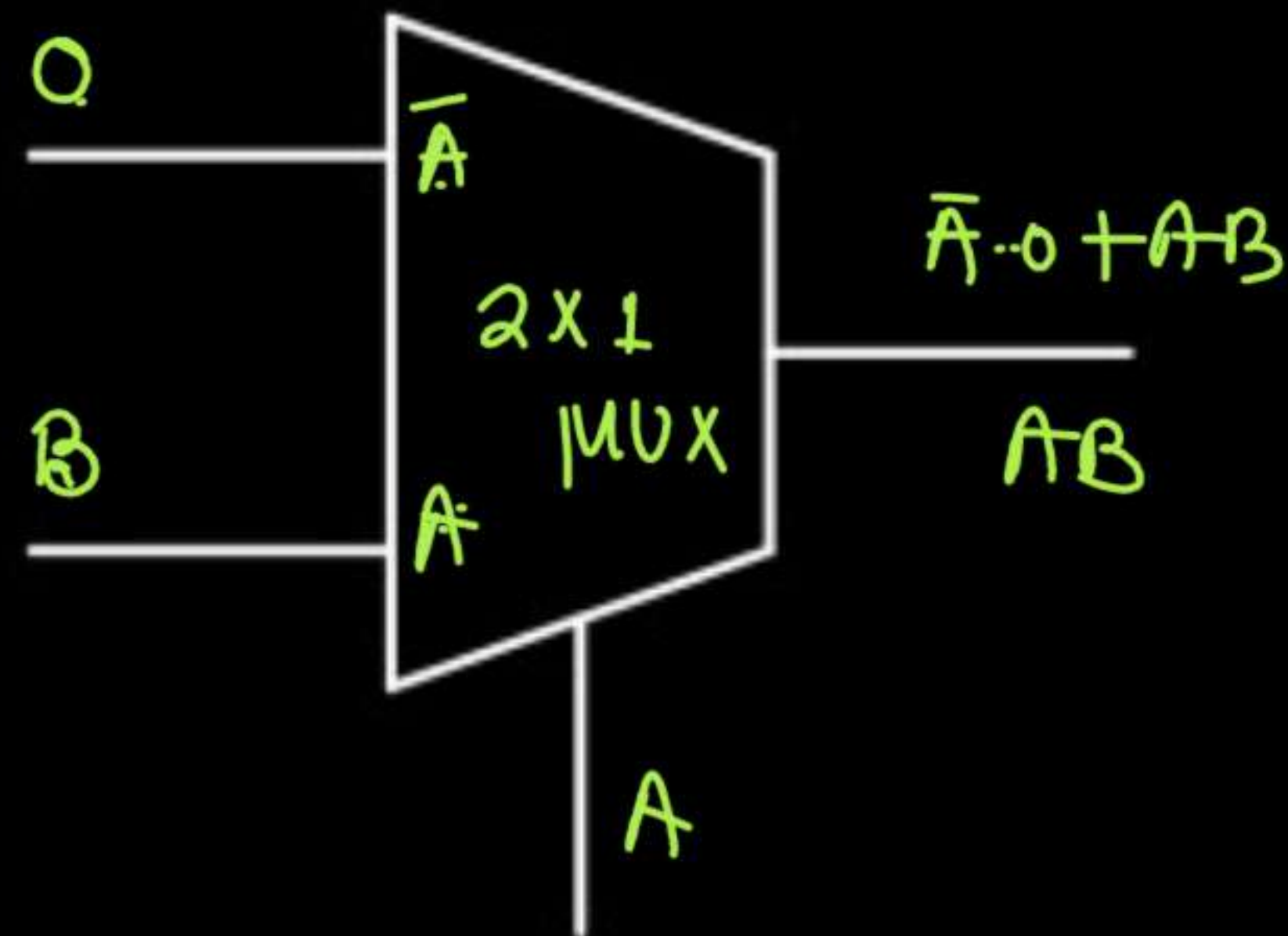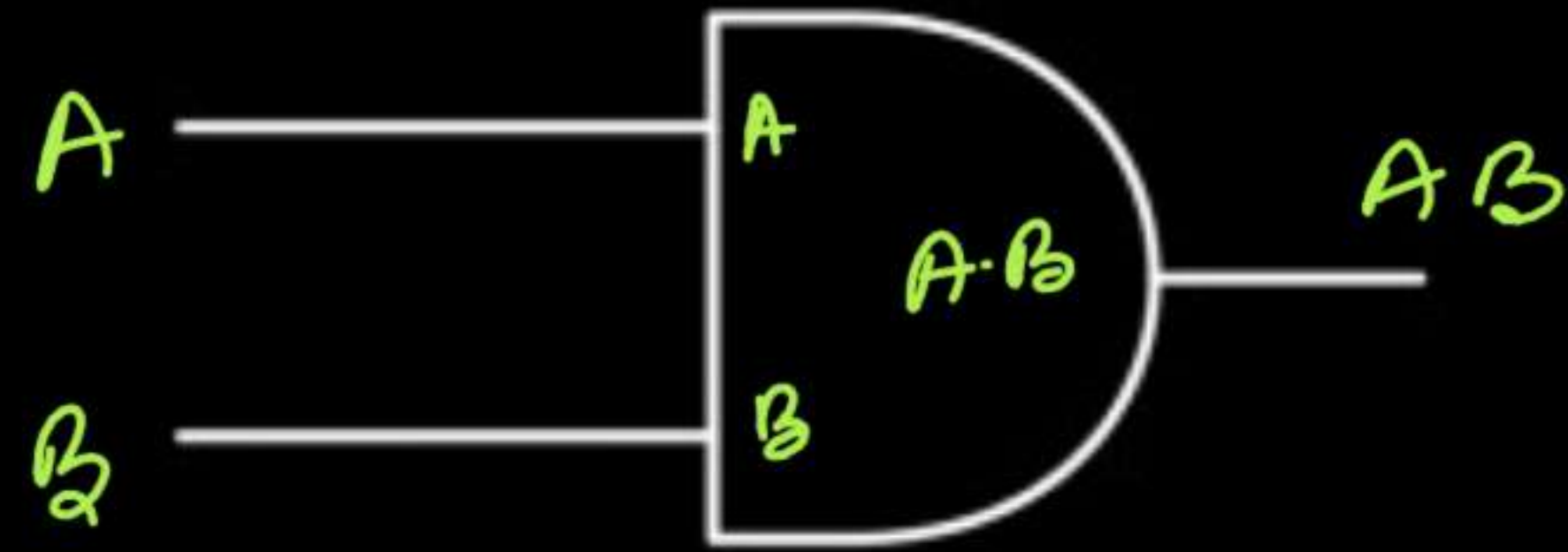





# MULTIPLEXER

## 3. OR GATE

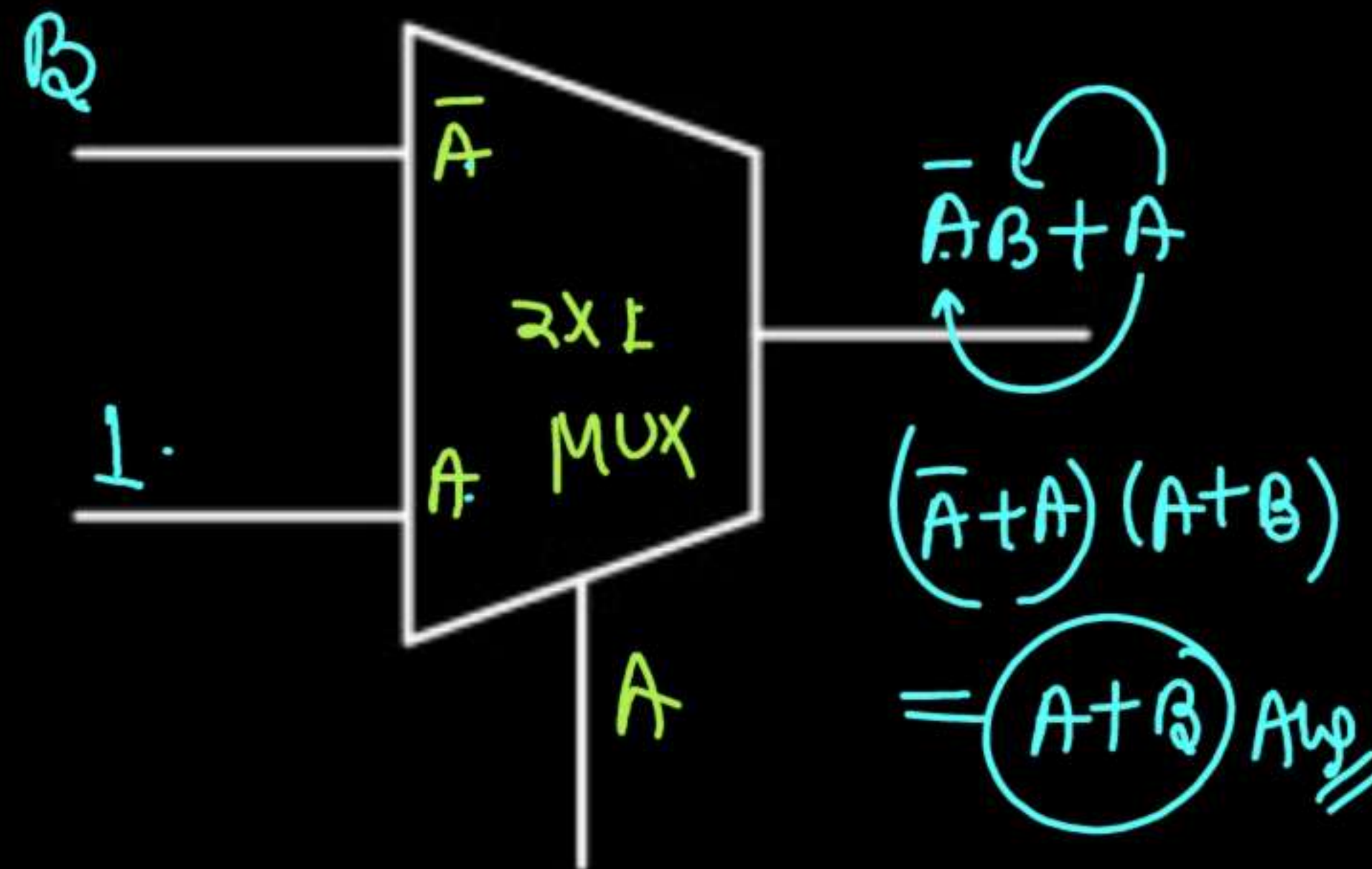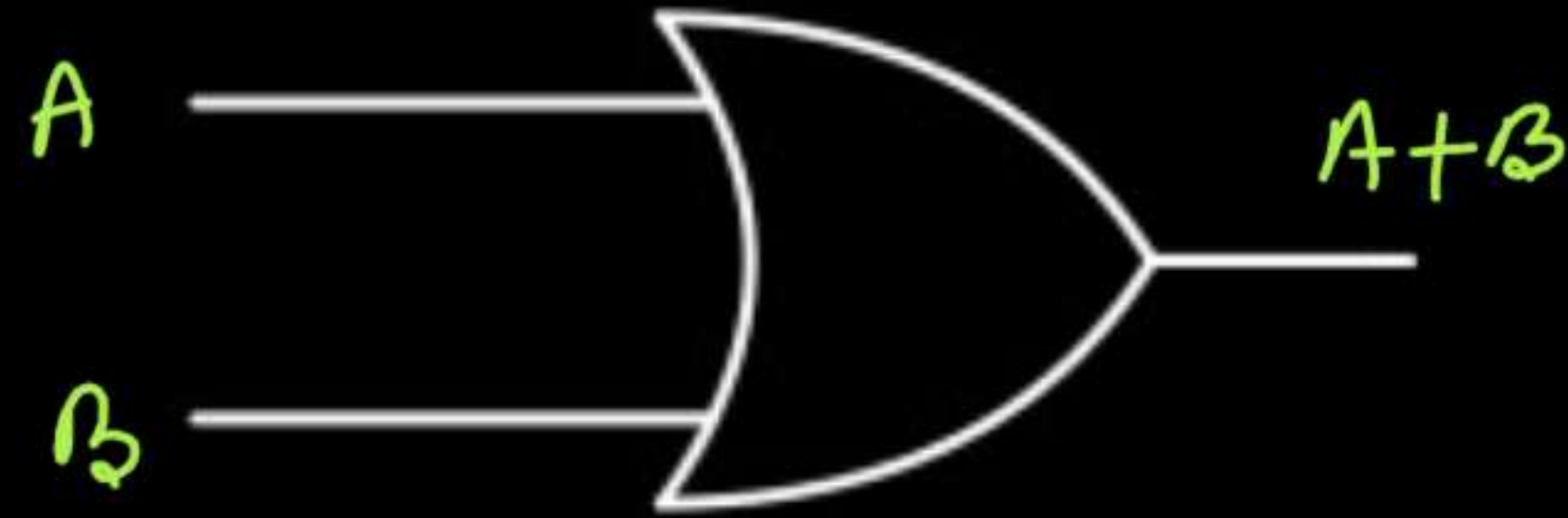



#### 4. NAND GATE

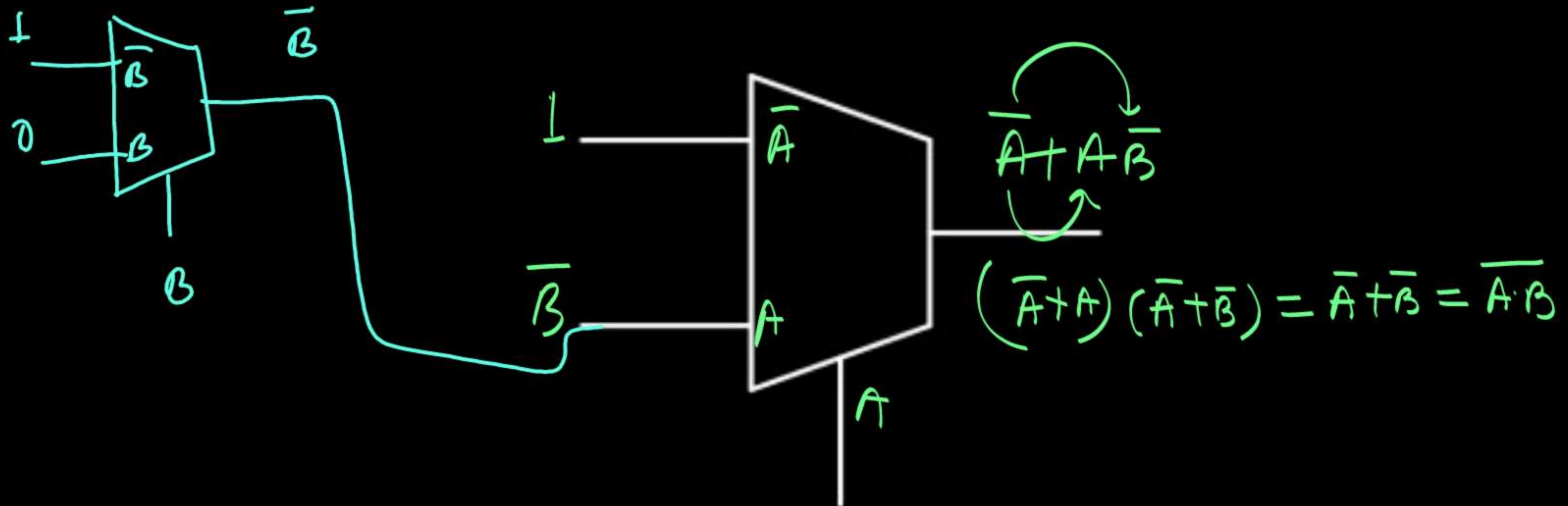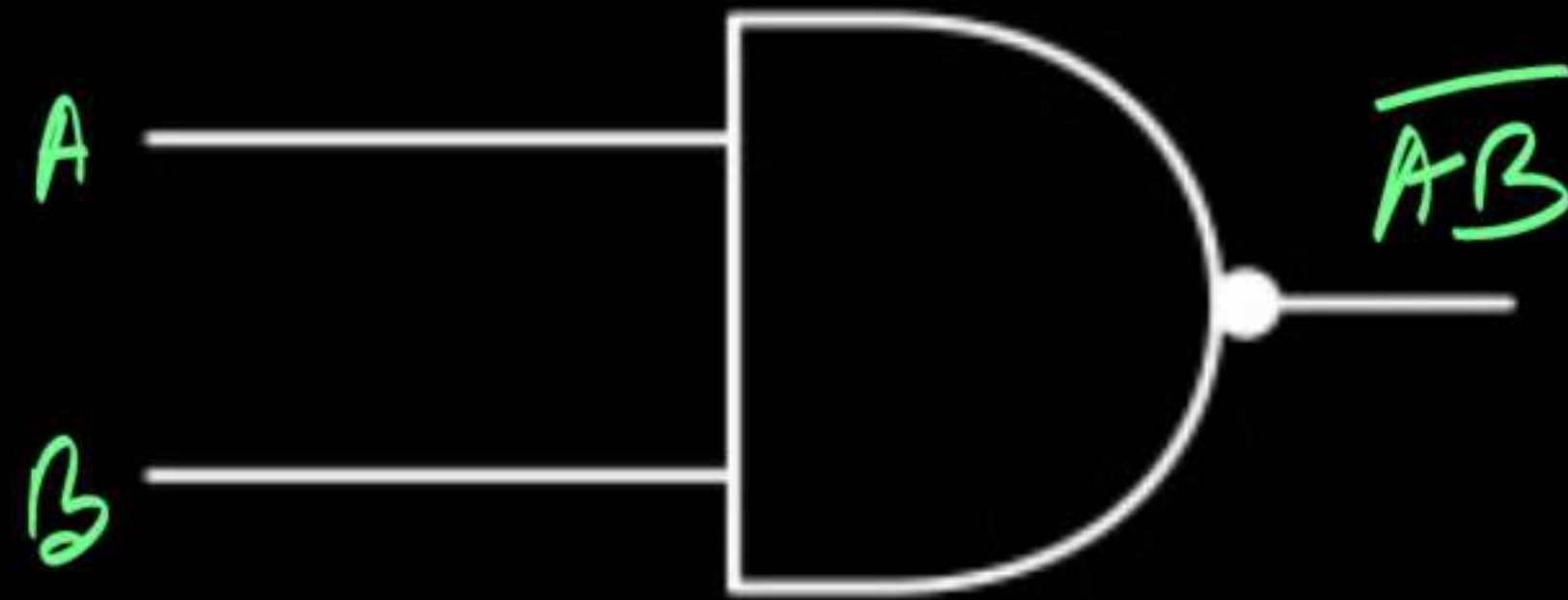

# MULTIPLEXER



## 5. NOR GATE

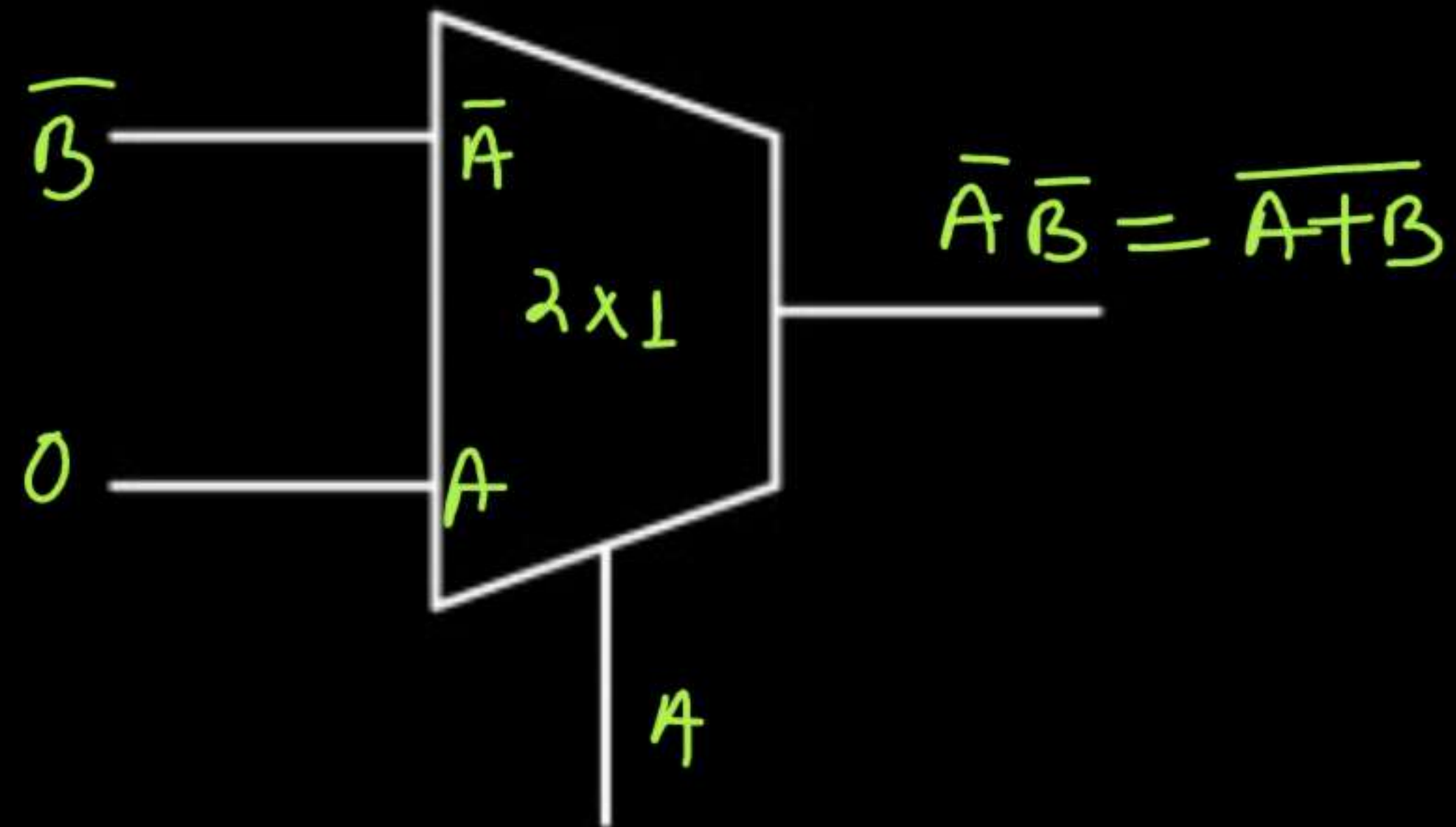
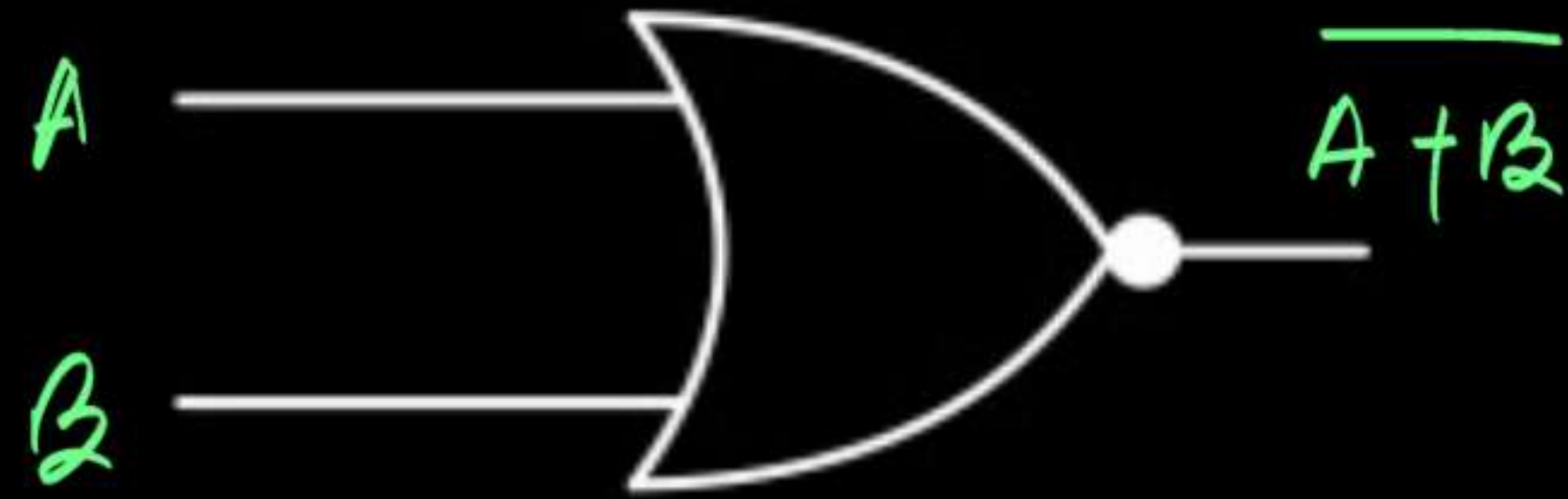




# MULTIPLEXER





## 6. X-OR GATE

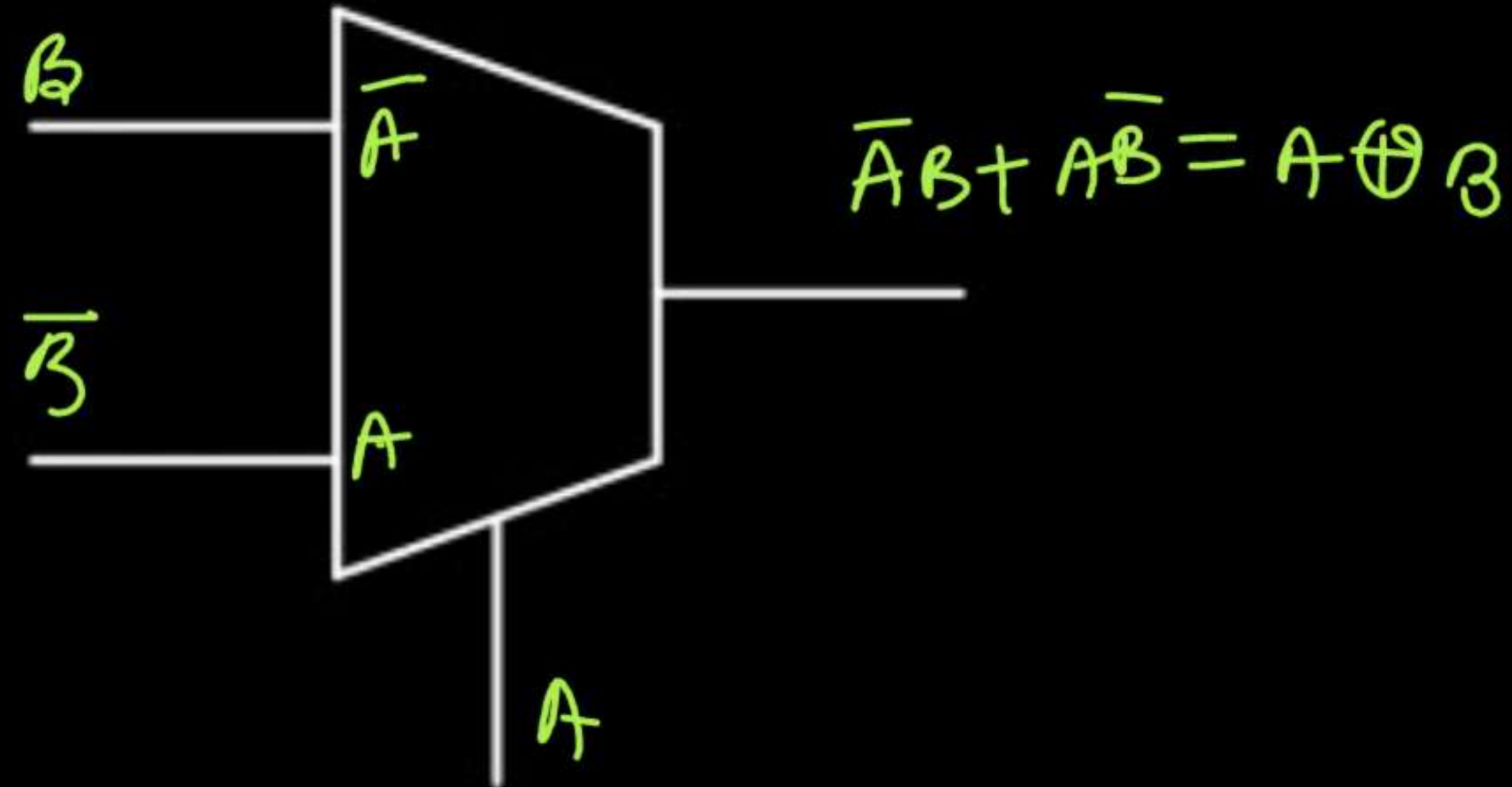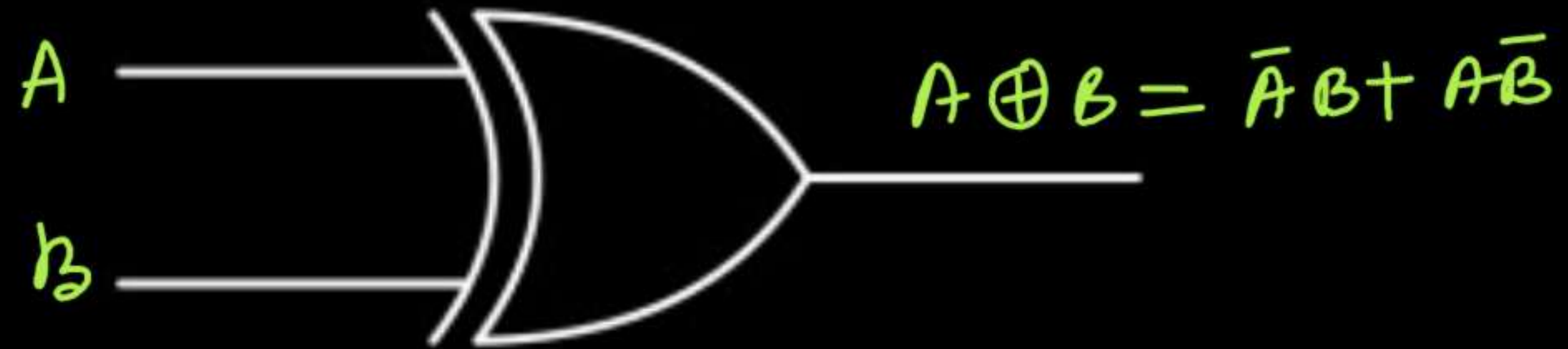

# MULTIPLEXER



## 7. X-NOR GATE

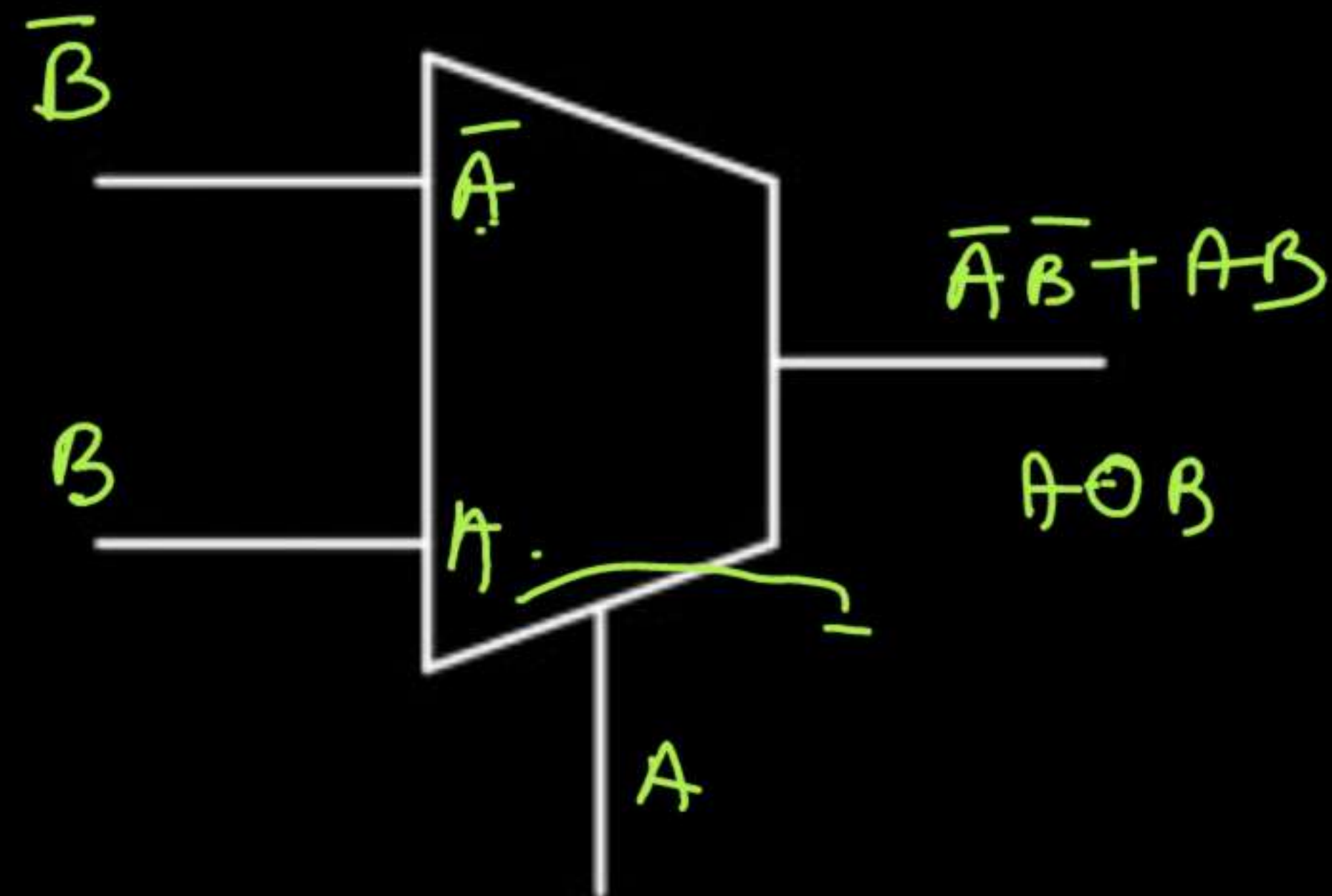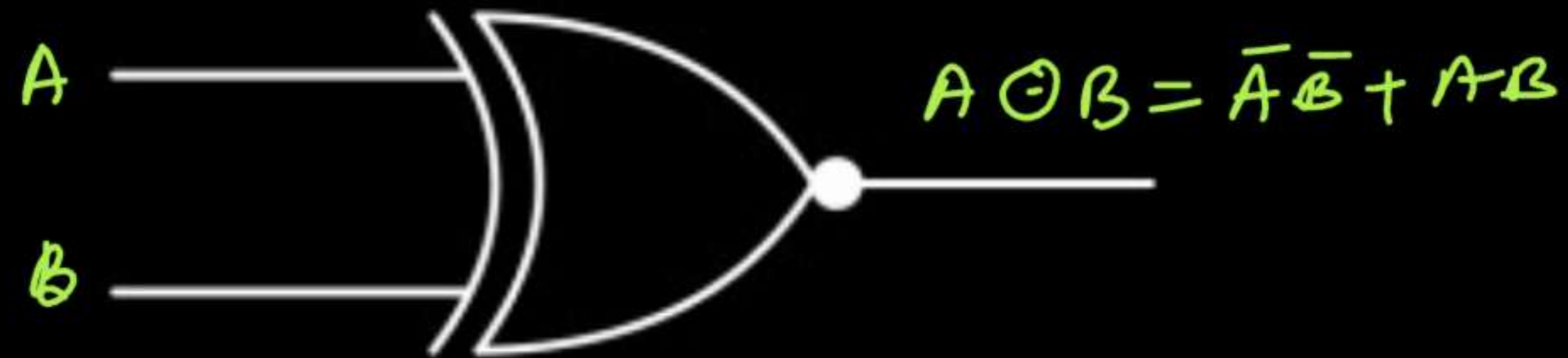

Ex 2  
NOTE :- To Design NOT, AND, OR

└────────→ One 2x1 MUX  
required

To Design NAND, NOR, X-OR, X-NOR

└────────→ Two 2x1 MUX  
required.



Q.

Design all Logic GATE by 4X1 MUX?

**Thank you**

**GW**  
*Soldiers !*

