

CS & IT ENGINEERING

Digital Logic
Logic Gate



DPP 02


Discussion Notes

By- CHANDAN SIR





TOPICS TO BE COVERED



01 Questions


02 Discussion

Q.1

For a 3-input logic circuit shown below, the output Z can be expressed as



 - A. $Q + \bar{R}$
- B. $P\bar{Q} + R$
- C. $\bar{Q} + R$
- D. $P + \bar{Q} + R$



$$\begin{aligned} Z &= \overline{P\bar{Q} \cdot \bar{Q}R} \\ &= \overline{P\bar{Q}} + \overline{\bar{Q}R} \\ &= \bar{P} + Q + Q + \bar{R} \\ &= \bar{P} + Q + \bar{R} \end{aligned}$$

Q.2

The complete set of only those Logic Gates designated as Universal Gates is

- A. NOT, OR and AND Gates
- B. XNOR, NOR and NAND Gates
- C. NOR and NAND Gates
- D. XOR, NOR and NAND Gates

Q.3


In the logic circuit shown in the figure, Y is given by

A. $Y = ABCD$

B. $Y = (A + B)(C + D)$

C. $Y = A + B + C + D$

D. $Y = AB + CD$

 

Q.4

$F = AB + CD + E$ will be implemented with how many minimum number NAND gates?



A.

Three

B.

Four

C.


Five

☒ D.

Six

$$AB + CD = X \quad \text{--- (3)}$$

$$F = X + E \quad \text{--- (3)}$$

 

Q.5

The minimum number of NAND gates required to reduce the expression $((A + B) C) D$ is

A.

6

B.

5

C.

8


D.

4

$$f = [AC + BC] \cdot D$$

$$X = AC + BC \rightarrow (3)$$

$$f = X \cdot D \rightarrow (2)$$

 

Q.6

In a two-input **NAND** gate, if both inputs are shorted, it will behave like a _____ gate.



A.

Buffer

B.


AND

☒ C.

NOT

D.

EX-OR

 

Q.7

For the circuit shown in figure the Boolean expression for the output Y in terms of inputs P, Q, R and S is



- A. $\bar{P} + \bar{Q} + \bar{R} + \bar{S}$
- ☒ B. $P + Q + R + S$
- C. $(\bar{P} + \bar{Q}) + (\bar{R} + \bar{S})$
- D. $(P + Q)(R + S)$



Q.8

A universal logic gate can implement any Boolean function by connecting sufficient number of them appropriately. Three gates are shown:

Which one of the following statements is TRUE ?

A.

Gate 1 is a universal gate.

B.



Gate 2 is a universal gate.


C.

Gate 3 is a universal gate

D.

None of the shown is a universal gate.

  

 

NAND

Q.9

Consider the following gate network:

Which one of the following gates is redundant?

A.

Gate No. 1

B.


Gate No. 2

C.

Gate No. 3

D.

Gate No. 4

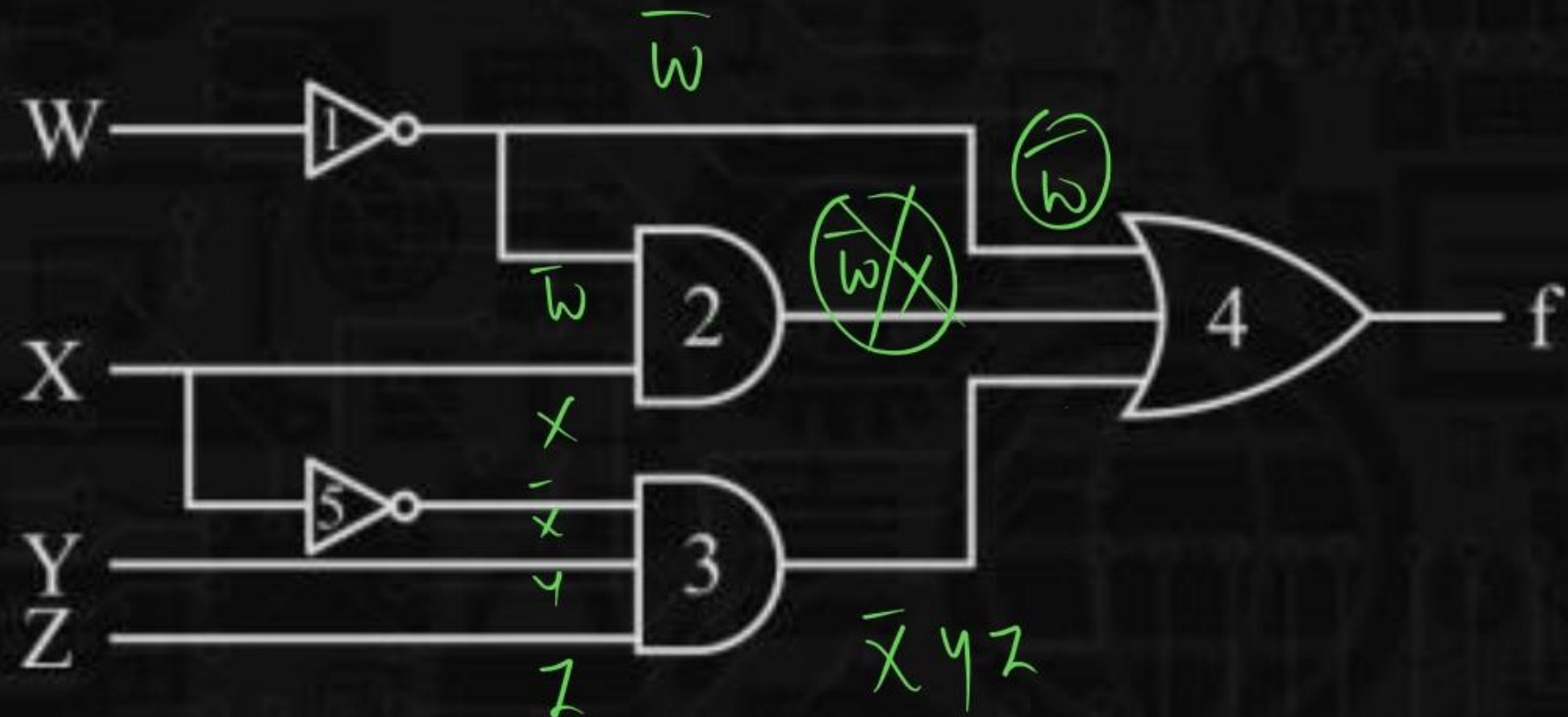

$$\begin{aligned}
 f &= \bar{W} + \bar{W}X + \bar{X}YZ \\
 &= \bar{W}(1+X) + \bar{X}YZ \\
 &= \bar{W} + XYZ
 \end{aligned}$$

Q.10

The minimum of NAND gates required to implement $A + A B C$ is equal to



~~A.~~

~~0~~

B.

1

C.

4

D.

7

$$A + A B C$$
$$A(1 + B C)$$

A



