

# CS & IT ENGINEERING



## DIGITAL LOGIC

### Sequential Circuit



Lecture No. 1



By- CHANDAN SIR






# TOPICS TO BE COVERED

01 LATCHES

02 PRACTICE

04 DISCUSSION


Sequential circuit  $\Rightarrow$

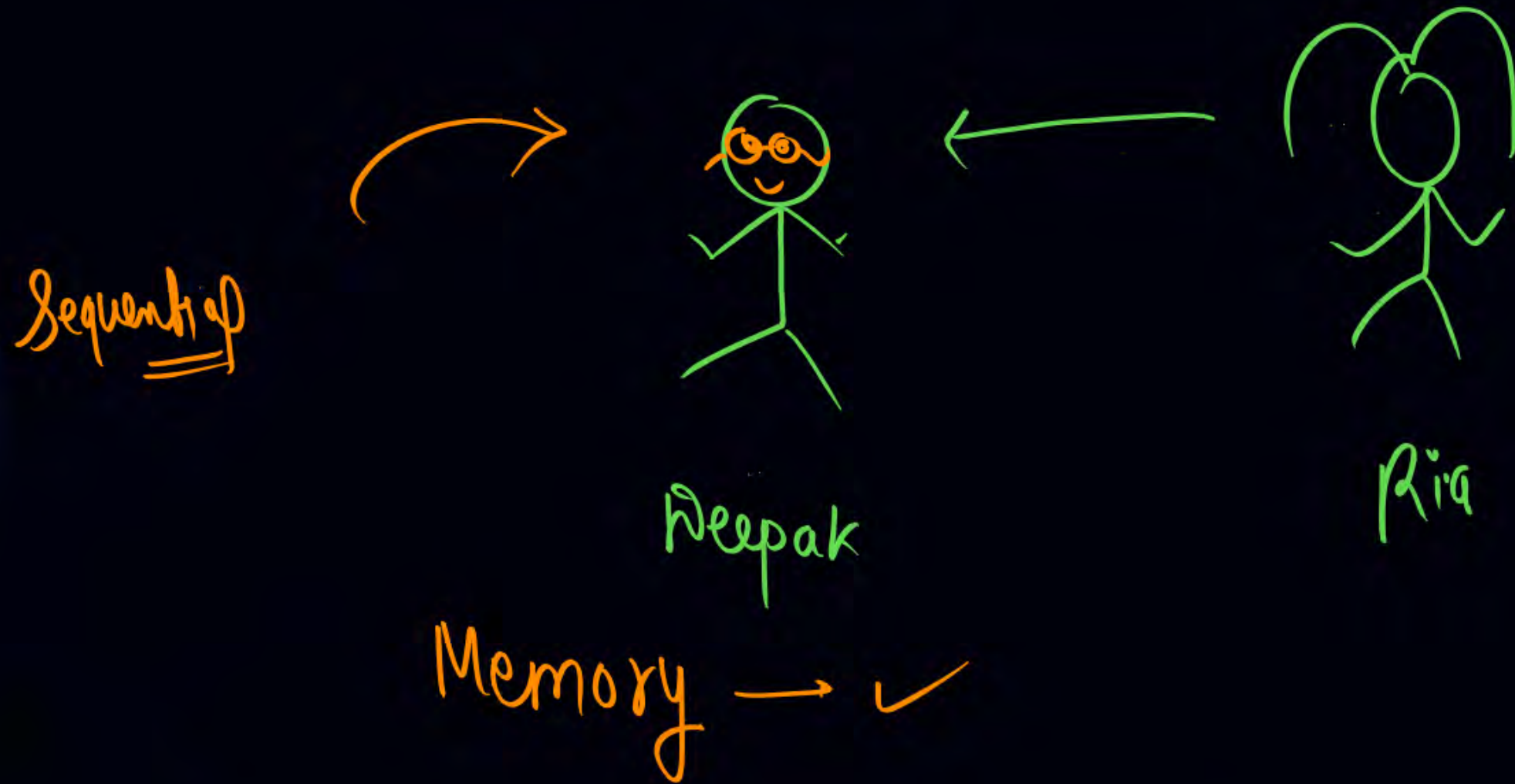

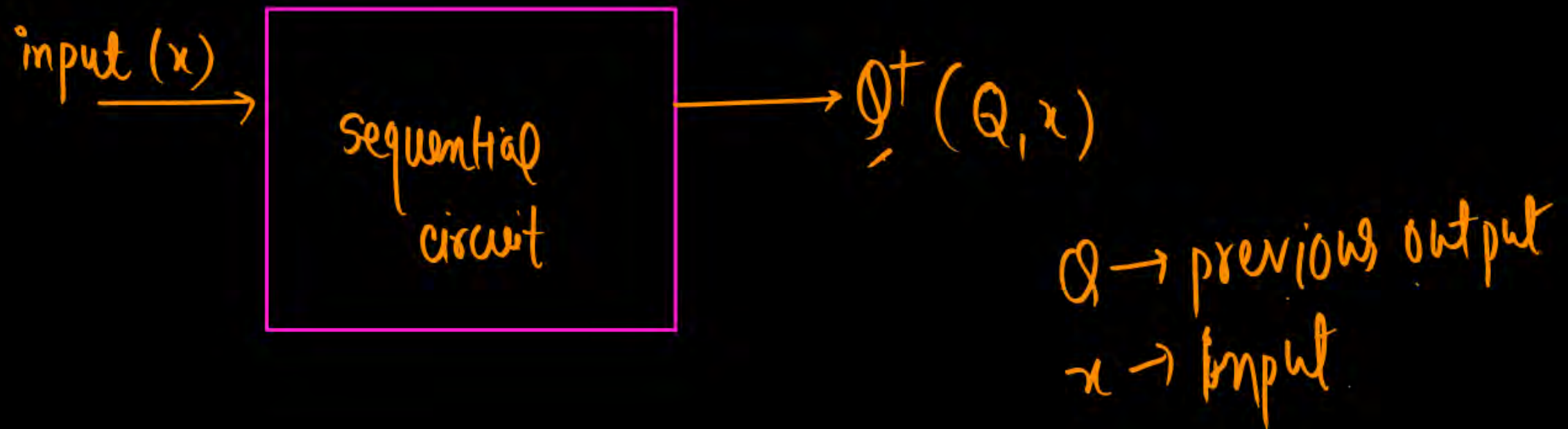
# SEQUENTIAL CIRCUIT




- ✓ A circuit with feedback and memory are called sequential circuit.
- ✓ Output of the sequential circuit depends on previous output as well as present state of input.





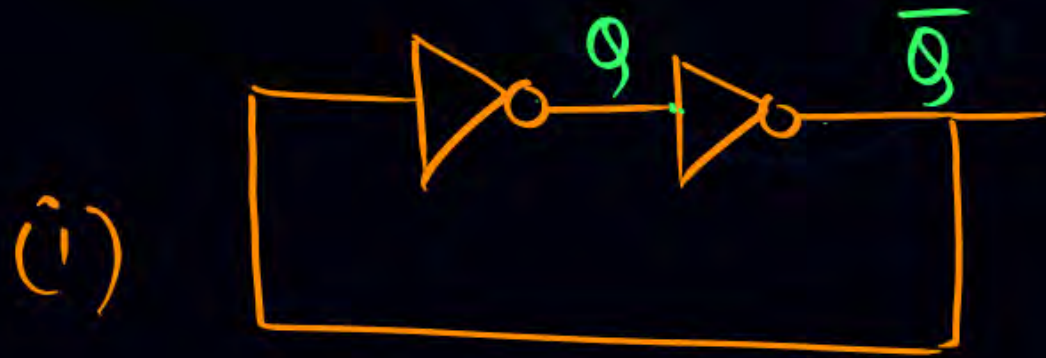

Basic memory element

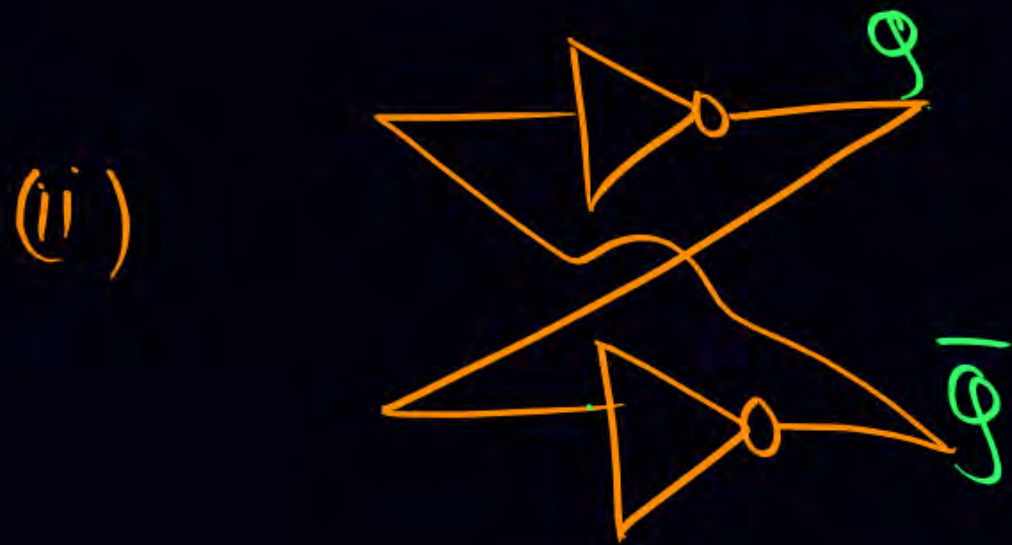

✓ (A)  $i = ii$

(B)  $i \neq ii$

(C) Mujhe nahi ata.

(D) I am interested in Ria only.

## Sequential circuit

① Latches → Basic memory element

② Flip-Flops

③ Registers



④ Counters

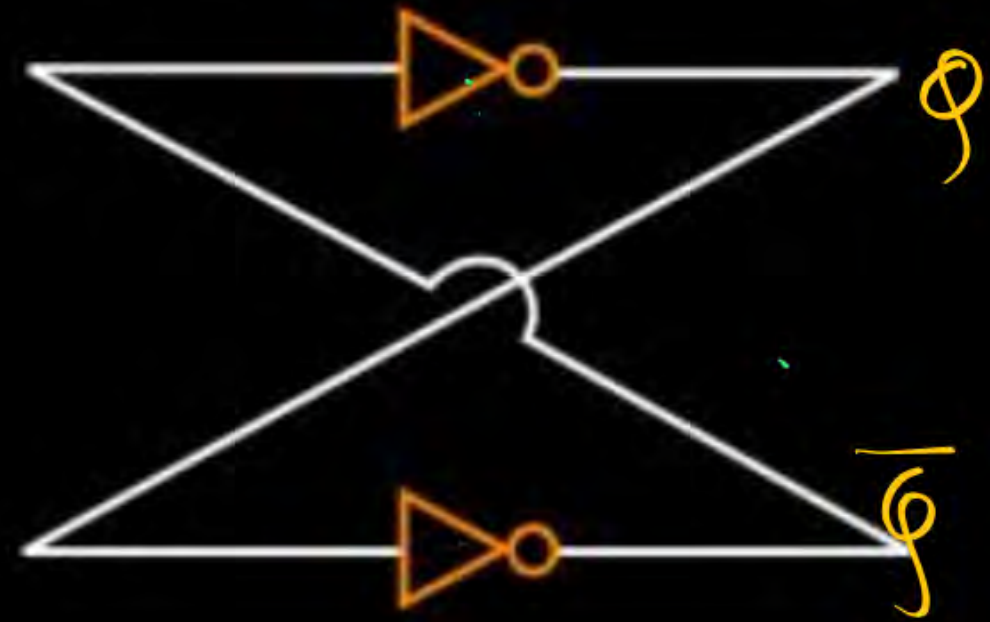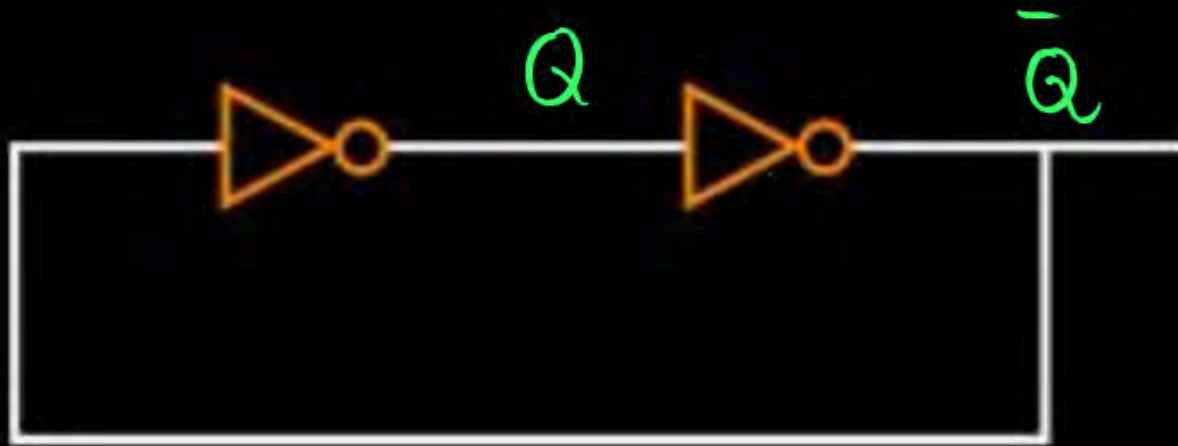
# LATCHES

time/CJSIR




- ✓ Basic memory element
- ✓ Latches are level triggered
- ✓ Latches has two output which is complement of each other



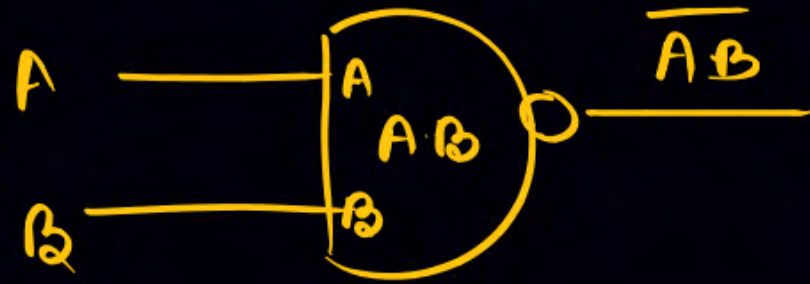



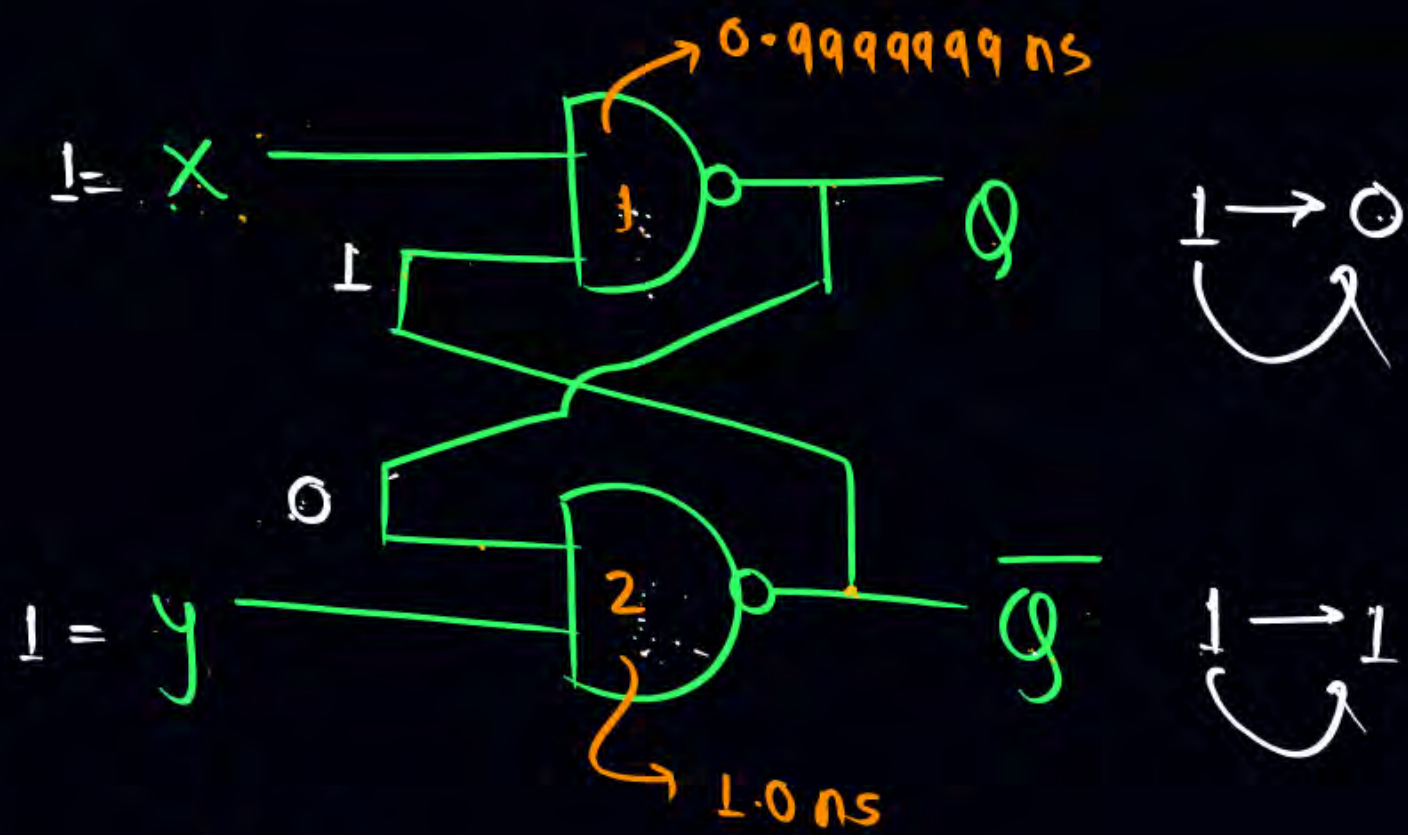

NAND

A	B	$y = \overline{A \cdot B}$
0	0	1
0	1	1
1	0	1
1	1	0

X	Y	Q	$\bar{Q}$	
0	0	1	1	X Invalid
0	1	1	0	
1	0	0	1	
1	1	0	0	→ HOLD

Racing Problem



## LATCHES




**Note :** Whenever  $X=Y=1$  is applied and invalid condition occurs than a NAND having lower propagation delay first change its output and other remain on its previous state are called racing problem or raising problem.




# LATCHES



SR → Set-Reset Latch

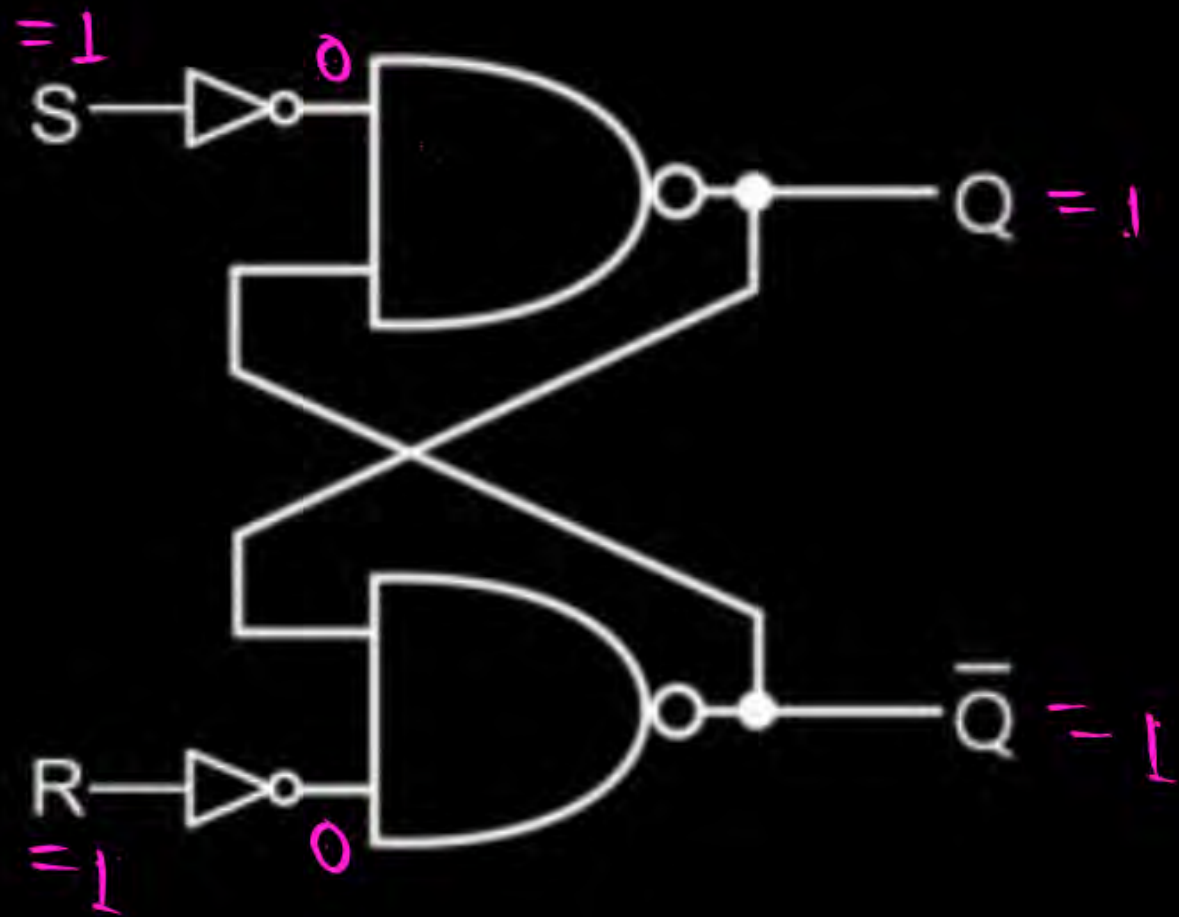


S	R	Q	Q̄	
0	0	Q	Q̄	HOLD
0	1	0	1	RESET
1	0	1	0	SET
1	1	X	X	(Invalid)

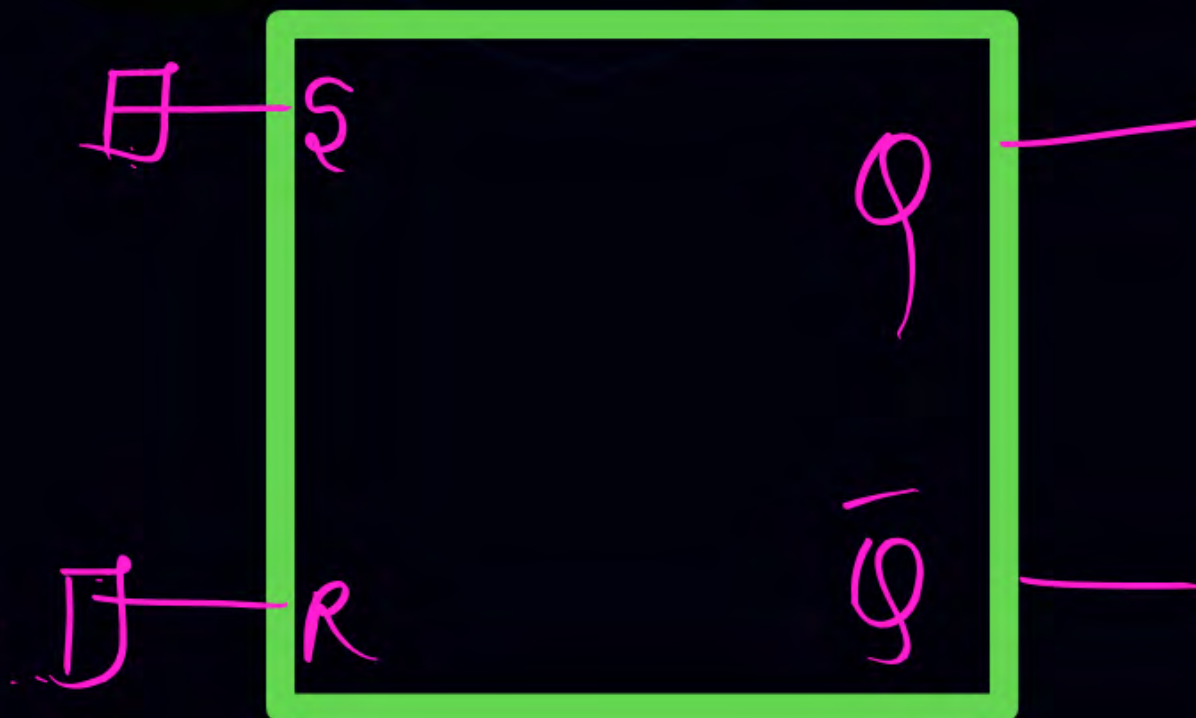

# LATCHES



S-R Latch by using NOR GATE

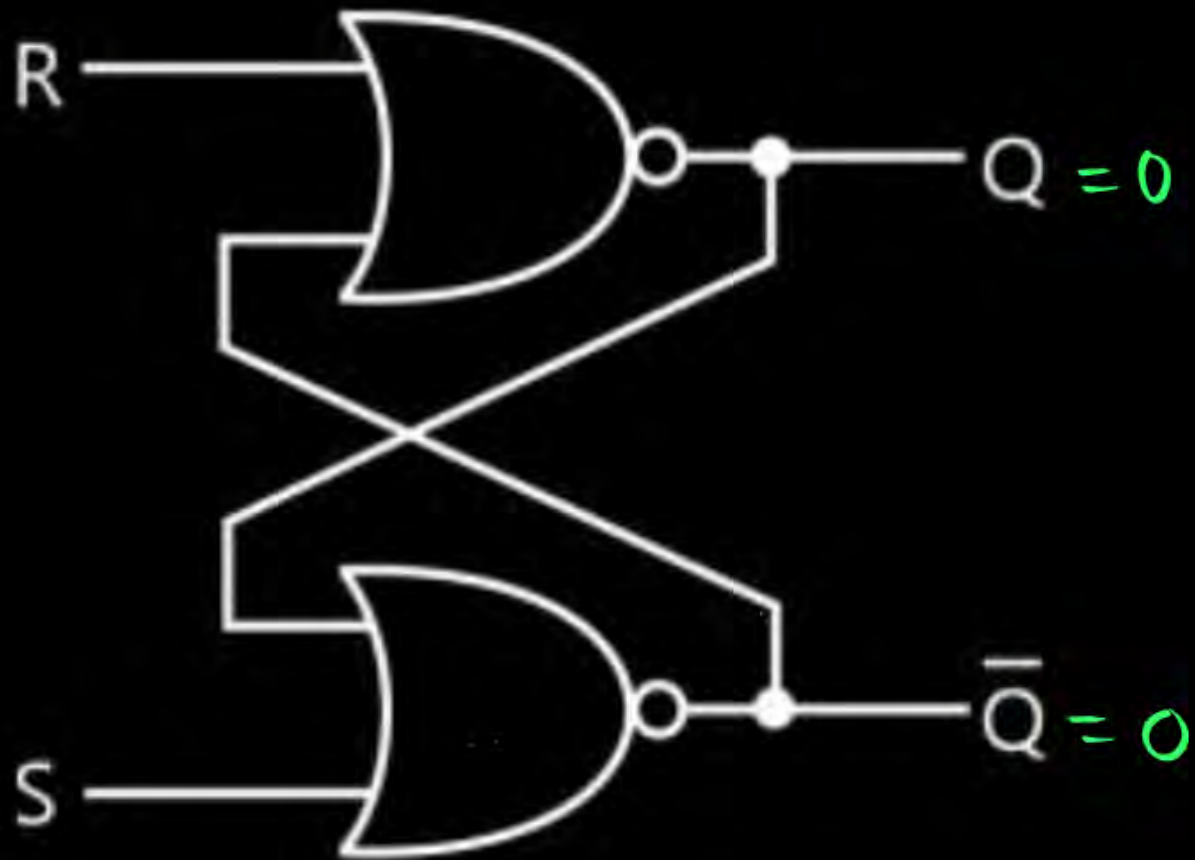

S	R	Q	$\bar{Q}$	
0	0	Q	$\bar{Q}$	(HOLD)
0	1	0	1	(RESET)
1	0	1	0	(SET)
1	1	X	X	(Invalid)

Forbidden  
don't care  
Mai nahi khel raha)


NOR

A	B	$y = \overline{A+B}$
0	0	1
0	1	0
1	0	0
1	1	0



# LATCHES


HW

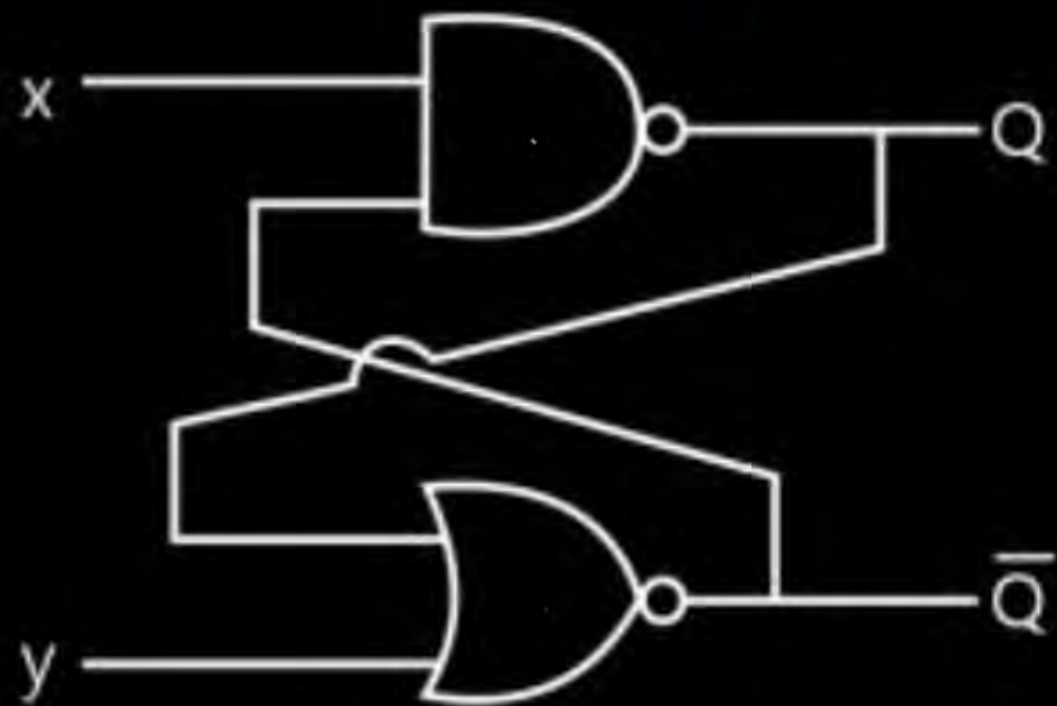

X	Y	Q	$\bar{Q}$
0	0		
0	1		
1	0		
1	1		

# LATCHES


Hw

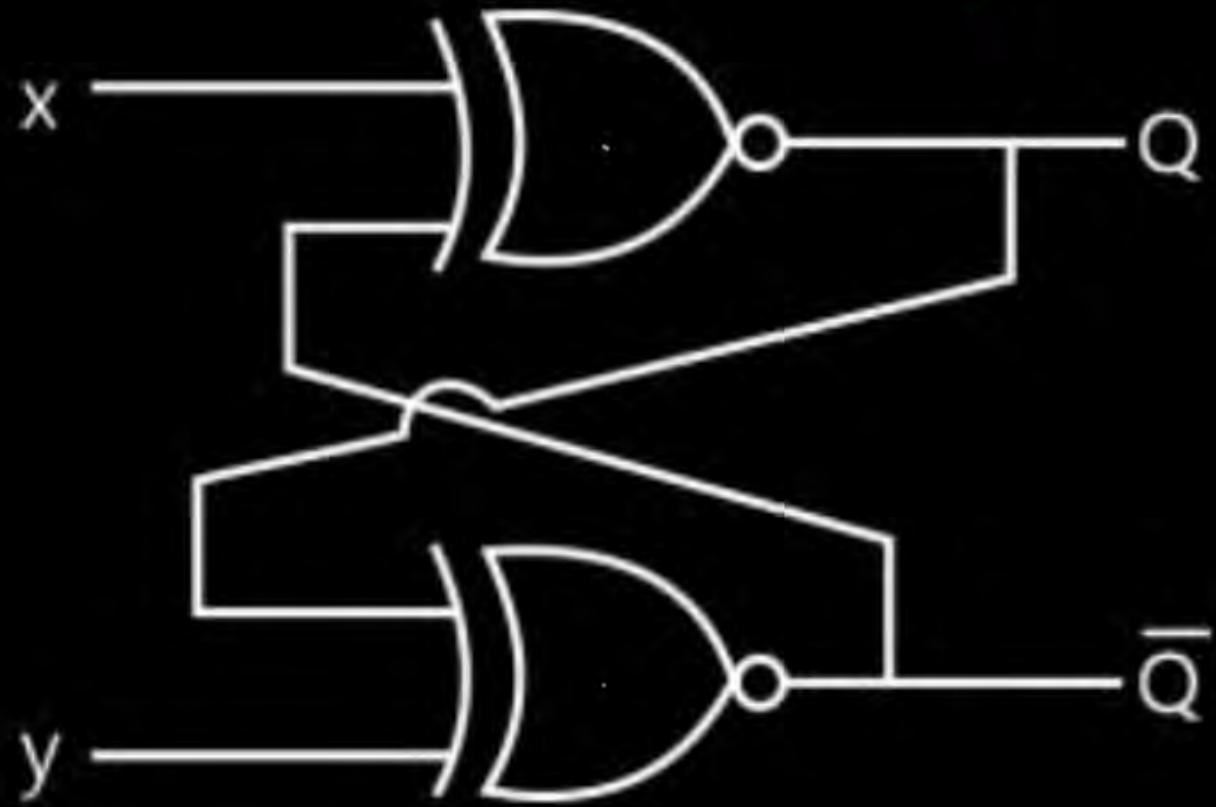

X	Y	Q	$\bar{Q}$
0	0		
0	1		
1	0		
1	1		

# LATCHES

H/W

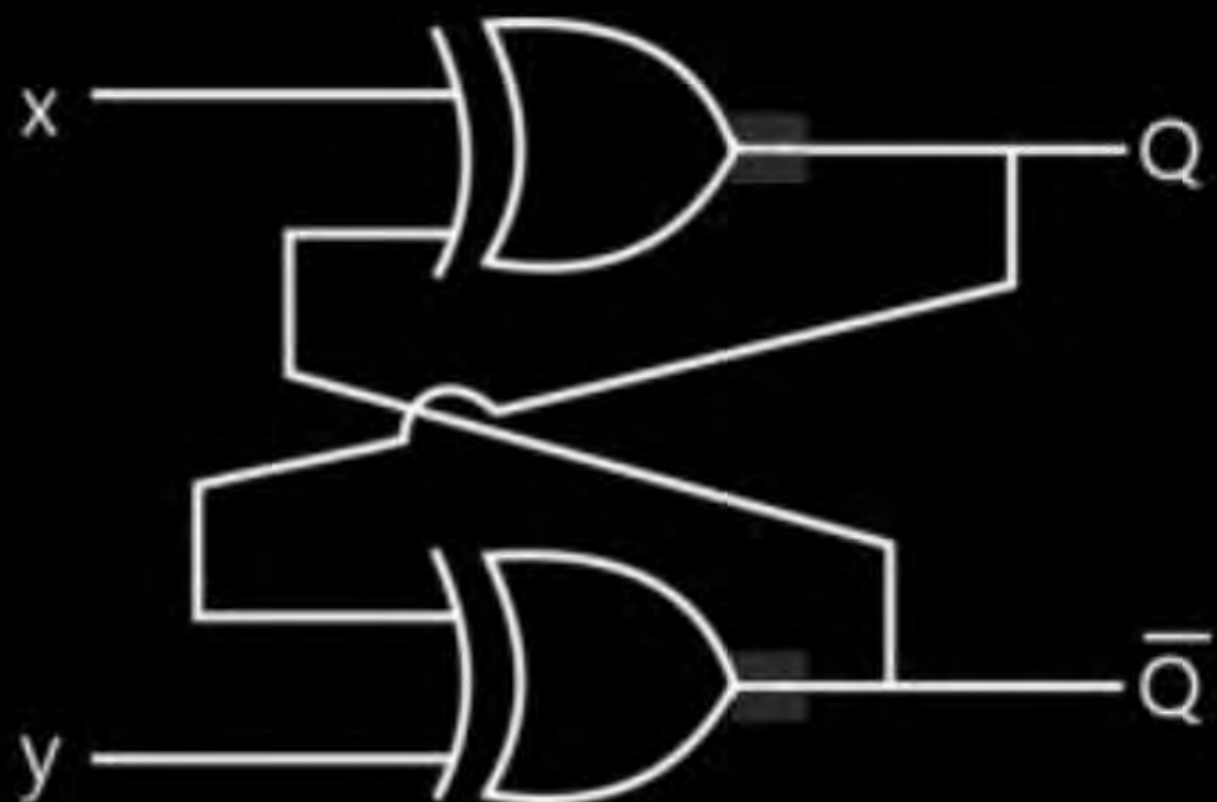


X	Y	Q	$\bar{Q}$
0	0		
0	1		
1	0		
1	1		



# LATCHES

H/W

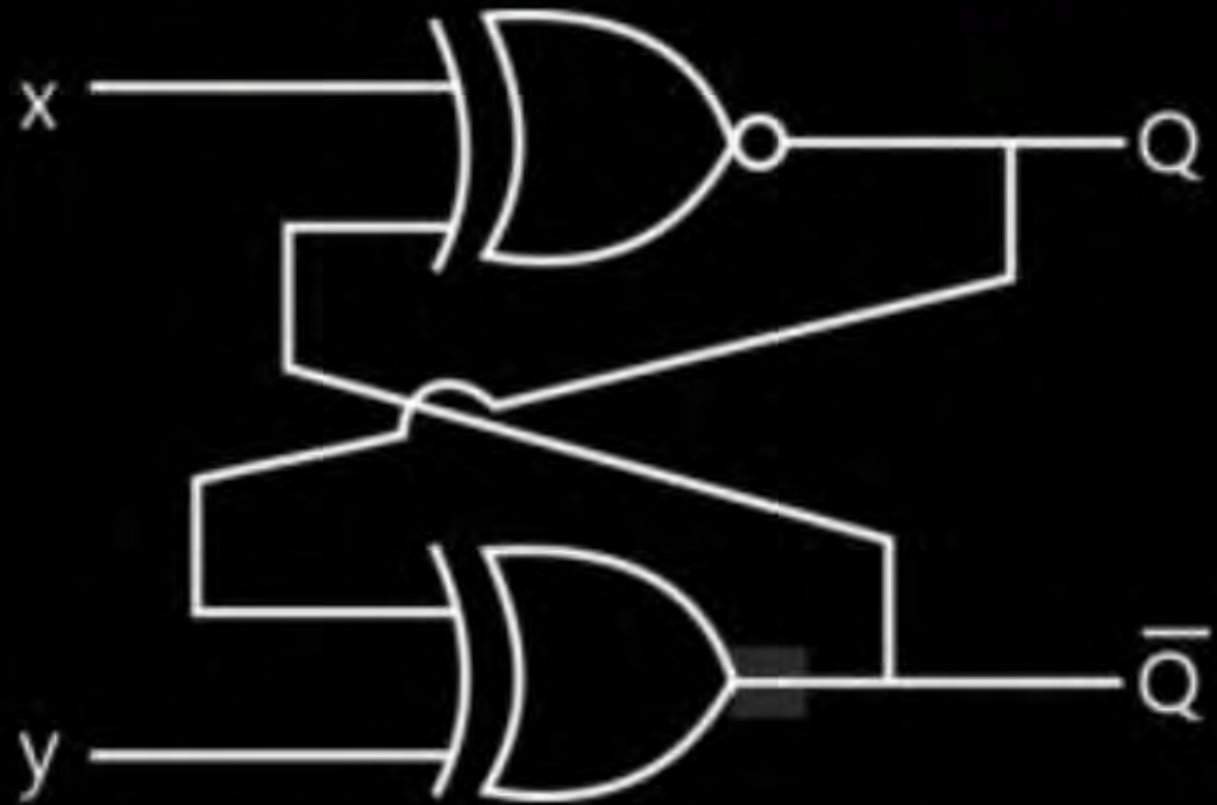

$X$	$Y$	$Q$	$\bar{Q}$
0	0		
0	1		
1	0		
1	1		

Thank you

**GW**  
*Soldiers !*

