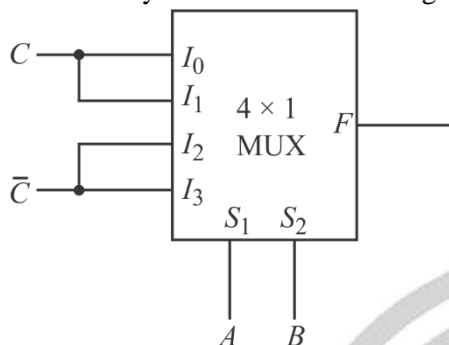


Digital Logic

COMBINATIONAL CIRCUIT

DPP - 02

1. The logic realized by the circuit shown in figure is




- (a) $F = A \odot C$ (b) $F = A \oplus C$
 (c) $F = B \odot C$ (d) $F = B \oplus C$

2. The minimum number of 2-to-1 multiplexers required to realize a 4-to-1 multiplexer is

- (a) 1 (b) 2
 (c) 3 (d) 4

 3. The Boolean function f implemented in the figure using two input multiplexers is




- (a) $\bar{A}\bar{B}C + AB\bar{C}$ (b) $ABC + \bar{A}\bar{B}\bar{C}$
 (c) $\bar{A}BC + \bar{A}\bar{B}\bar{C}$ (d) $\bar{A}\bar{B}C + \bar{A}BC$

4. A designer has multiplexer units of size 2×1 and multiplexer of size 16×1 is to be realized. The number of units of 2×1 MUXs required, will be

- (a) 30 (b) 7
 (c) 15 (d) 11

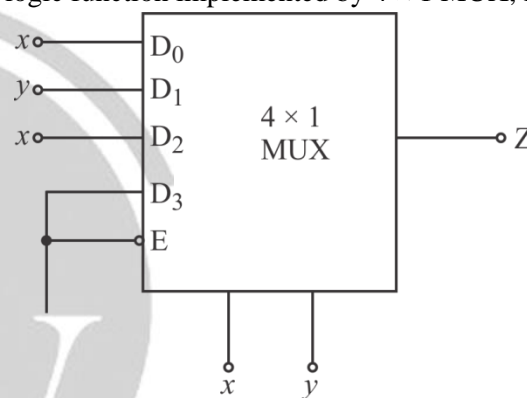5. The logic function implemented by 4×1 MUX, is



- (a) $Z = xy$ (b) $Z = x + y$
 (c) $Z = \overline{x + y}$ (d) $x \oplus y$

6. The minimum number of multiplexers of size 2×1 required to implement a 2-input XNOR gate and 2-input AND gate, are

- (a) 1 and 1 (b) 2 and 1
 (c) 2 and 2 (d) 3 and 1

Answer Key

1. (b)
2. (c)
3. (a)

4. (c)
5. (d)
6. (b)



Hints and solutions


1. $F = \bar{A}\bar{B}C + \bar{A}BC + A\bar{B}\bar{C} + ABC$

$$F = \bar{A}C(B + \bar{B}) + A\bar{C}(B + \bar{B})$$

$$F = \bar{A}C + A\bar{C}$$

$$F = A \oplus C$$

2.

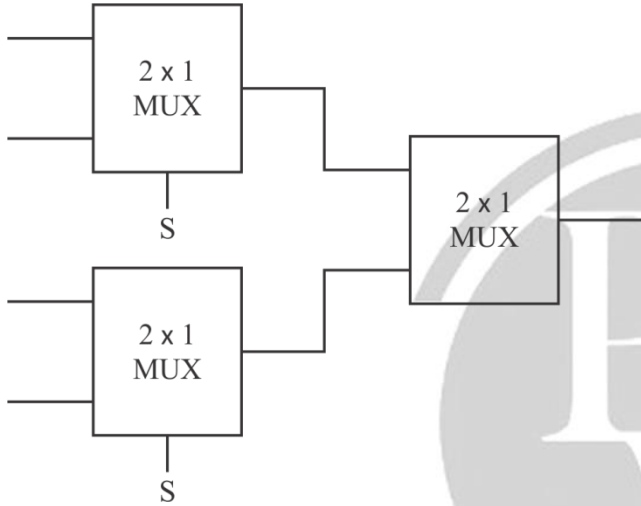

3. $E = \bar{B}C + B\bar{C}$

$$f = AE$$

$$f = A(\bar{B}C + B\bar{C})$$

$$f = A\bar{B}C + AB\bar{C}$$

4. $\frac{16}{2} = 8$

$$\frac{8}{2} = 4$$

$$\frac{4}{2} = 2$$

$$\frac{2}{2} = 1$$

$$\frac{15}{1}$$

Total 15 2×1 MUX required to implement 16×1 MUX.


5. $z = \bar{x}yx + \bar{x}yy + x\bar{y}x + xy \cdot 0$

$$z = \bar{x}y + x\bar{y}x$$


$$z = \bar{x}y + x\bar{y}$$

$$z = x \oplus y$$

6. X-NOR gate implementation

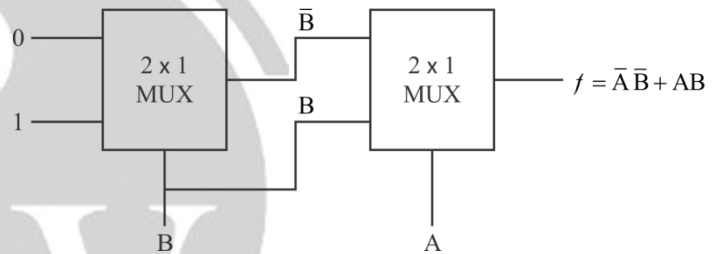

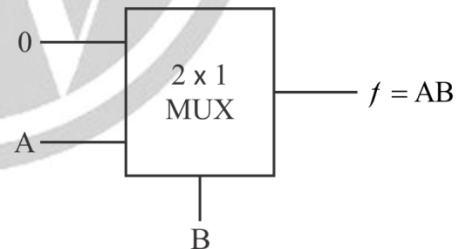Two 2×1 MUX required to implement X-NOR gate.



One 2×1 MUX required to implement AND gate.



Any issue with DPP, please report by clicking here:- <https://forms.gle/t2SzQVvQcs638c4r5>

For more questions, kindly visit the library section: Link for web: <https://smart.link/sdfez8ejd80if>



PW Mobile APP: <https://smart.link/7wwosivoicgd4>