

CS & IT ENGINEERING

DIGITAL LOGIC

Combinational Circuit



Lecture No. 6



By- CHANDAN SIR



TOPICS TO BE COVERED

01 DMux


02 Encoder

03 questons


05 Discussion

DE-MUX \Rightarrow

\rightarrow DE-MUX is called AND Logic

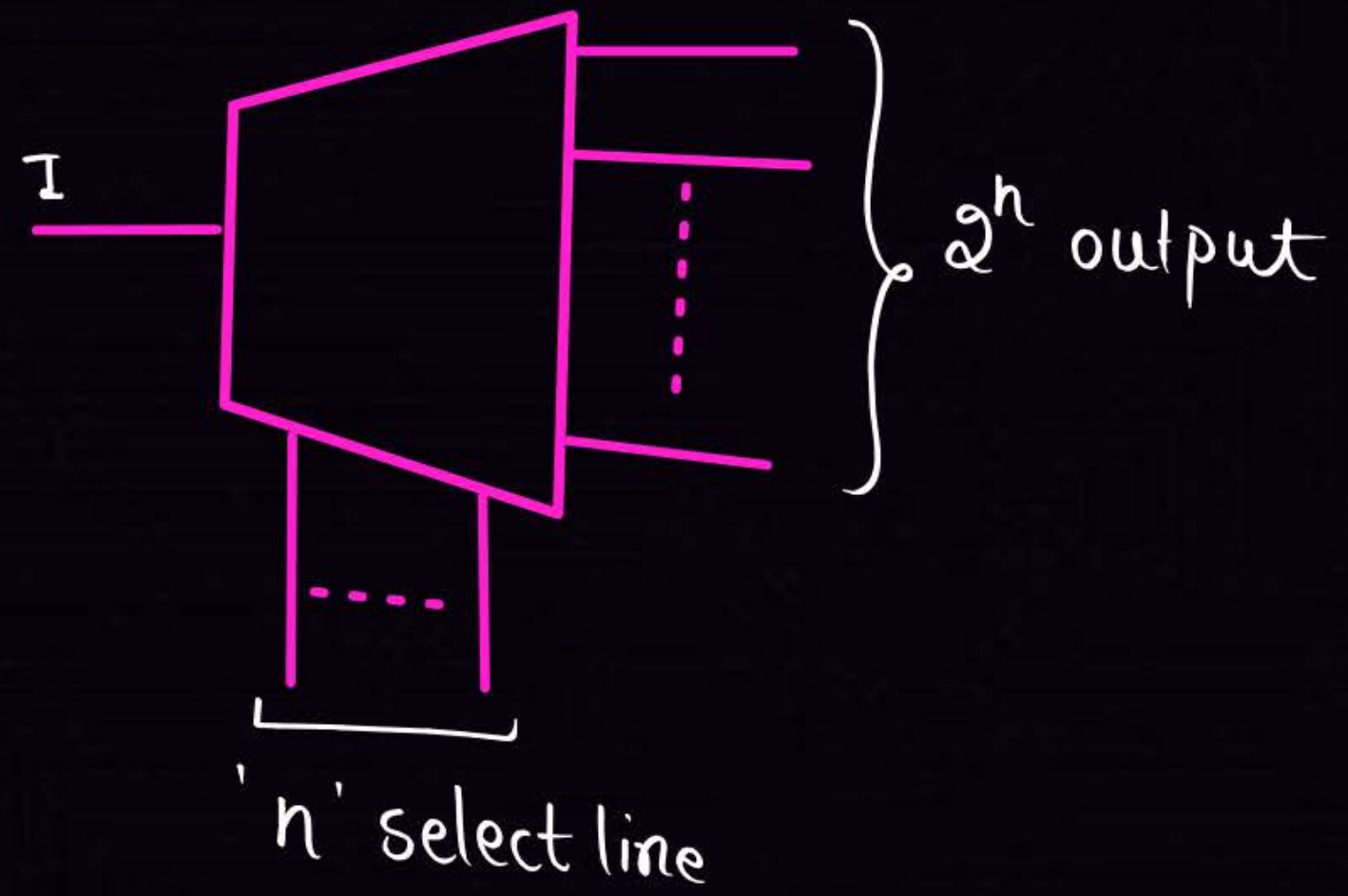

Q. Design 1x2 DE-MUX?

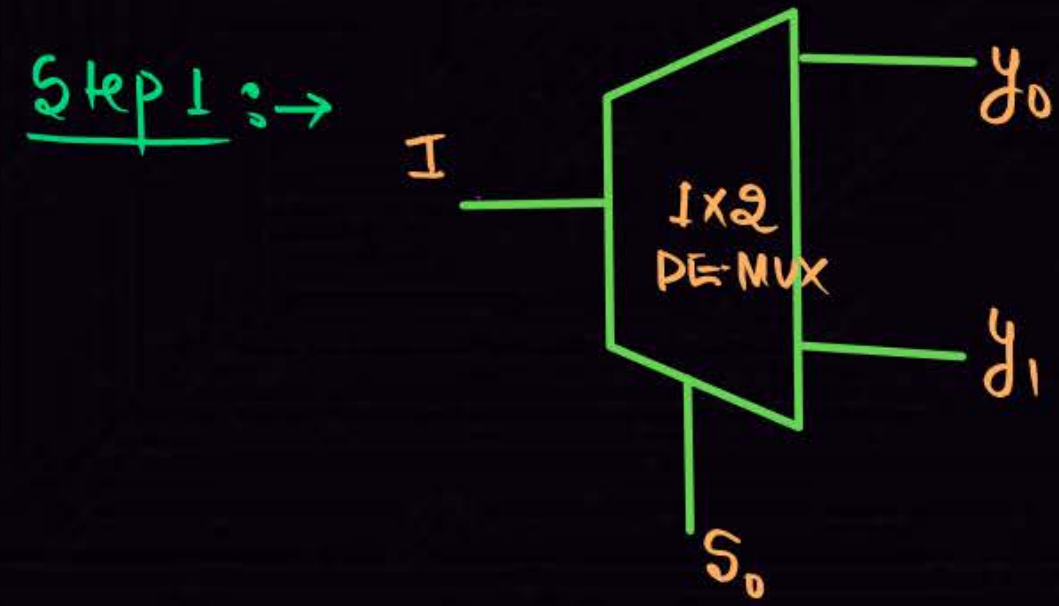

Step 2:-

S_0	y_0	y_1
0	1	0
1	0	1


Step 3:-

$$y_0 = \overline{S_0} I$$

$$y_1 = S_0 I$$


Step 4:-

Step 5:-

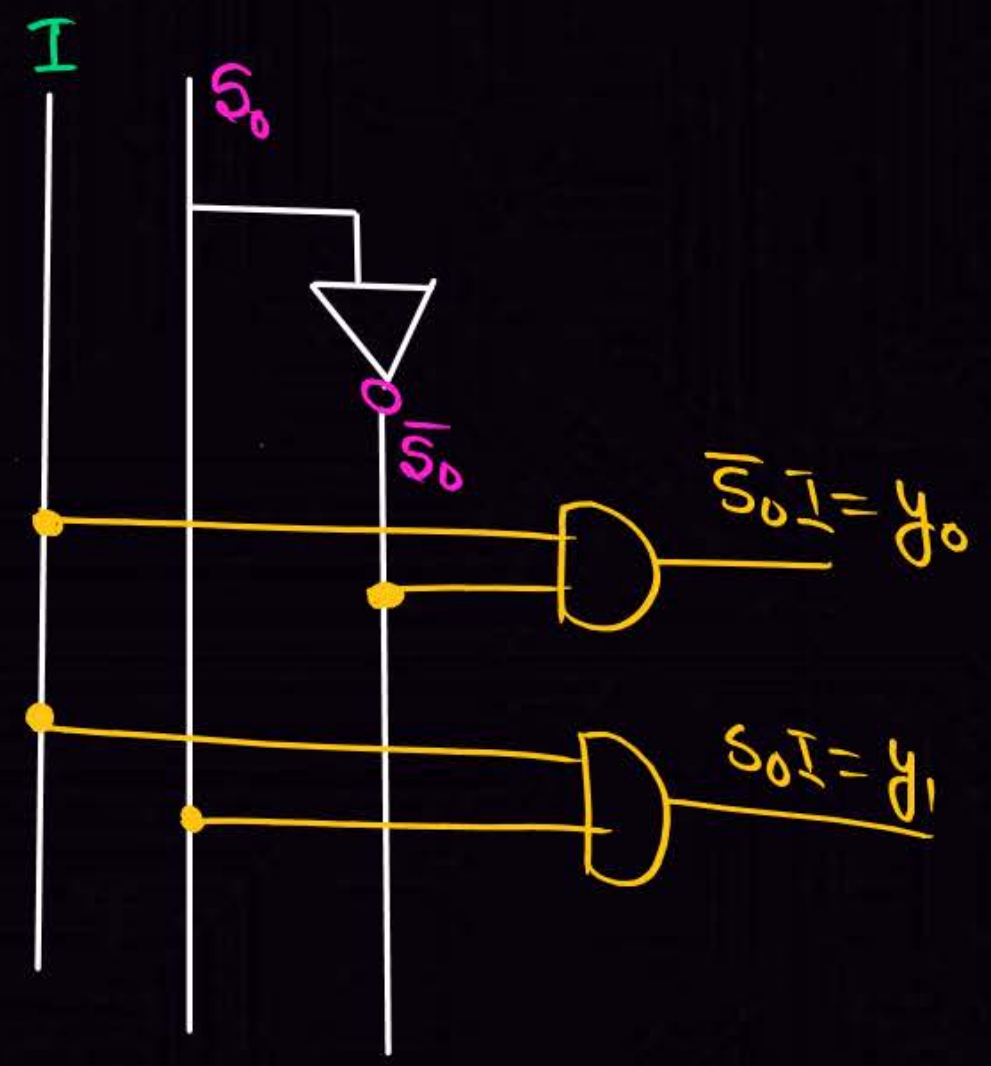

Q Design a 1x4 DEMUX?

Step 1.

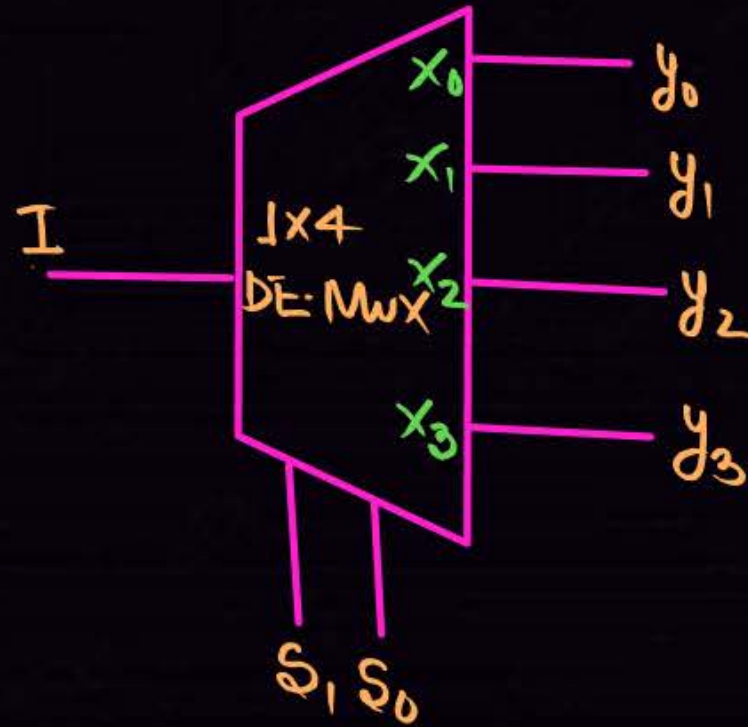

Step 2:

S_1	S_0	y_0	y_1	y_2	y_3
0	0	I	0	0	0
0	1	0	I	0	0
1	0	0	0	I	0
1	1	0	0	0	I

Step 3:-

$$y_0 = \bar{S}_1 \bar{S}_0 I$$

$$y_1 = \bar{S}_1 S_0 I$$



$$y_2 = S_1 \bar{S}_0 I$$

$$y_3 = S_1 S_0 I$$

Step 4:

Step 5:

$$y_0 = \bar{s}_1 \bar{s}_0 I$$

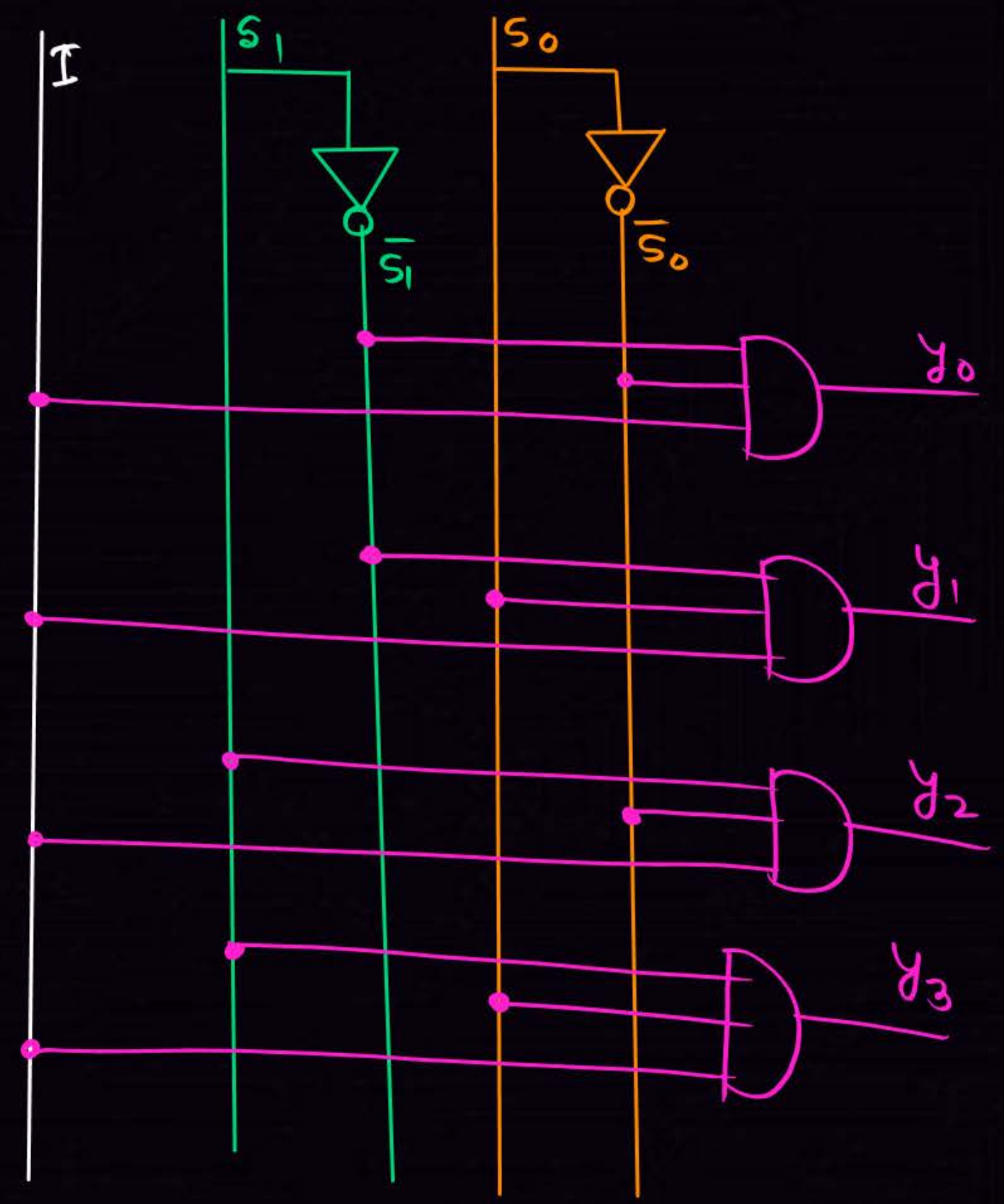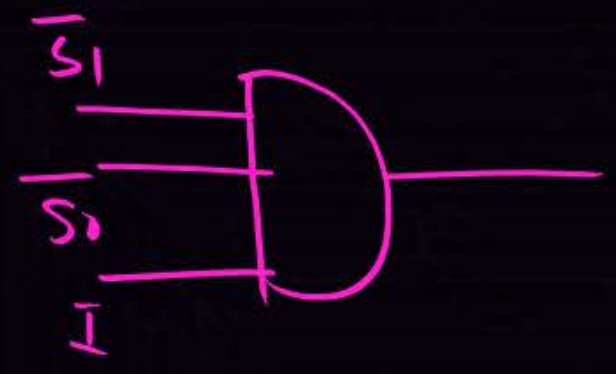


✓ Q₂ Design a 1X8 DE-MUX

✓ Q₃ Design a 1X16 DE-MUX.


ENCODER

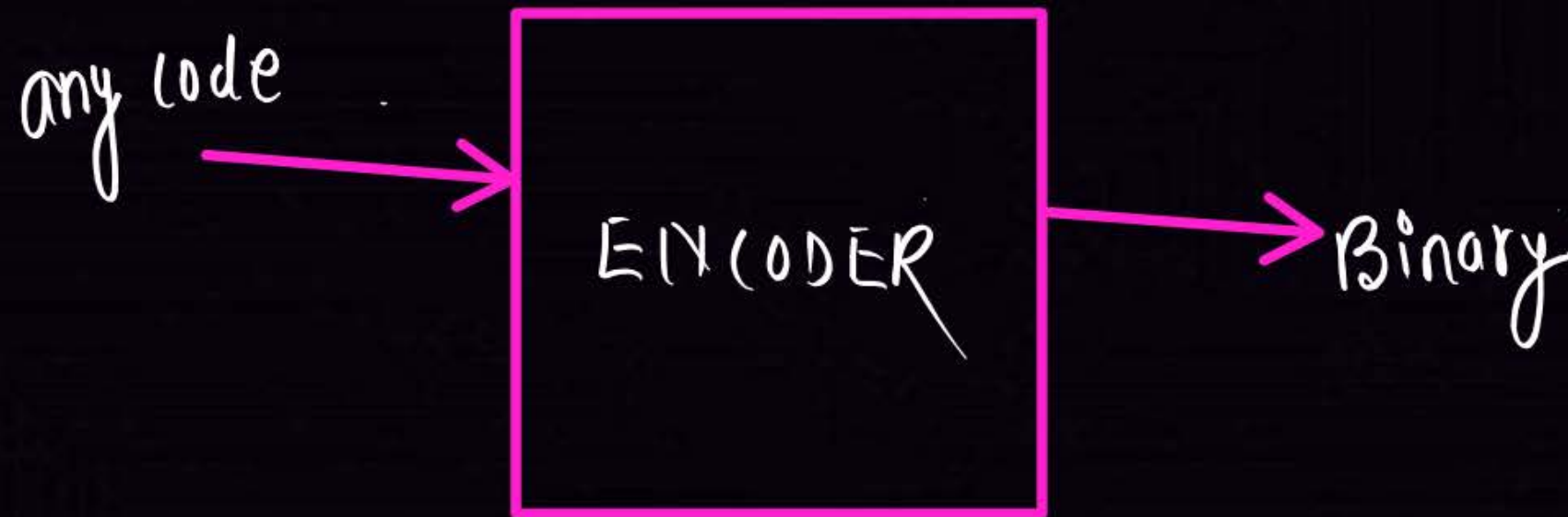↳ A circuit which is use to convert any code into Binary are called Encoder.



- ✓ 1) 4x2 Encoder (Quad to Binary)
- ✓ 2) 8x3 Encoder (Octa to Binary)
- ✓ 3) 16x4 Encoder (Hexa to Binary)

Q Design a 4x2 Encoder

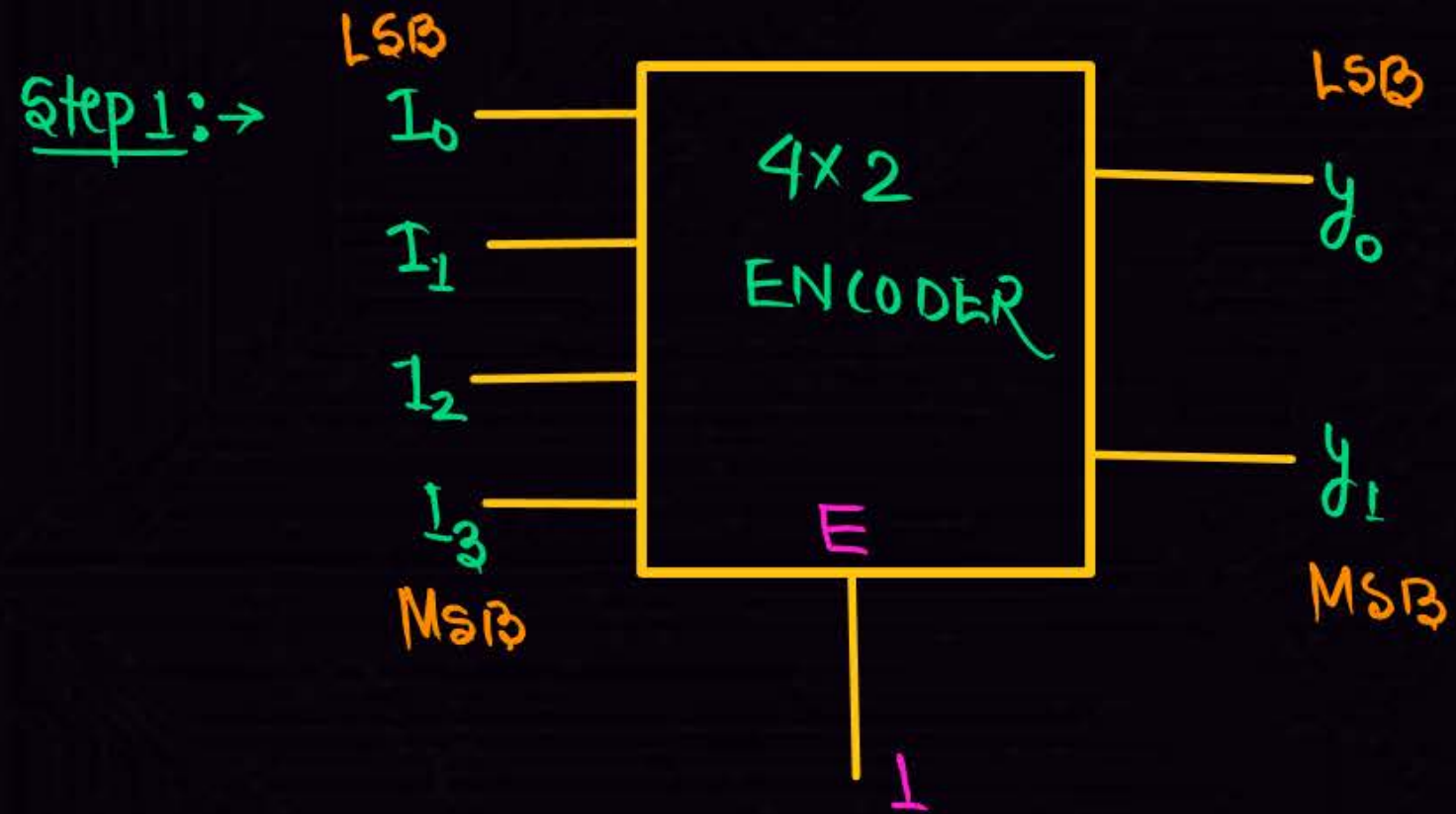

Step 2:-

I_3	I_2	I_1	I_0	y_1	y_0
0	0	0	1	0	0
0	0	1	0	0	1
0	1	0	0	1	0
1	0	0	0	1	1


Step 3:

$$y_0 = I_1 + I_3$$


$$y_1 = I_2 + I_3$$

Step 4:

Step 5:

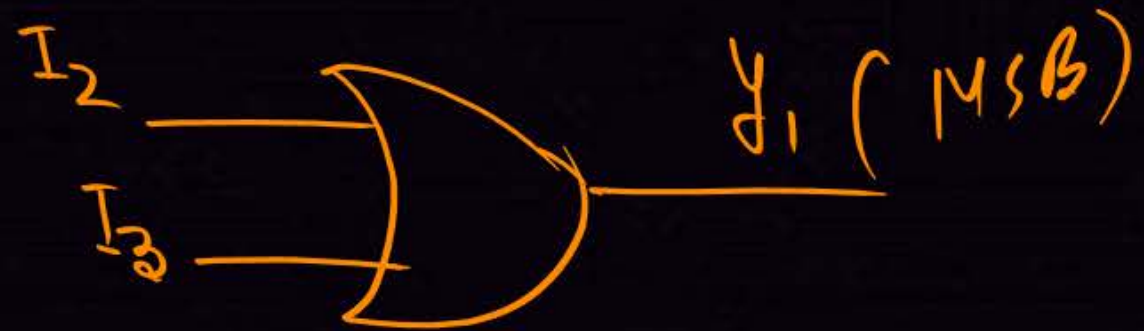

Q Design a 8×3 Encoder?

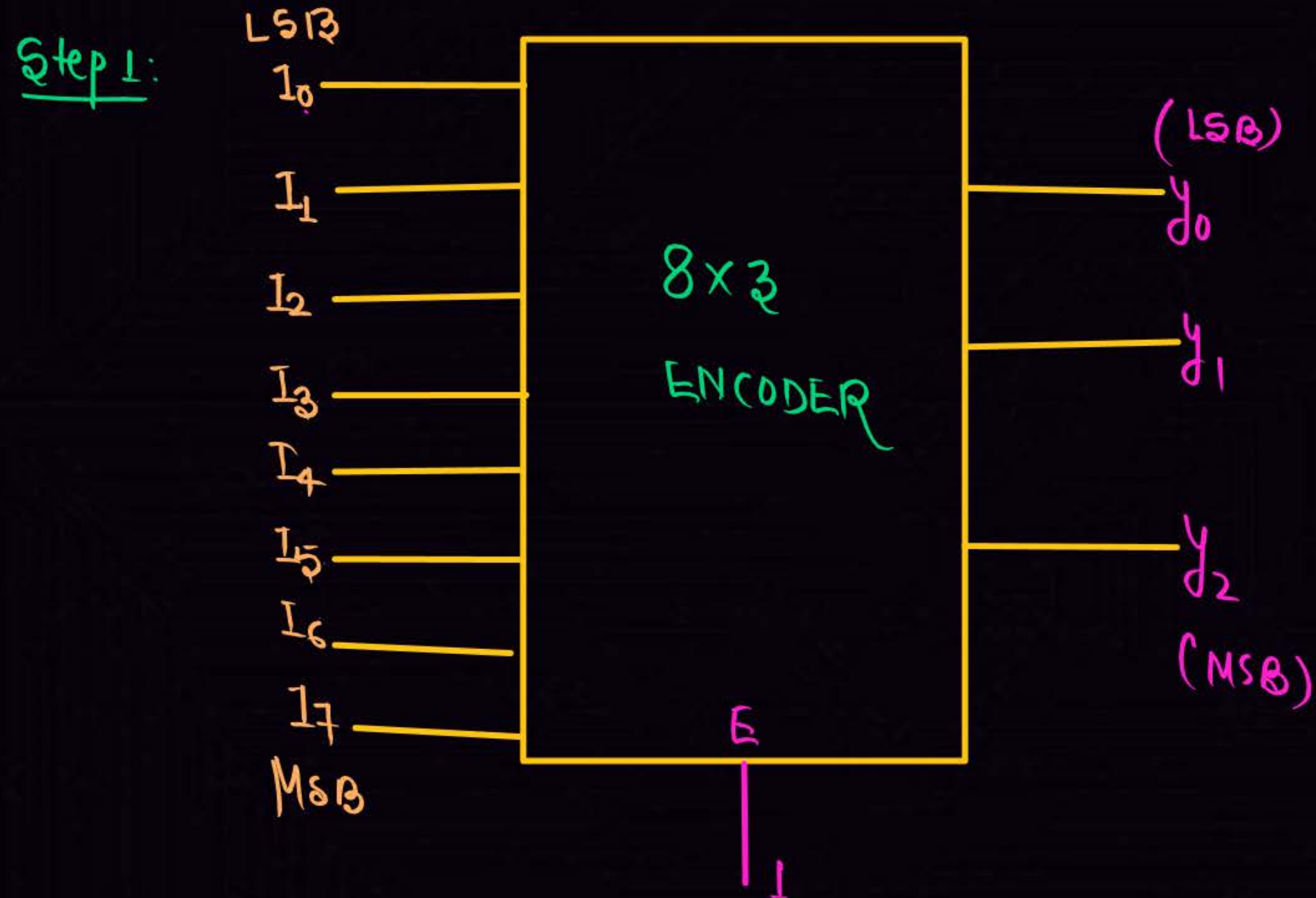

Step 2:

MSB								LSB		
I_7	I_6	I_5	I_4	I_3	I_2	I_1	I_0	y_2	y_1	y_0
0	0	0	0	0	0	0	1	0	0	0
0	0	0	0	0	0	1	0	0	0	1
0	0	0	0	0	1	0	0	0	1	0
0	0	0	0	1	0	0	0	0	1	1
0	0	0	1	0	0	0	0	1	0	0
0	0	1	0	0	0	0	0	1	0	1
0	1	0	0	0	0	0	0	1	1	0
1	0	0	0	0	0	0	0	1	1	1




Step 3: $y_0 = I_1 + I_3 + I_5 + I_7$

$y_1 = I_2 + I_3 + I_6 + I_7$

$y_2 = I_4 + I_5 + I_6 + I_7$


Step 4:

Step 5:

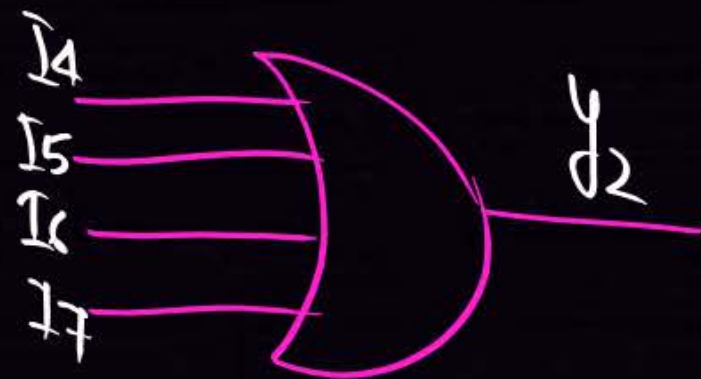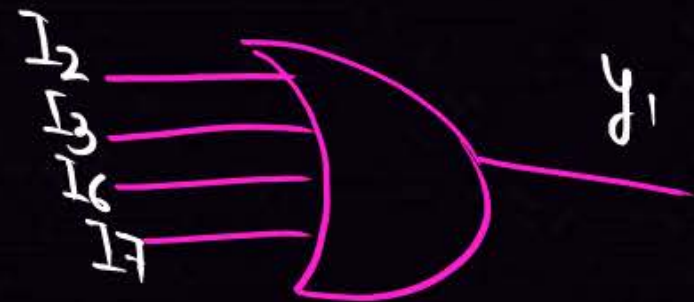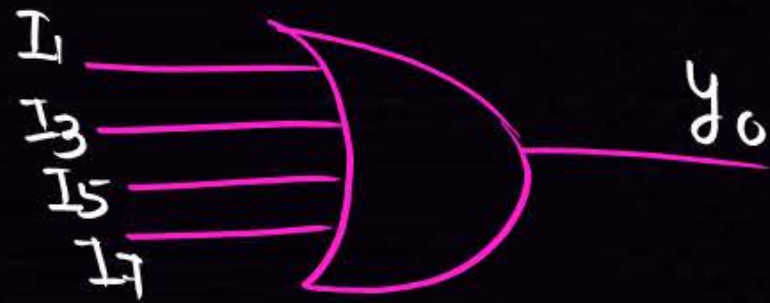

HW
Q Design a 16x4 ENCODER

NOTE :- PRIORITY ENCODER

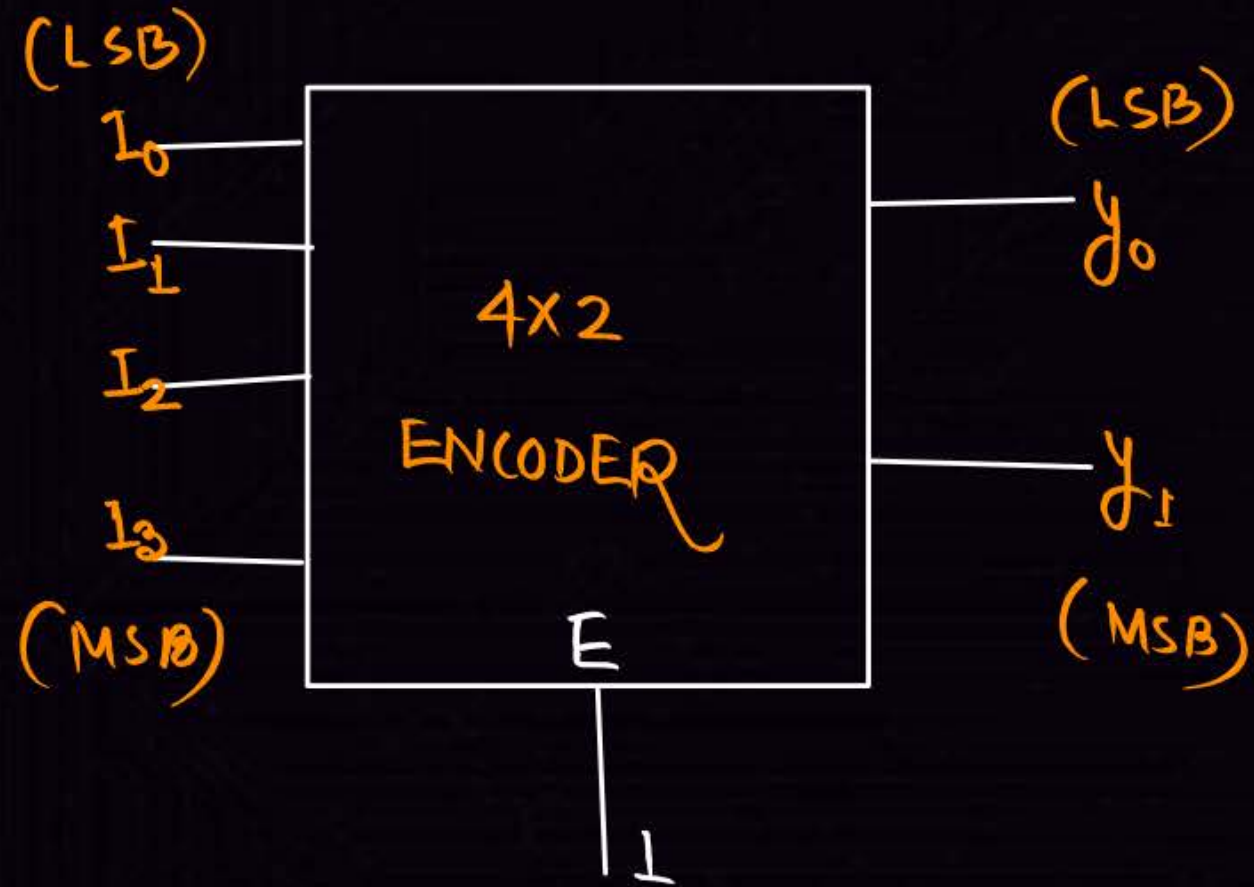

LSB priority Encoder

MSB				LSB	
I_3	I_2	I_1	I_0	y_1	y_0
X	X	X	1	0	0
X	X	1	0	0	1
X	1	0	0	1	0
1	0	0	0	1	1

→ weighted, self complemented

Decimal	BCD	Excess-3 code	4 2 2 1	Gray code
→ 0	0000	0011	0 0 0 0	
→ 1	0001	0100	0 0 0 1	
→ 2	0010	0101	0 0 1 0	
→ 3	0011	0110	0 0 1 1	
→ 4	0100	0111	0 1 1 0	
→ 5	0101	1000	1 0 0 1	
→ 6	0110	1001	1 1 0 0	
→ 7	0111	1010	1 1 0 1	
→ 8	1000	1011	1 1 1 0	
→ 9	1001	1100	1 1 1 1	

Decimal $\begin{cases} \rightarrow \text{Weighted code} \\ \rightarrow \text{Self complemented} \end{cases}$

$10^3 \quad 10^2 \quad 10^1 \quad 1$
 $a_3 \quad a_2 \quad a_1 \quad a_0$

5231

$r \rightarrow \underline{\text{Base (Radix)}}$

Complement

$(r-1)'s$

1's

7's

9's

$r's \text{ complement}$

2's

8's

10's

$r=2$

$r=8$

$r=10$

$9's$

3 $\xrightarrow{\text{9's complement}}$?
6

$$\begin{array}{r} 9 \\ - 3 \\ \hline 6 \end{array}$$

$$\begin{array}{r} 9 \\ - 6 \\ \hline 3 \end{array}$$

$$\begin{array}{r} 9 \quad 9 \\ - 0 \quad 9 \\ \hline 9 \leftrightarrow 0 \end{array}$$

$$\begin{array}{r} 9 \quad 9 \\ - 1 \quad 8 \\ \hline 8 \leftrightarrow 1 \end{array}$$

$$\begin{array}{r} 999 \\ - 236 \\ \hline 763 \\ \hline \end{array}$$

BCD $\begin{cases} \rightarrow \text{weighted code} \\ \rightarrow \text{Not a self complemented code} \end{cases}$
 \rightarrow Binary Coded Decimal

\rightarrow Each decimal numbers are represented by 4 bits.

$\begin{cases} \text{Decimal} \rightarrow 0 \\ \text{BCD} \rightarrow 0000 \end{cases}$

$\begin{cases} \text{Decimal} \rightarrow 9 \\ \text{BCD} \rightarrow 1001 \end{cases}$

$\begin{cases} \text{Decimal} \rightarrow 29 \\ \text{BCD} \rightarrow 00101001 \end{cases}$

$\begin{cases} \text{Decimal} \rightarrow 3 \\ \text{BCD} \rightarrow 0011 \end{cases}$

Decimal $\rightarrow 10$
 BCD $\rightarrow 00010000$

Excess-3 Code \Rightarrow

\rightarrow It is not a weighted code

\rightarrow Self complemented code

Thank you

GW
Soldiers!

