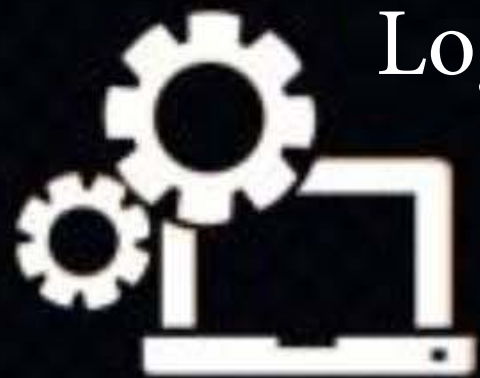


# CS & IT ENGINEERING

Digital Logic  
Logic Gate



**Lecture No. 5**



By- CHANDAN SIR



# TOPICS TO BE COVERED

**01** NAND GATE

**02** NOR GATE

**03** Discussion

$$f(A, B, C) = \bar{A} B C$$



$$1 + 2 + 2 = 5$$



$$f(A,B,C) = AB + CD \\ \equiv$$

3



Case (1)  $A \cdot B \cdot \bar{C} \cdot D \cdot E \dots$

**NAND**

$$\Rightarrow (2n-2) + k$$

$n \rightarrow$  Total no. of Variable

$k \rightarrow$  Total no. of complement Variable.

**NOR**

$$\Rightarrow (3n-3) - k$$

$n \rightarrow$  no. of Variables

$k \rightarrow$  no. of complement Variables.

Ex

$$f = A \cdot \bar{B} \cdot C$$

$$n = 3$$

$$k = 1$$

**NAND**

$$(2n-2) + k$$

$$= (2 \times 3 - 2) + 1$$

$$= 5 \text{ Ans}$$

**NOR**

$$(3n-3) - k$$

$$(3 \times 3 - 3) - 1$$

$$6 - 1$$

$$= 5 \text{ Ans}$$

Ex.  $f = \bar{A}B\bar{C}D$

$n=4$     $k=2$

NAND

$$(2n-2)+k$$

$$\Rightarrow (2 \times 4 - 2) + 2$$

$$= 8$$

Ans

NOR

$$(3n-3)-k$$

$$(3 \times 4 - 3) - 2$$



$$= 7$$

Ans



NAND

$$f = \bar{A}BC$$

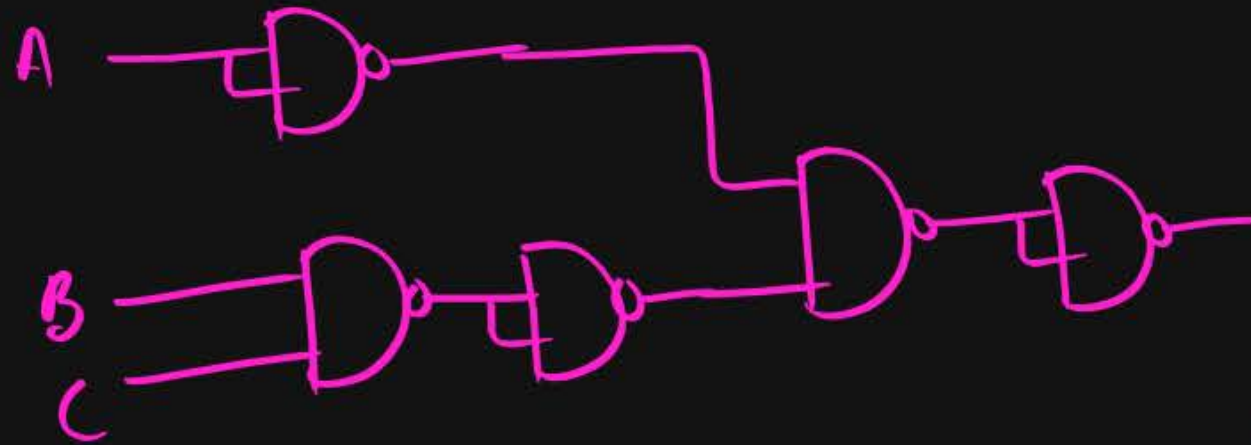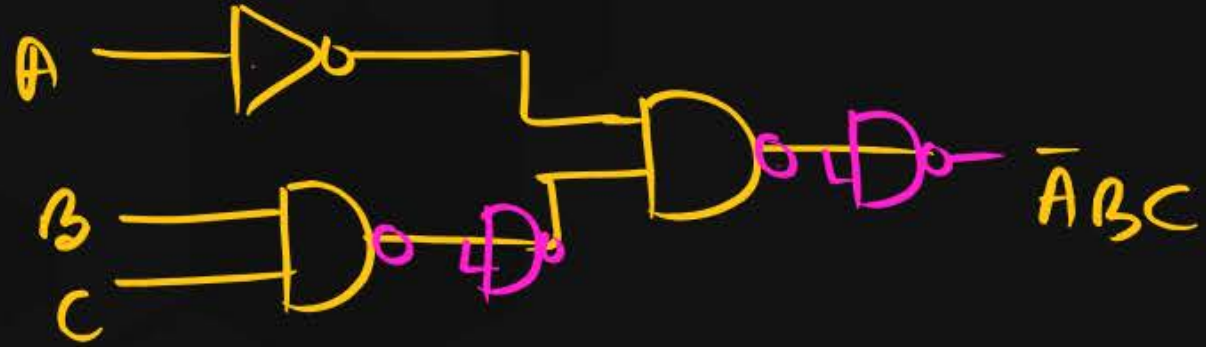

5 AP



NAND



$$f = A \cdot B \cdot \bar{C} \cdot \bar{D}$$

$$n=4 \quad K=2$$

$$(2n-2)+K$$

$$=(2 \times 4 - 2) + 2$$

$$= 8$$

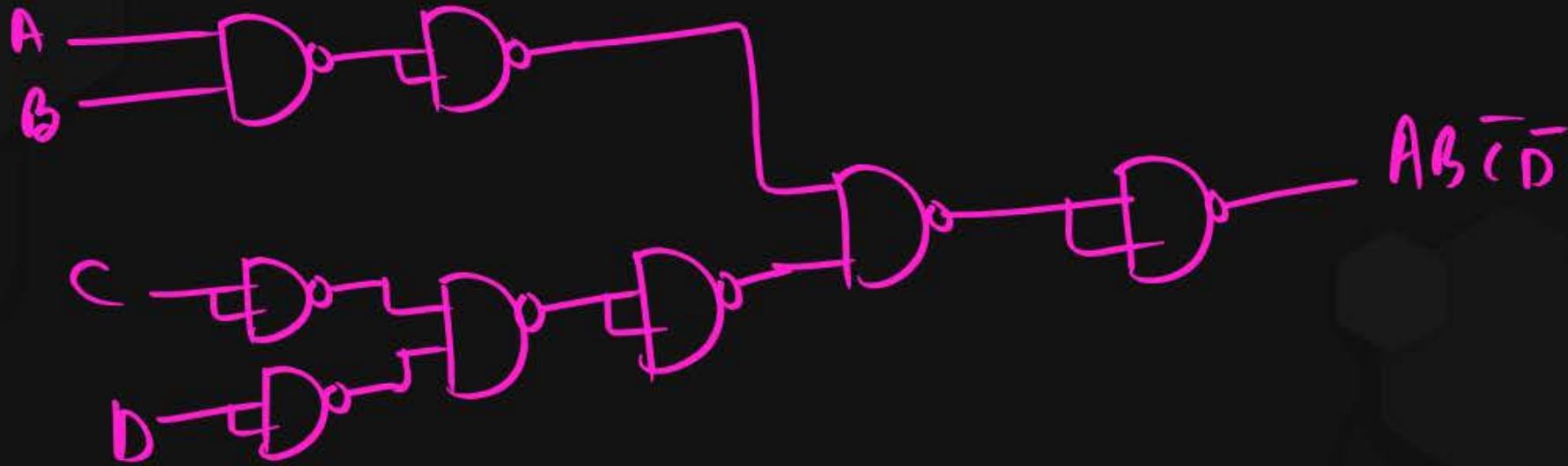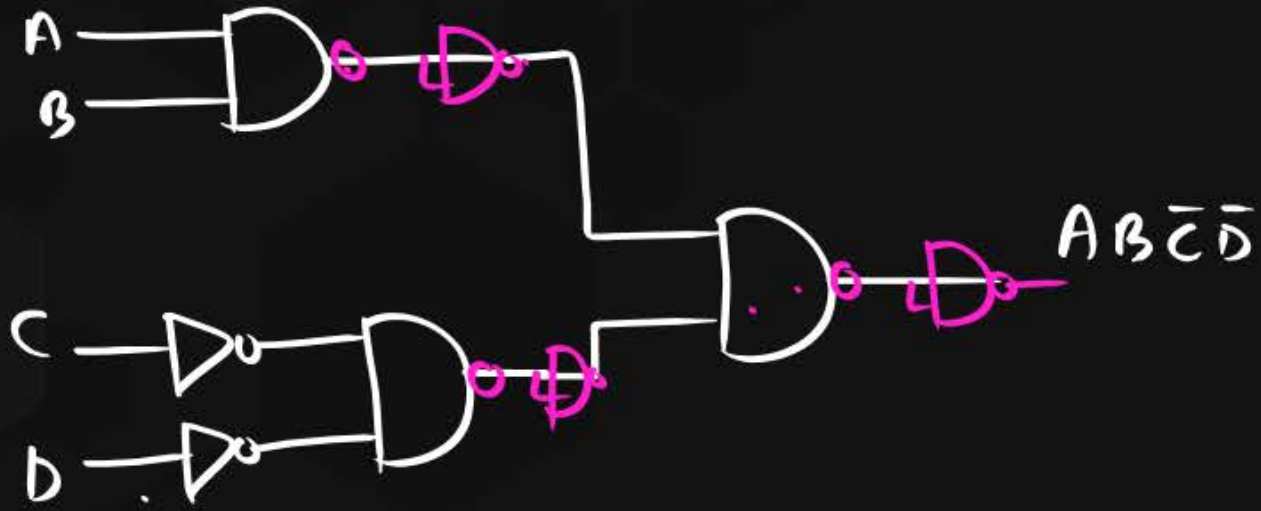


Q  $f = \bar{A}BCDE$

$n=5$   $k=1$

$NAND \Rightarrow (2n-2)+k$

$\Rightarrow (2 \times 5 - 2) + 1$

$= 9$  Ans

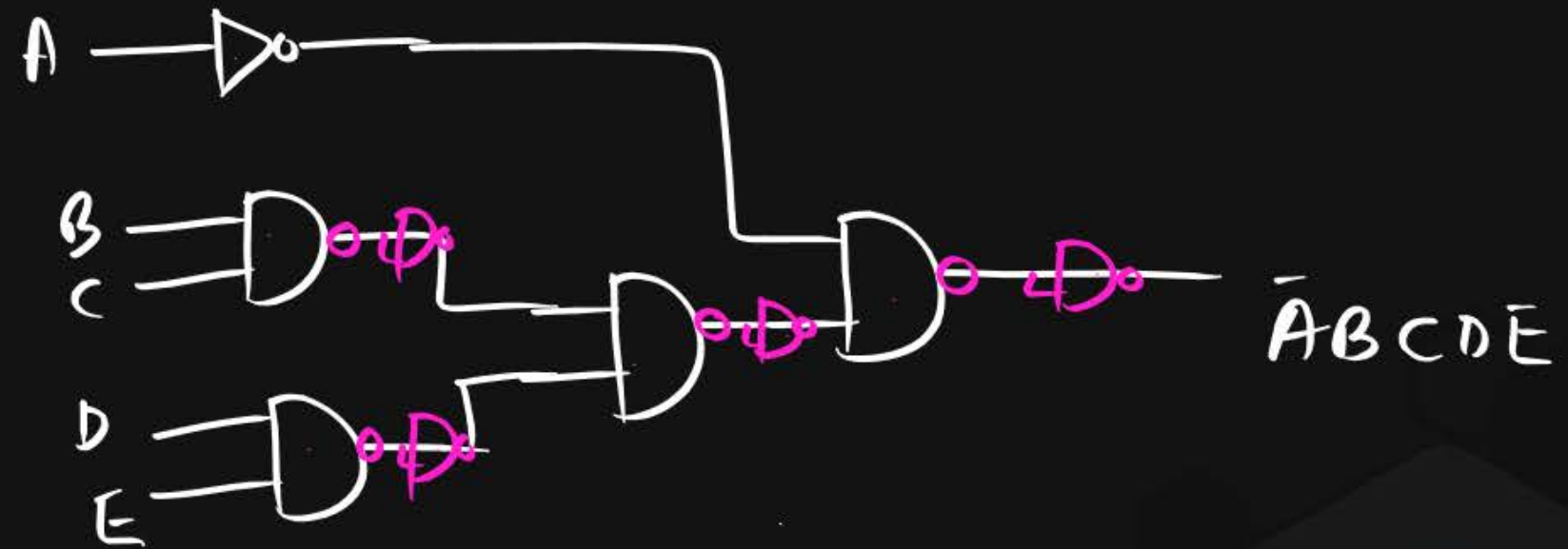

Case (2)  $A+B+\bar{C}+D+\bar{E}+\bar{F}+\dots\dots\dots$

NAND

$$(3n-3)-k$$

NOR


$$(2n-2)+k$$

Ex  $f = \bar{A} + B \quad n=2 \quad k=1$


$$\begin{aligned} \underline{\text{NAND}} &= (3n-3)-k \\ &= (3 \times 2 - 3) - 1 \\ &= 9 \text{ Ans.} \end{aligned}$$

$$\begin{aligned} \underline{\text{NOR}} &= (2n-2)+k \\ &= (2 \times 2 - 2) + 1 \\ &= 3 \text{ Ans.} \end{aligned}$$



$$\bar{A} + B$$

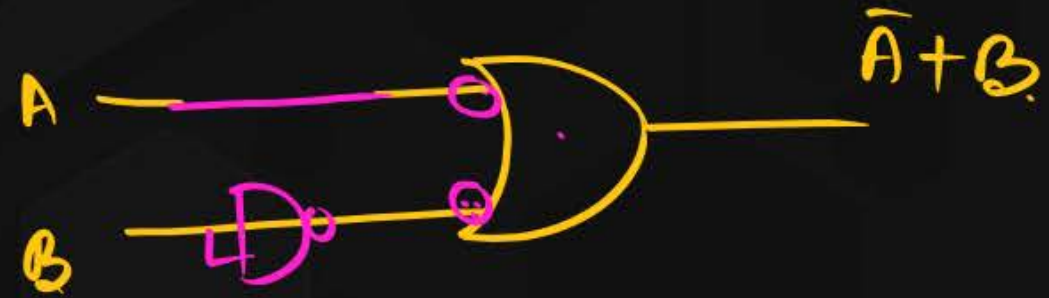

NAND = 2.

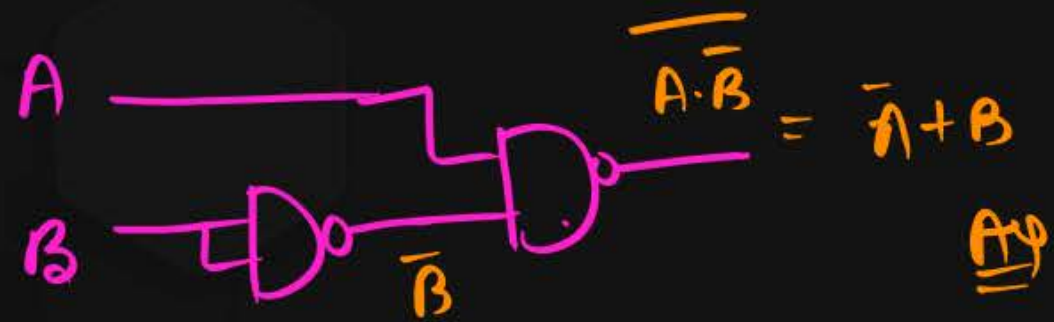

$$\bar{A} + B$$

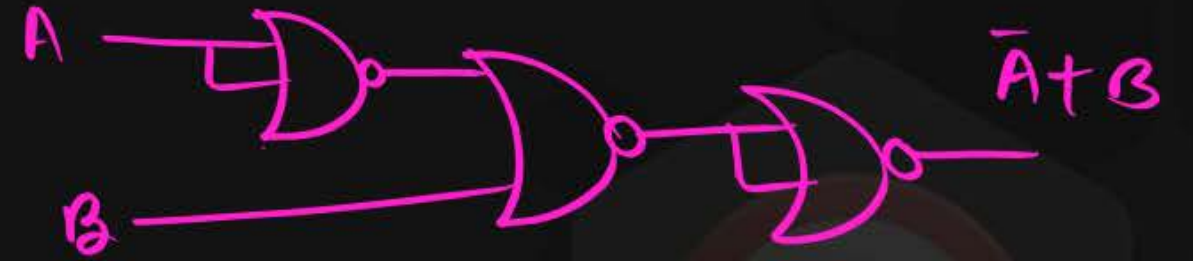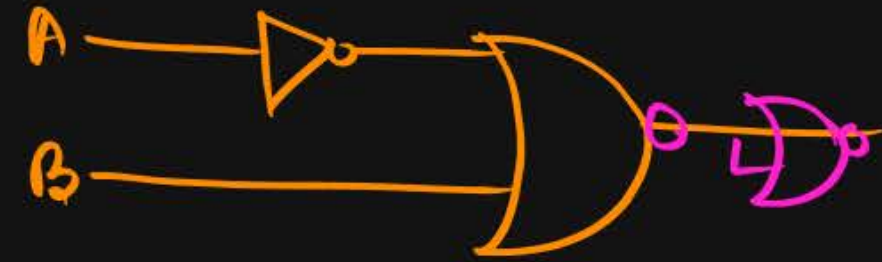



Q  $f = \bar{A} + \bar{B} + C$





NAND  $n=3$   $k=2$

$$\Rightarrow (3n-3)-k$$

$$= (3 \times 3 - 3) - 2$$

$$= 4$$

Ans

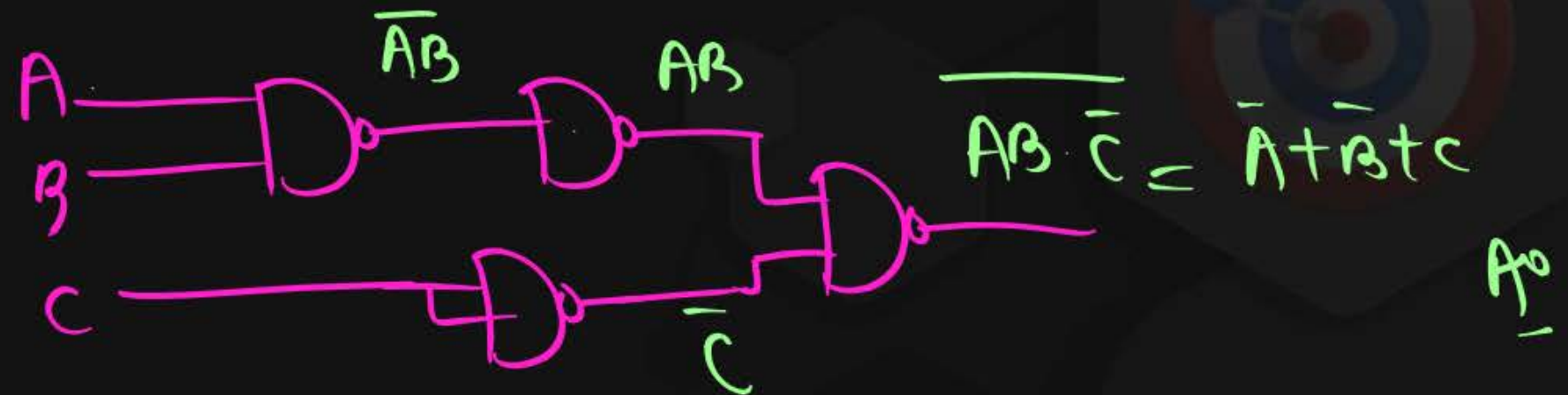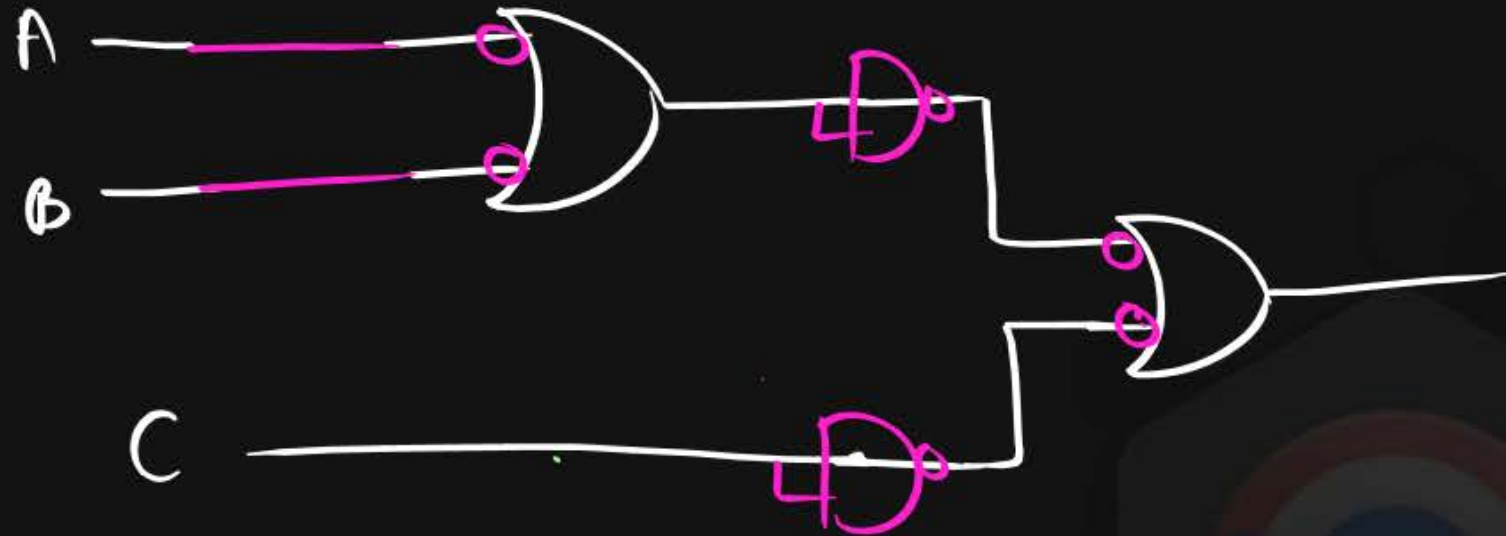

Q



$$f = \bar{A} + \bar{B} + C$$

NOR


$$(2n-2)+K$$

$$(2 \times 3 - 2) + 2$$

$$6 = \underline{\underline{Ans}}$$

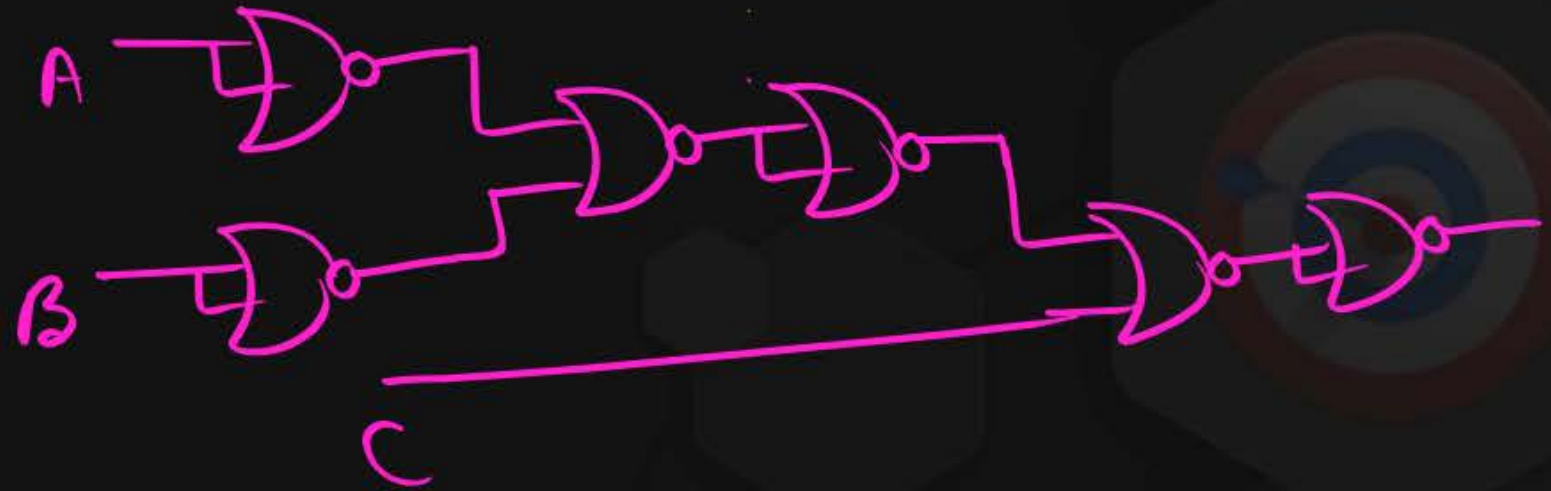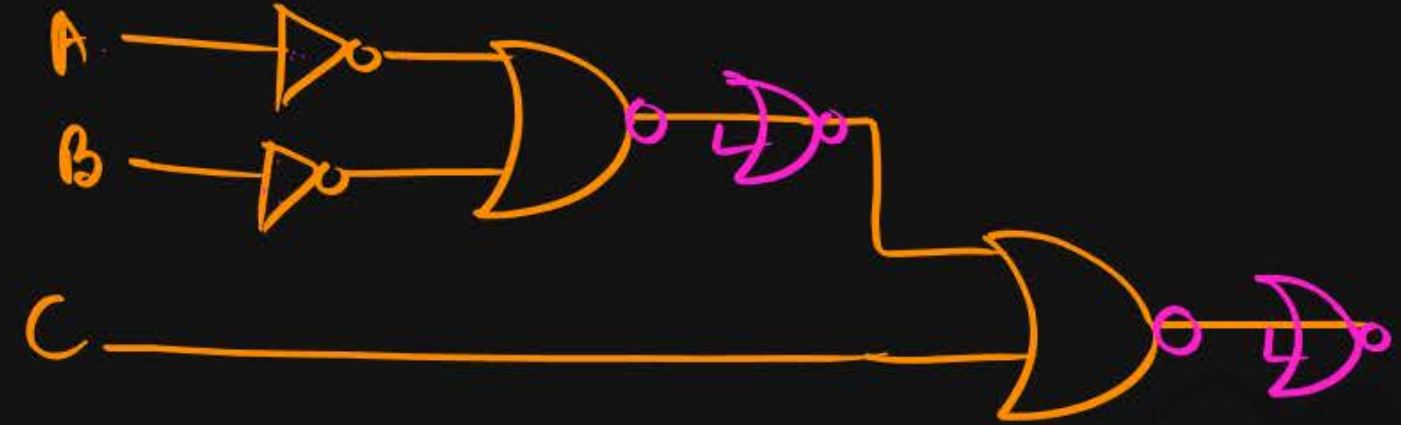

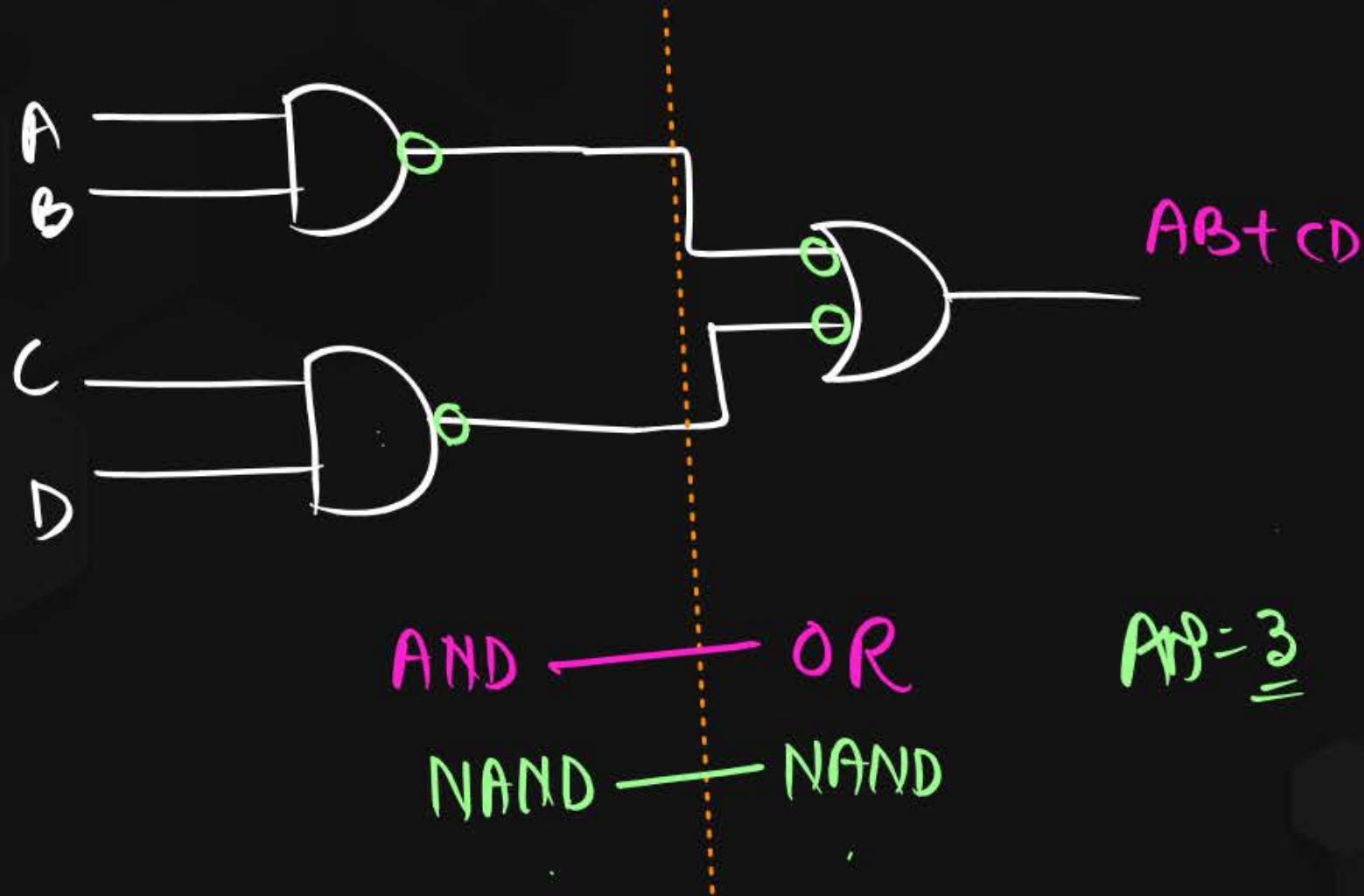Case(3)  $f = AB + CD$   $\rightarrow$  SOP Sum of product  
Type function



AOI  
AND-OR-Inverter

AB = 3



₹100

NOTE → Whenever in the problem minimum number of NAND GATE are asked, then write the function in SOP form and Implement it by using AOI which is a AND-OR Implementation and this is exactly equal to NAND-NAND Implementation.




Q  $A+BC$

NAND?

$$A \cdot A + BC$$

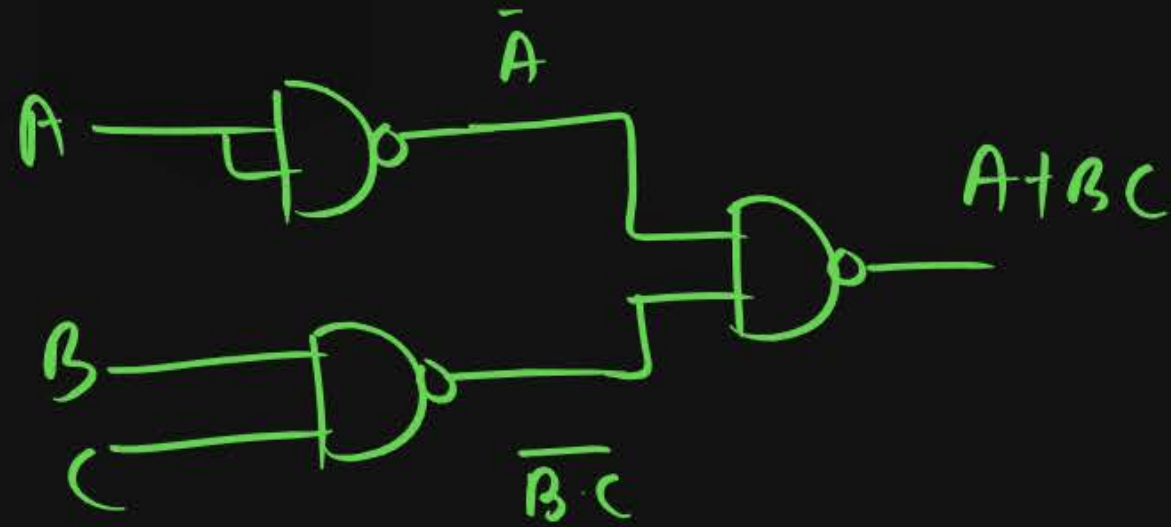
$$\overline{\overline{A} \cdot \overline{BC}} = A + BC$$



Q  $f = \overline{A\bar{B}} + CD$

3 NAND


1 NAND

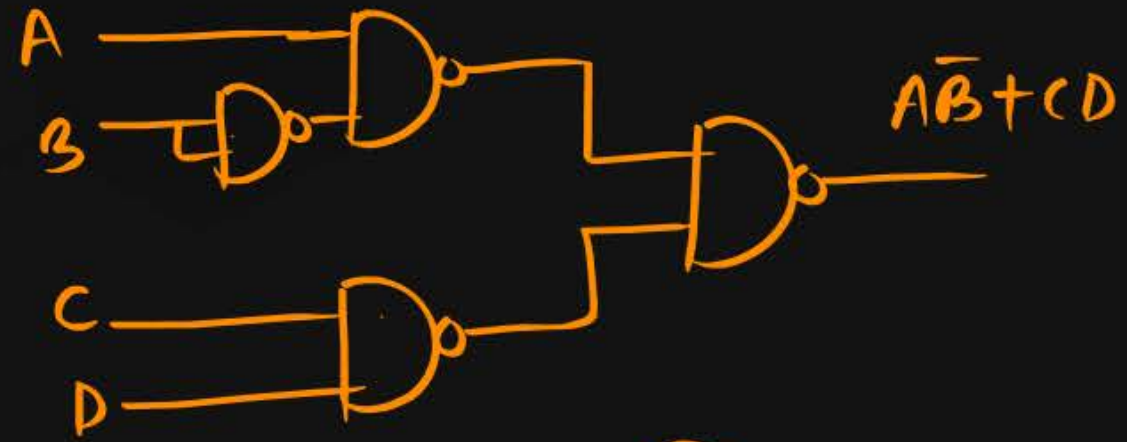

④ Ans

$$\underline{Q} \quad f = A + B$$

$$= A \cdot A + B \cdot B$$

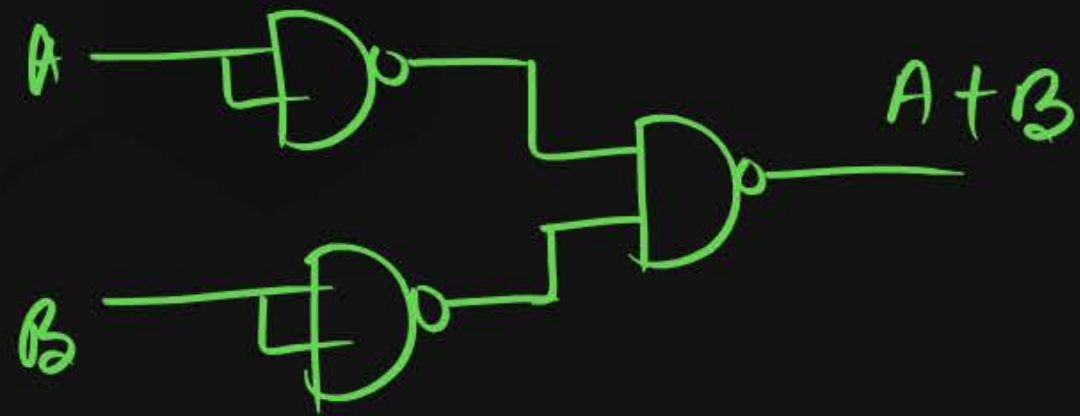


Q  $f = AB + CD + E$

NAND = ?

$f = X + E$

$X = AB + CD$

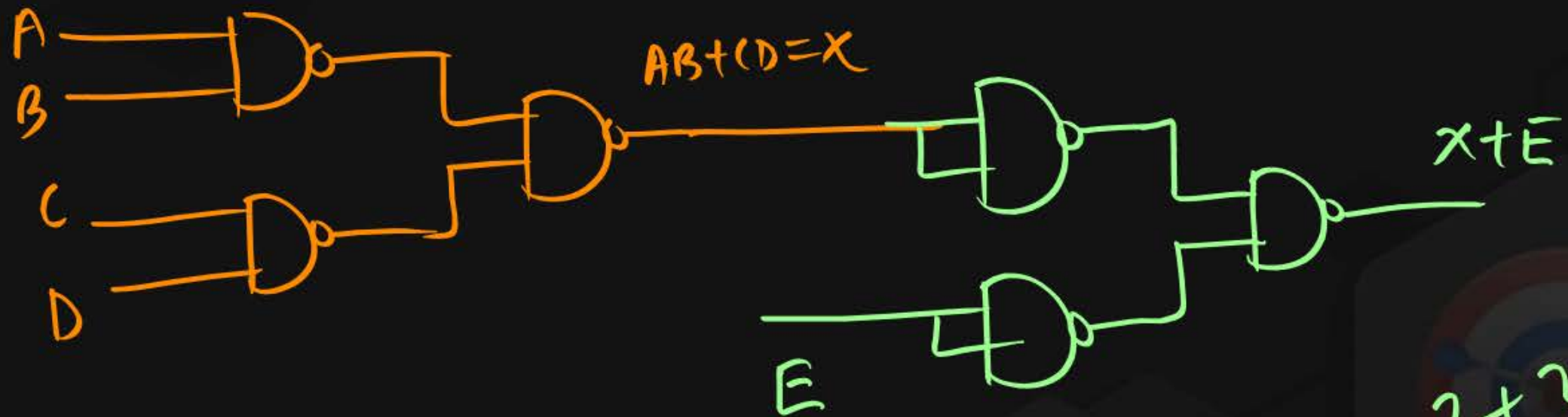

$3 + 3 = 6$



$$\textcircled{3} \quad X + E \quad \text{---} \quad \textcircled{3}$$

$$X = AB + CD$$

$$\text{---} \quad \textcircled{3}$$


$$3 + 3 = 6$$

$$f = \overset{3}{\textcircled{AB + CD}} + E$$

$\text{---} \quad X$



$$= X + E \rightarrow 3 + 3 = 6$$

$$X + E$$

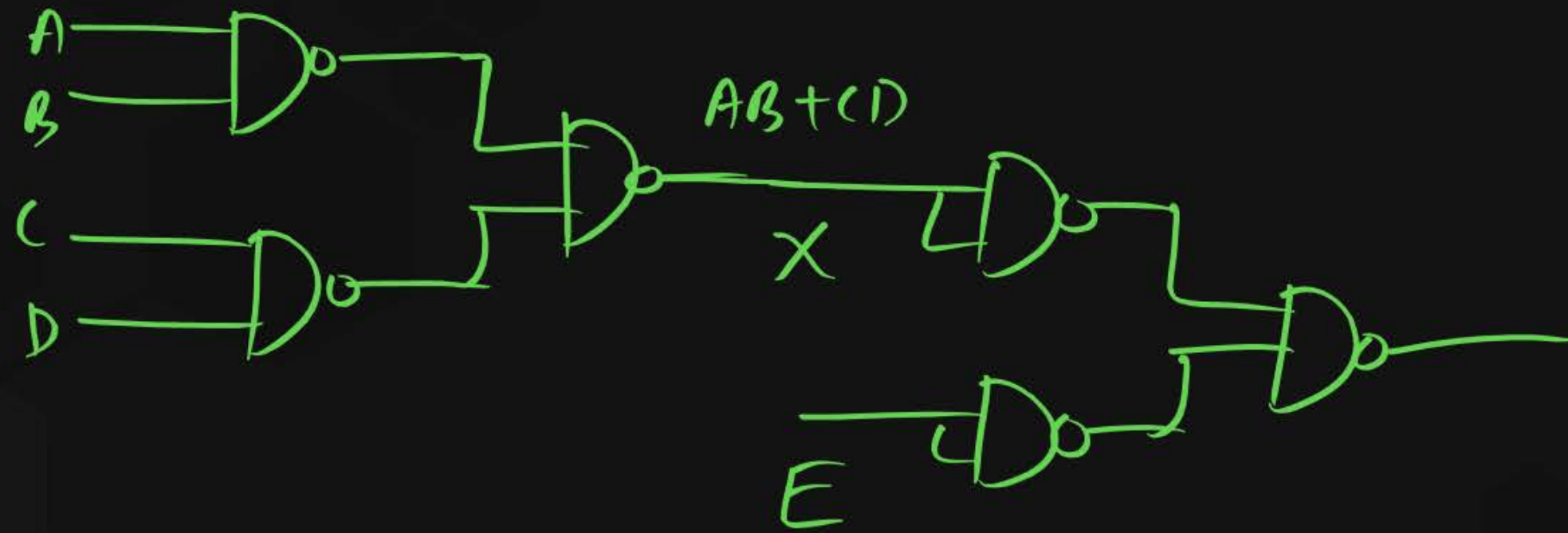

Q

$$\underline{AB + CD + EF}$$

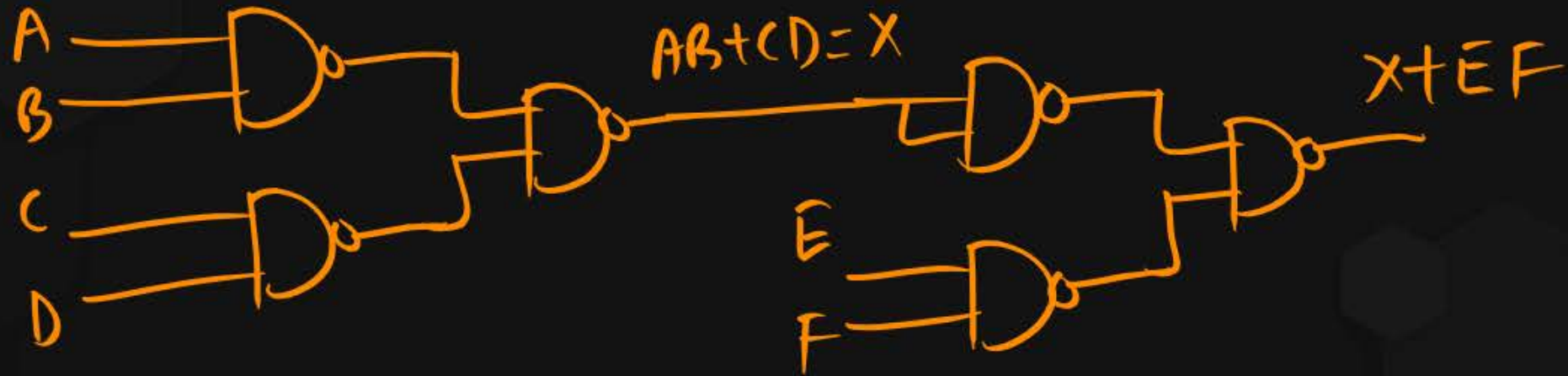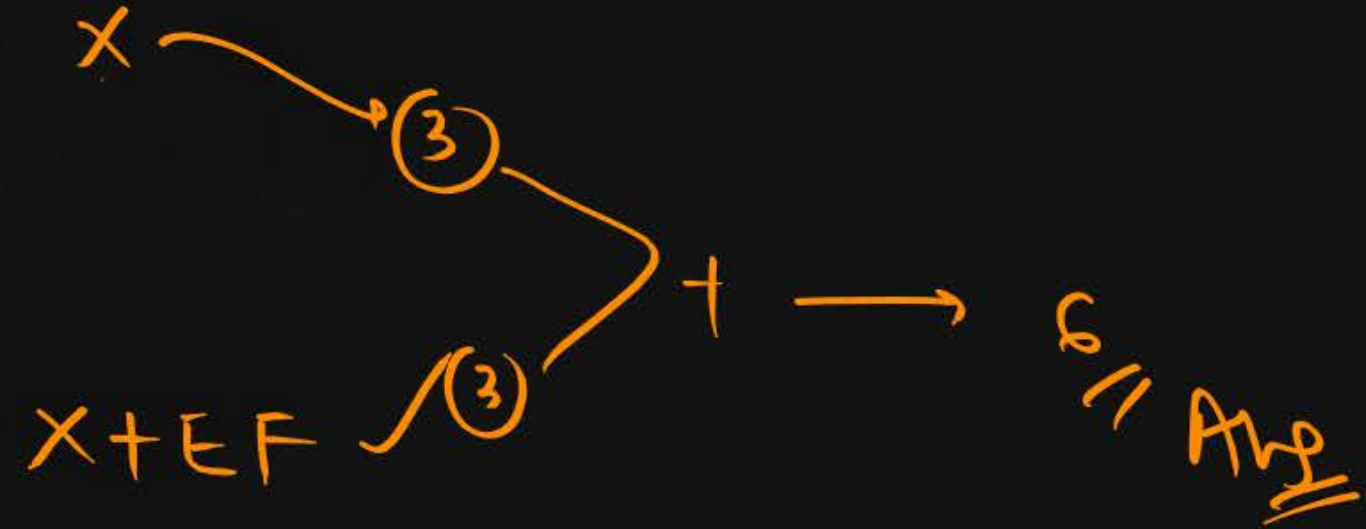


$$Q = \overline{A}\overline{B} + CD$$

③

NAND=?

⑤

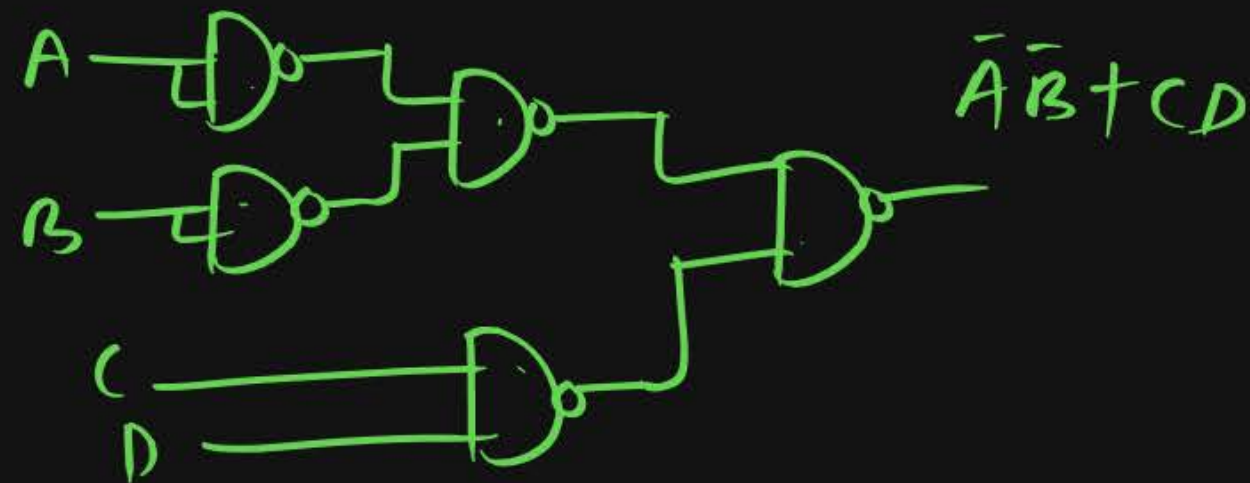



**Thank you**

**GW**  
*Soldiers !*

